

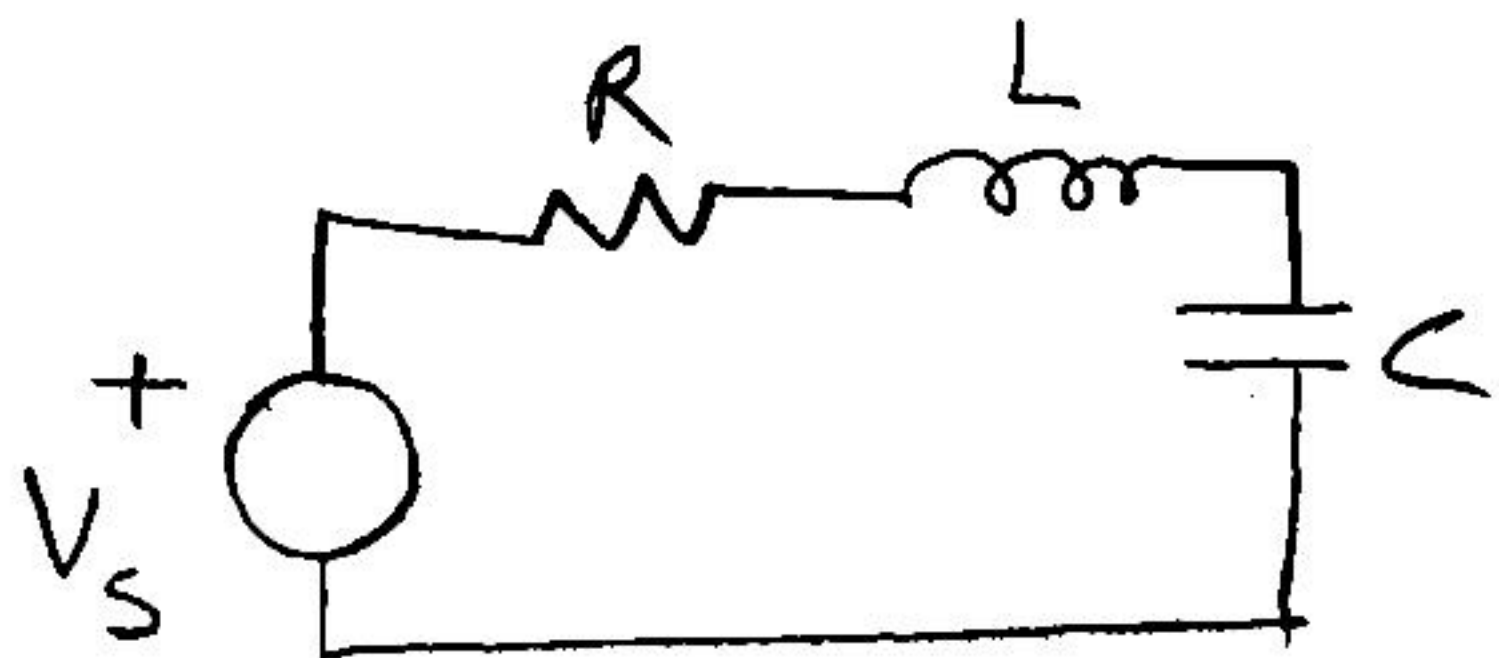


e21

Sinusoidal steady state Analysis

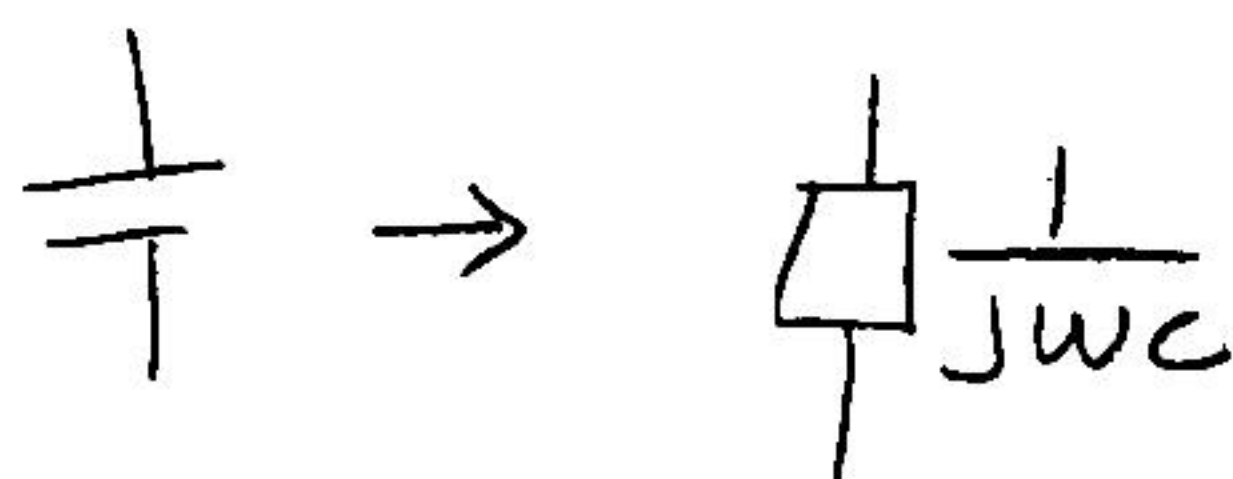

$$V_s = A \cos(\omega t + \phi)$$

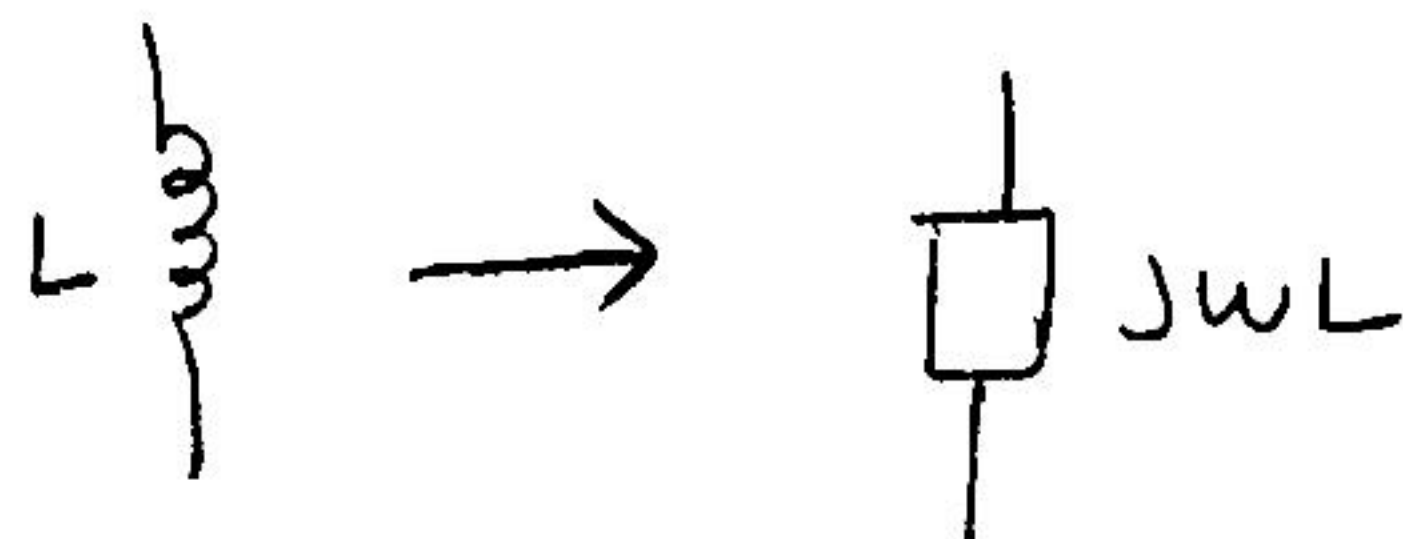

$$A \cos(\omega t + \phi) \rightarrow A e^{j\phi} \quad A \angle \phi$$

EXAMPLE 9.6

A $90 \, \Omega$ resistor, a $32 \, \text{mH}$ inductor, and a $5 \, \mu\text{F}$ capacitor are connected in series across the terminals of a sinusoidal voltage source, as shown in Fig. 9.15. The steady-state expression for the source voltage v_s is $750 \cos(5000t + 30^\circ) \, \text{V}$.

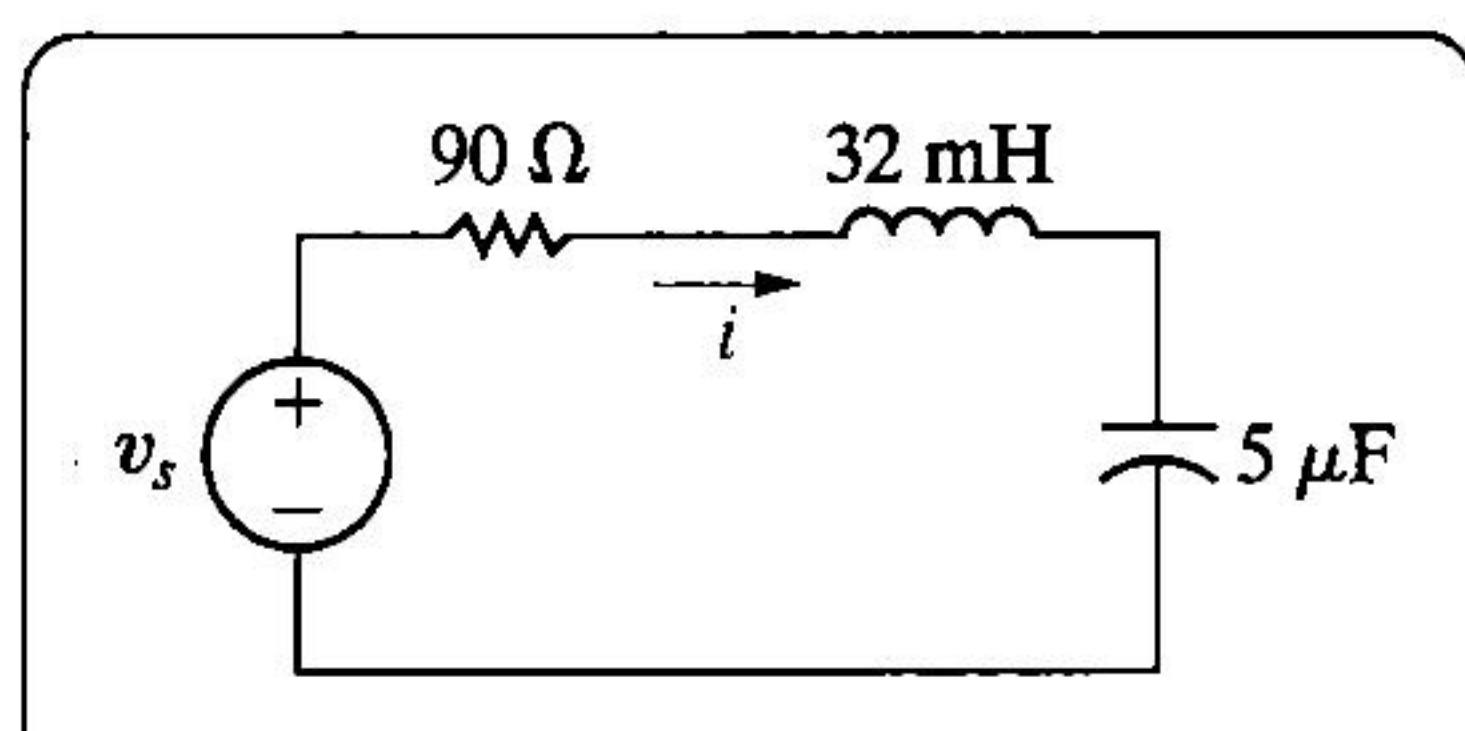


Figure 9.15 The circuit for Example 9.6.

a) Construct the frequency-domain equivalent circuit.

b) Calculate the steady-state current i by the phasor method.

SOLUTION

a) From the expression for v_s , we have $\omega = 5000 \, \text{rad/s}$. Therefore the impedance of the $32 \, \text{mH}$ inductor is

$$Z_L = j\omega L = j(5000)(32 \times 10^{-3}) = j160 \, \Omega,$$


and the impedance of the capacitor is

$$Z_C = j \frac{-1}{\omega C} = -j \frac{10^6}{(5000)(5)} = -j40 \, \Omega.$$


The phasor transform of v_s is

$$V_s = 750 \angle 30^\circ \, \text{V}.$$

Figure 9.16 illustrates the frequency-domain equivalent circuit of the circuit shown in Fig. 9.15.

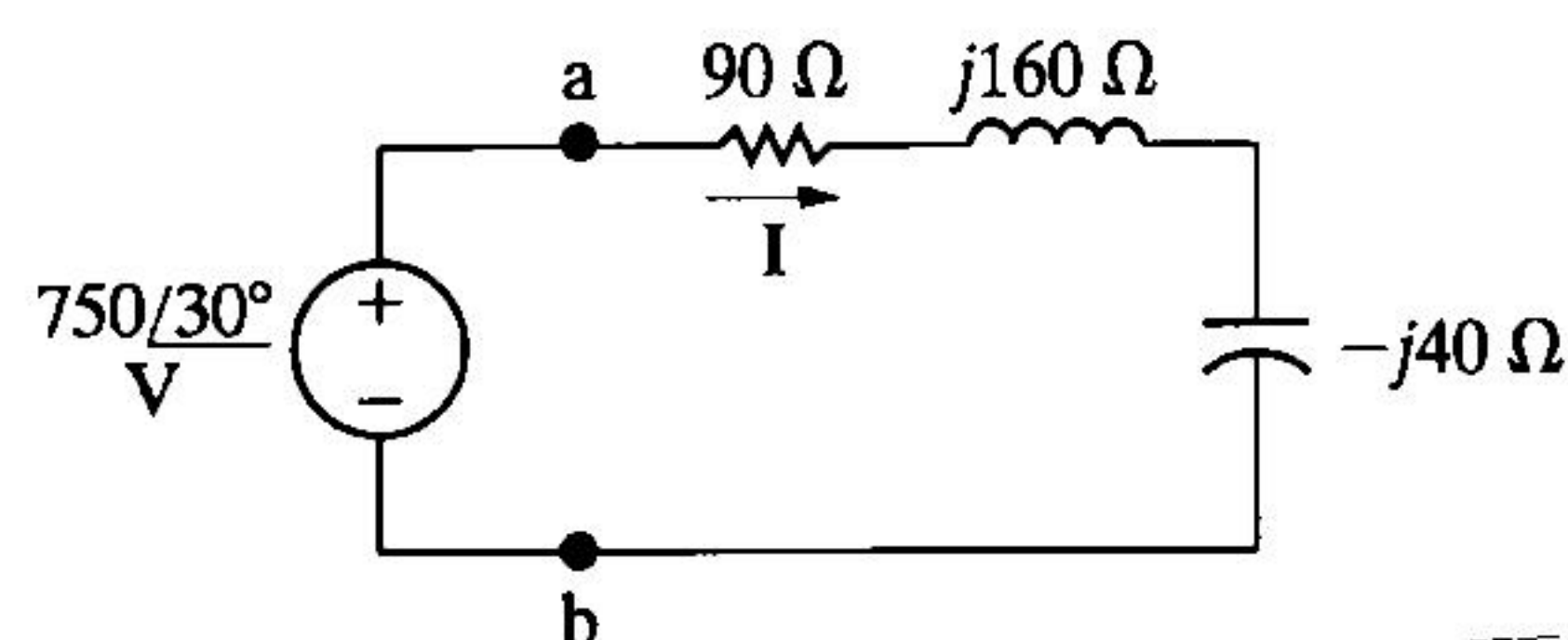
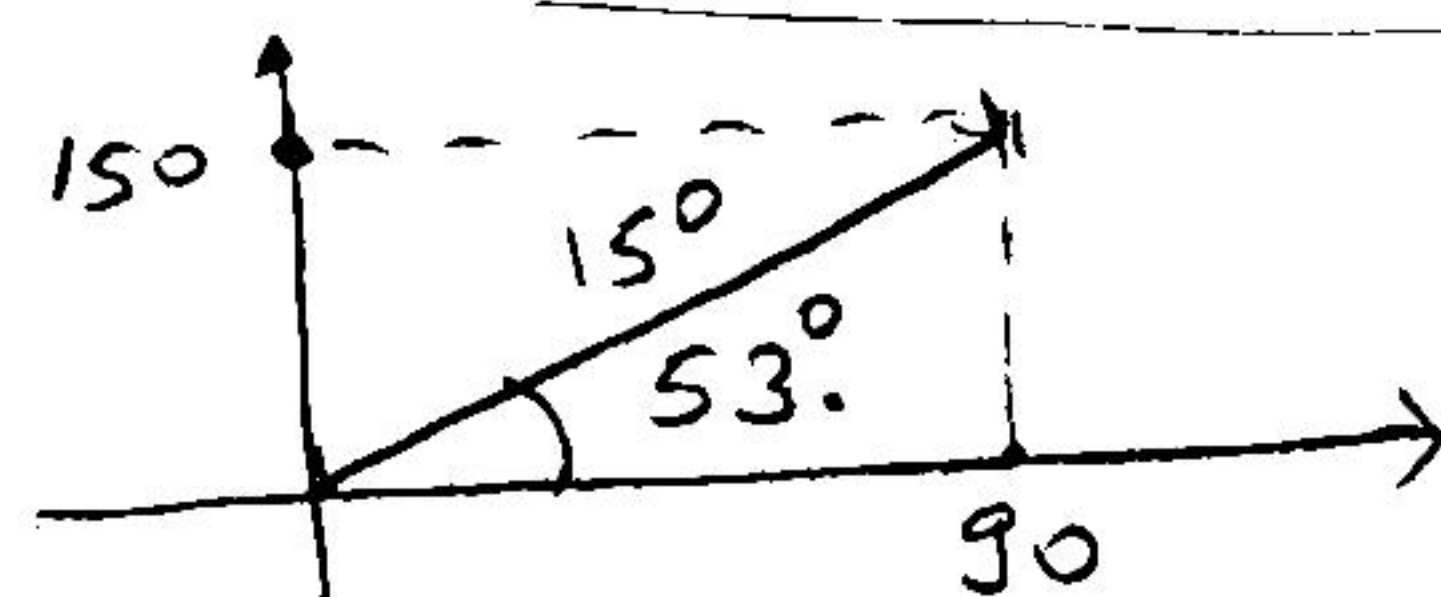
$$\begin{aligned} Z_{ab} &= 90 + j160 - j40 \\ &= 90 + j120 = 150 \angle 53.13^\circ \, \Omega. \end{aligned}$$



$$I = \frac{750 \angle 30^\circ}{150 \angle 53.13^\circ} = 5 \angle -23.13^\circ \, \text{A}.$$

$$i = 5 \cos(5000t - 23.13^\circ) \, \text{A}.$$

EXAMPLE 9.7

The sinusoidal current source in the circuit shown in Fig. 9.18 produces the current $i_s = 8 \cos 200,000t$ A.

- Construct the frequency-domain equivalent circuit.
- Find the steady-state expressions for v , i_1 , i_2 , and i_3 .

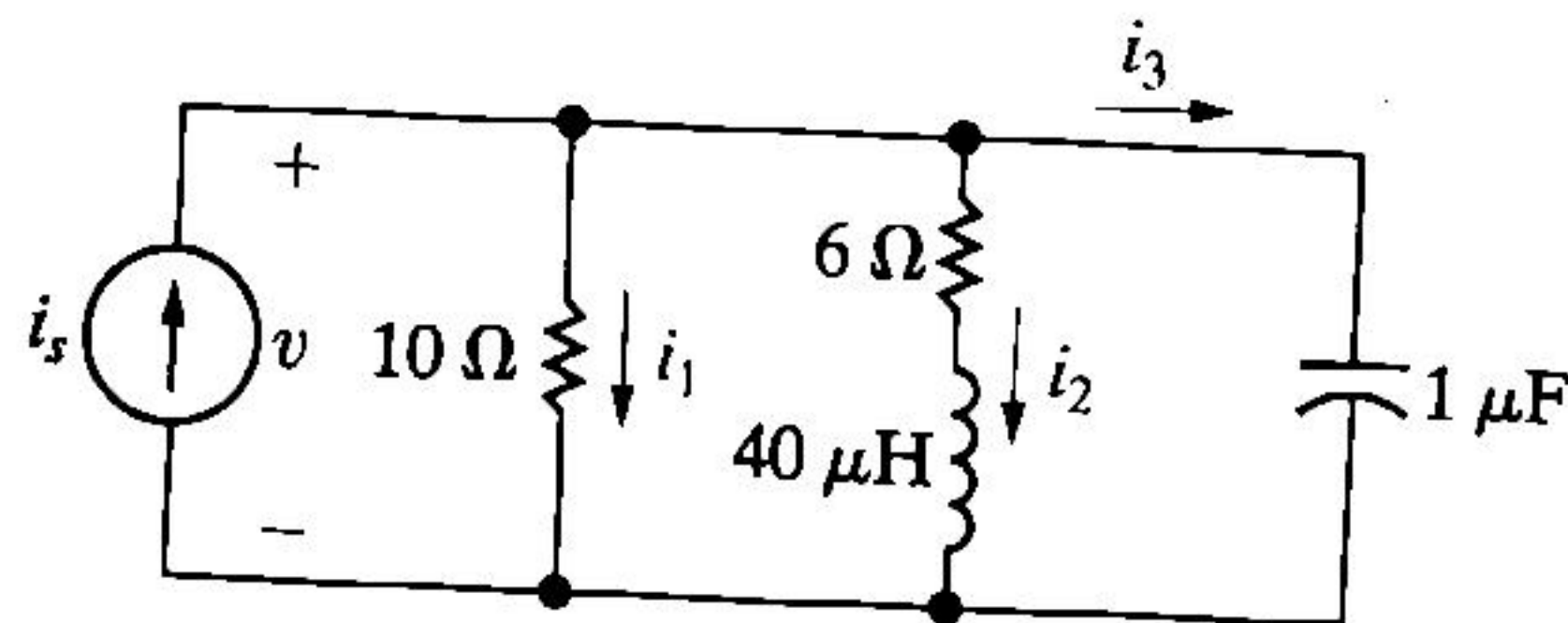


Figure 9.18 The circuit for Example 9.7.




SOLUTION

$$\omega = 200,000$$

$$40 \mu\text{H} \rightarrow j\omega L = j \times 200,000 \times 40 \times 10^{-6} = j8$$

$$1 \mu\text{F} \rightarrow \frac{1}{j\omega C} = \frac{1}{j \times 200,000 \times 1 \times 10^{-6}} = \frac{1}{j0.2} = -j5$$

Note: $\frac{1}{j} = -j$

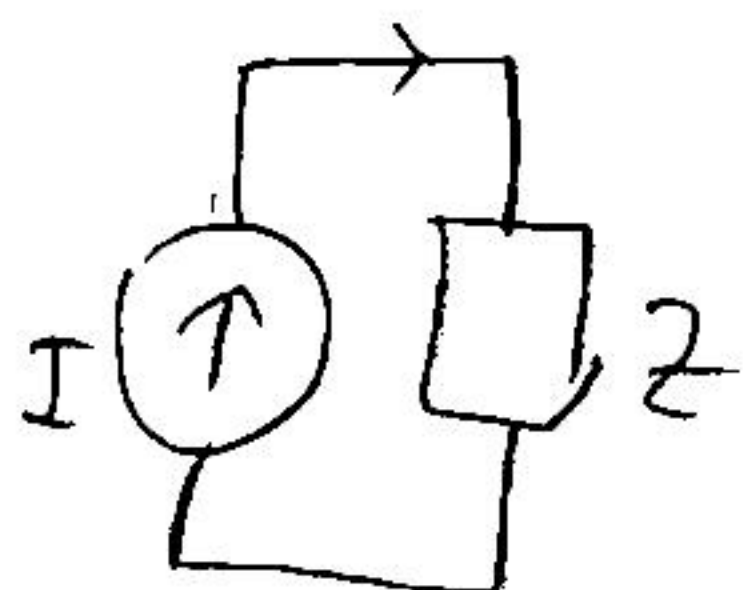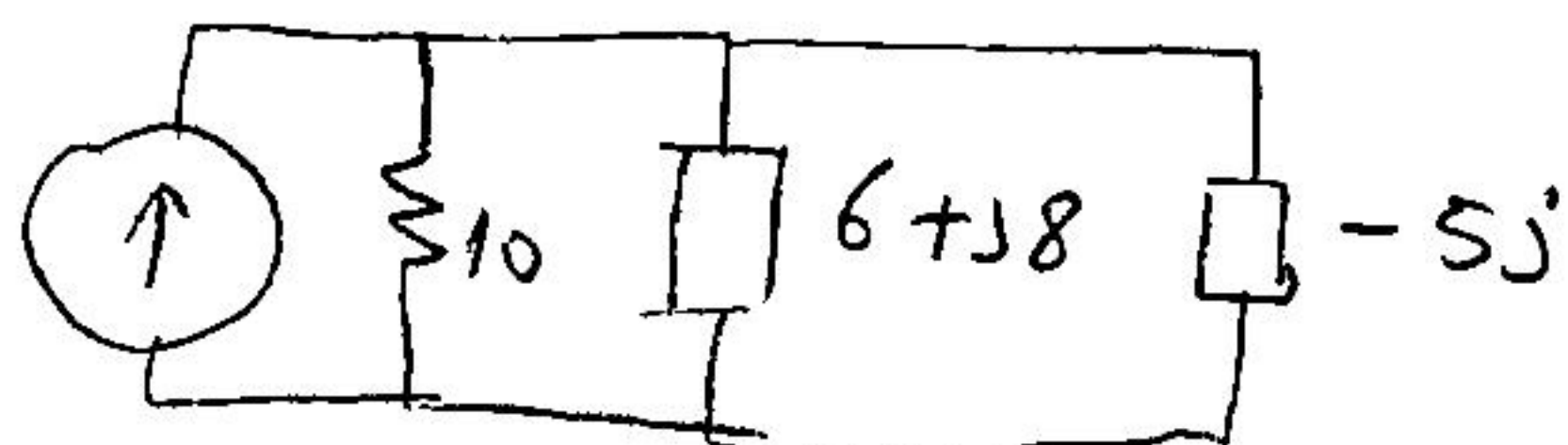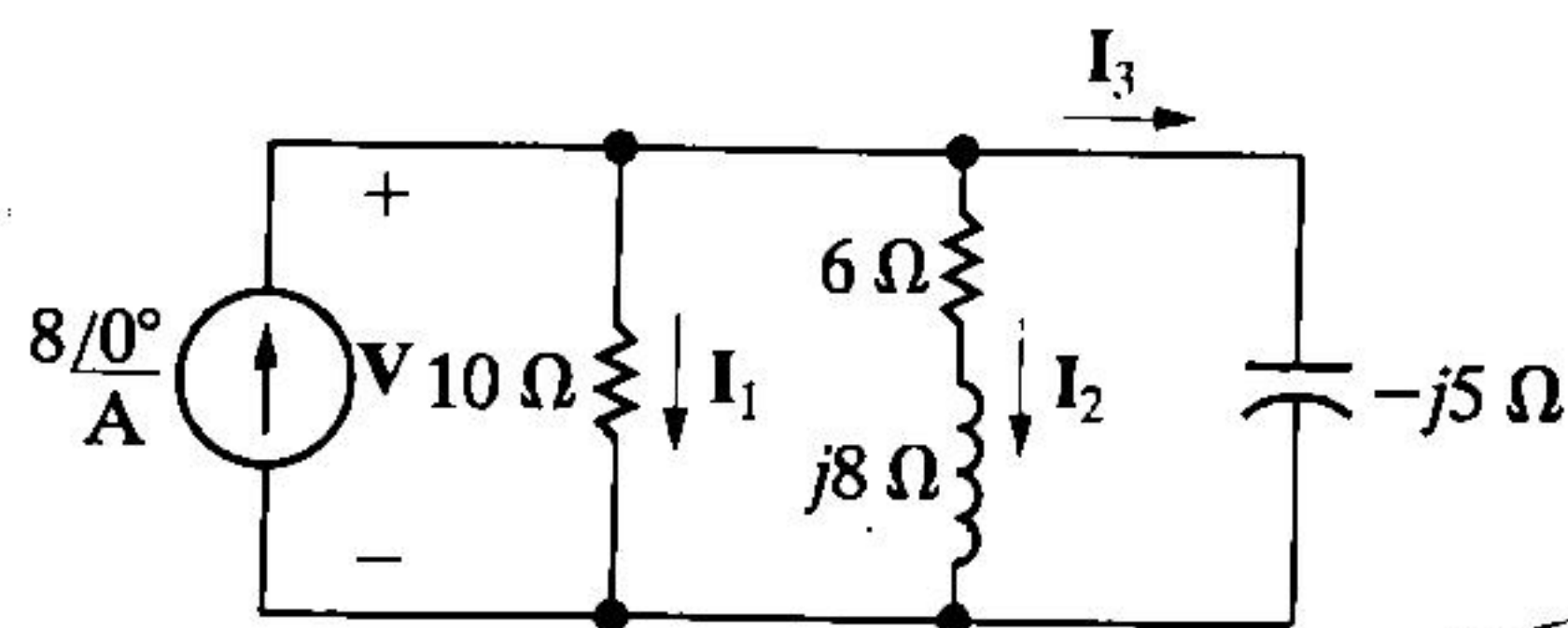

$$\frac{1}{Z} = \frac{1}{10} + \frac{1}{6+j8} + \frac{1}{-j5}$$

$$= 0.1 + 0.06 - j0.08 + 0.2j$$

$$\frac{1}{6+j8} = \frac{6-j8}{100} = 0.06 - j0.08$$

Note: $\frac{1}{a+bj} = \frac{a-bj}{a-bj} \frac{1}{a+bj} = \frac{a-bj}{a^2+b^2}$

$$\frac{1}{Z} = 0.16 + 0.12j$$

$$= \sqrt{0.16^2 + 0.12^2} \angle \tan^{-1} \frac{0.12}{0.16}$$


$$= 0.2 \angle 36.8^\circ$$

$$Z = \frac{1}{0.2 \angle 36.8} = \frac{1}{0.2} \angle -36.8 = 5 \angle -36.8$$

$$V = Z I = 5 \angle -36.8 \times 8 = 40 \angle -36.8$$

$$I_1 = \frac{V}{R} = \frac{40 \angle -36.8}{10} = 4 \angle -36.8$$
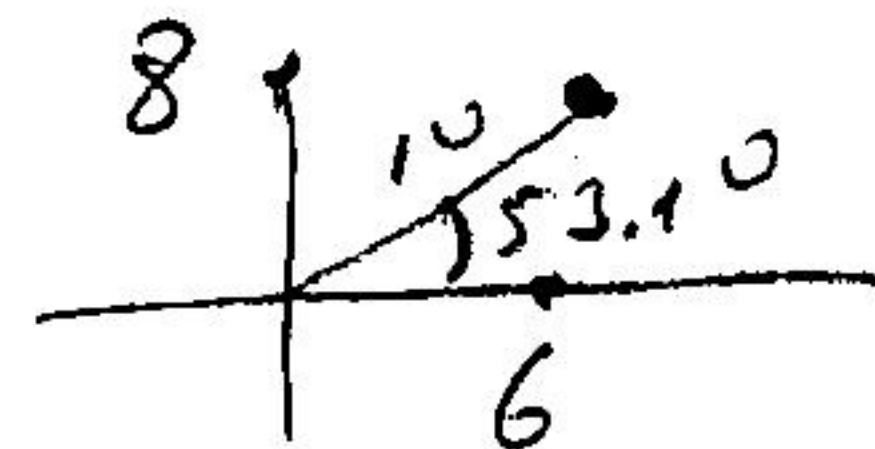
$$I_2 = \frac{V}{6+j8} = \frac{40 \angle -36.8}{10 \angle 53.1} = 4 \angle 90$$



$$I_3 = \frac{V}{-j5} = \frac{40 \angle -36.8}{5 \angle -90} = 8 \angle 53.2$$

The corresponding steady-state time-domain expressions are

$$v = 40 \cos(200,000t - 36.87^\circ) \text{ V},$$


$$i_1 = 4 \cos(200,000t - 36.87^\circ) \text{ A},$$

$$i_2 = 4 \cos(200,000t - 90^\circ) \text{ A},$$

$$i_3 = 8 \cos(200,000t + 53.13^\circ) \text{ A}.$$

Sinusoidal steady state power

EP1

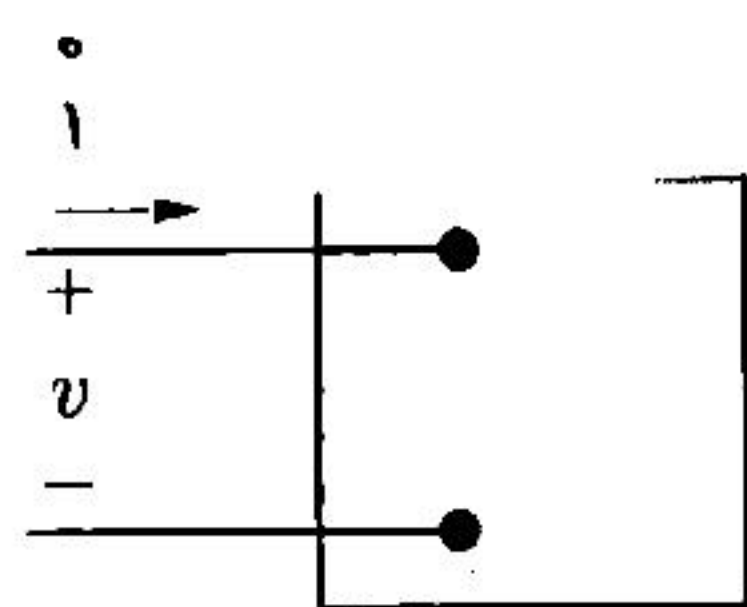

$$p = v \cdot i$$

The black box representation of a circuit used for calculating power.

$$v = V_m \cos(\omega t + \theta_v),$$

$$i = I_m \cos(\omega t + \theta_i),$$

$$v = V_m \cos(\omega t + \theta_v - \theta_i),$$

$$i = I_m \cos \omega t.$$

$\theta_v - \theta_i$ = phase angle between V and i

$$p = V_m I_m \cos(\omega t + \theta_v - \theta_i) \cos \omega t.$$

$$\cos \alpha \cos \beta = \frac{1}{2} \cos(\alpha - \beta) + \frac{1}{2} \cos(\alpha + \beta)$$

$$p = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(2\omega t + \theta_v - \theta_i).$$

$$\cos(\alpha + \beta) = \cos \alpha \cos \beta - \sin \alpha \sin \beta$$

$$\cos(2\omega t + \theta_v - \theta_i) = \cos 2\omega t \cos(\theta_v - \theta_i) - \sin 2\omega t \sin(\theta_v - \theta_i)$$

$$p = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \cos 2\omega t - \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \sin 2\omega t.$$

10.2 ♦ Average and Reactive Power

$$p = P + P \cos 2\omega t - Q \sin 2\omega t,$$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i),$$

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i).$$

P is called the **average power**, and Q is called the **reactive power**

The two loads in the circuit shown in Fig. 10.14 can be described as follows: Load 1 absorbs an average power of 8 kW at a leading power factor of 0.8. Load 2 absorbs 20 kVA at a lagging power factor of 0.6.

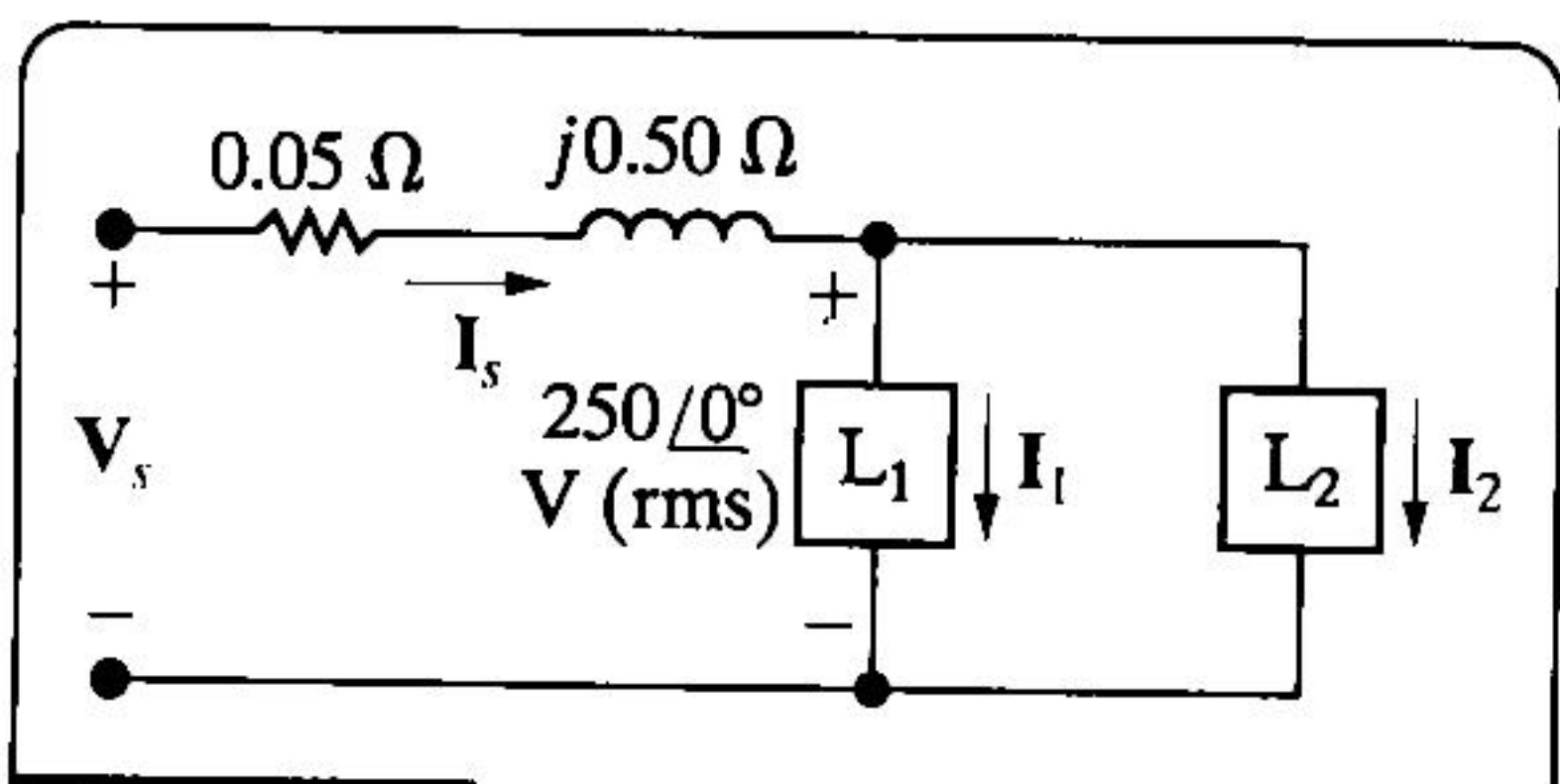


Figure 10.14 The circuit for Example 10.6.

- Determine the power factor of the two loads in parallel.
- Determine the apparent power required to supply the loads, the magnitude of the current, I_s , and the average power loss in the transmission line.
- Given that the frequency of the source is 60 Hz, compute the value of the capacitor that would correct the power factor to 1 if placed in parallel with the two loads. Recompute the values in (b) for the load with the corrected power factor.

SOLUTION


- All voltage and current phasors in this problem are assumed to represent effective values.

$$S = \frac{1}{2} \underline{V} \underline{I}^* = \underline{V}_{eff} \underline{I}_{eff}^*$$

Load 1

average power $P = 8 \text{ kW}$
 $= 8000 \text{ W}$


leading power factor 0.8

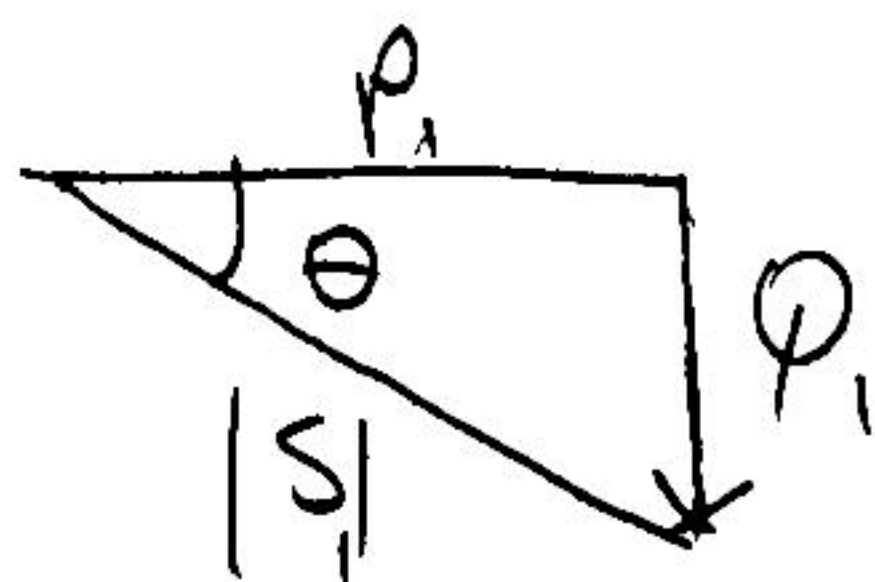

$$\cos \theta = 0.8$$


Q is minus

NOTE:

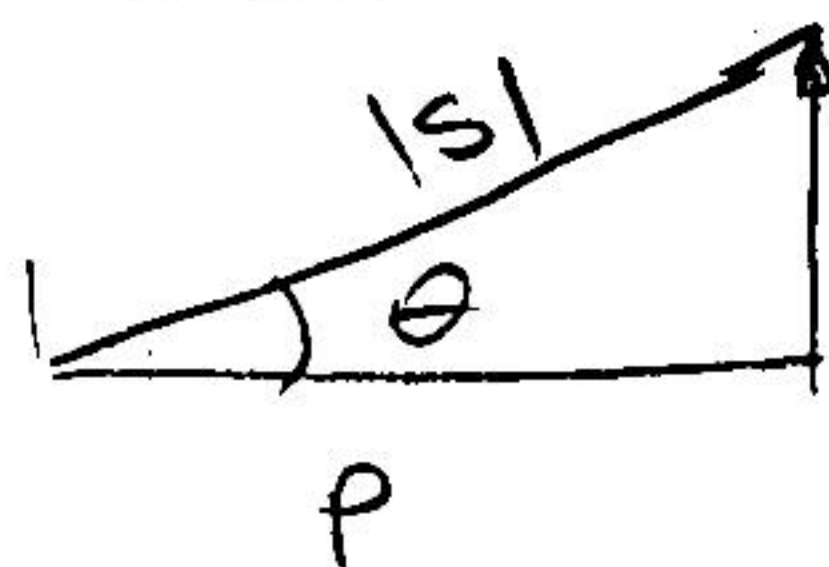

lagging power factor

$$\theta > 0 \quad \varphi > 0$$

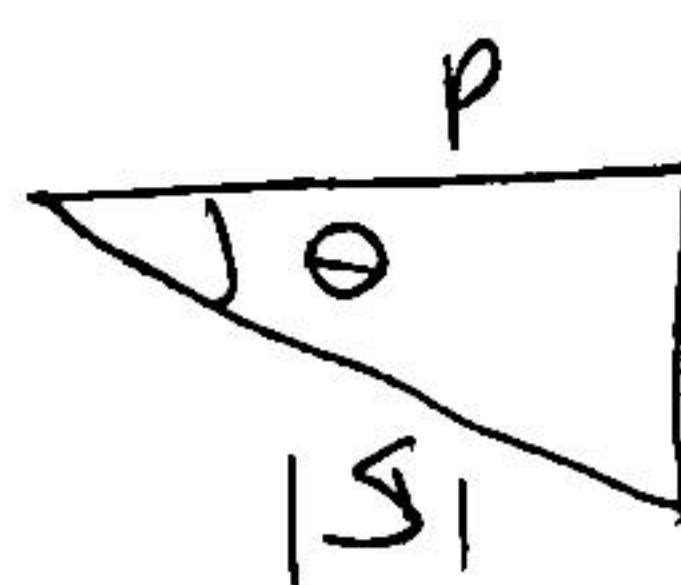

leading power factor

$$\theta < 0 \quad \varphi < 0$$

$$\cos \theta = 0.8 \Rightarrow \theta = 36.8$$

$$\text{But } \theta < 0 \Rightarrow \theta = -36.8$$

$$\frac{Q_1}{P_1} = \tan \theta = \tan(-36.8)$$

$$= -0.75$$

$$\frac{Q_1}{8000} = -0.75$$


$$Q_1 = 8000 \times (-0.75) = -6000$$

$$S_1 = P_1 + jQ_1 = 8000 - j6000$$

load 2

absorbs 20 kVA $\Rightarrow |S| = 20000$

lagging power factor 0.6

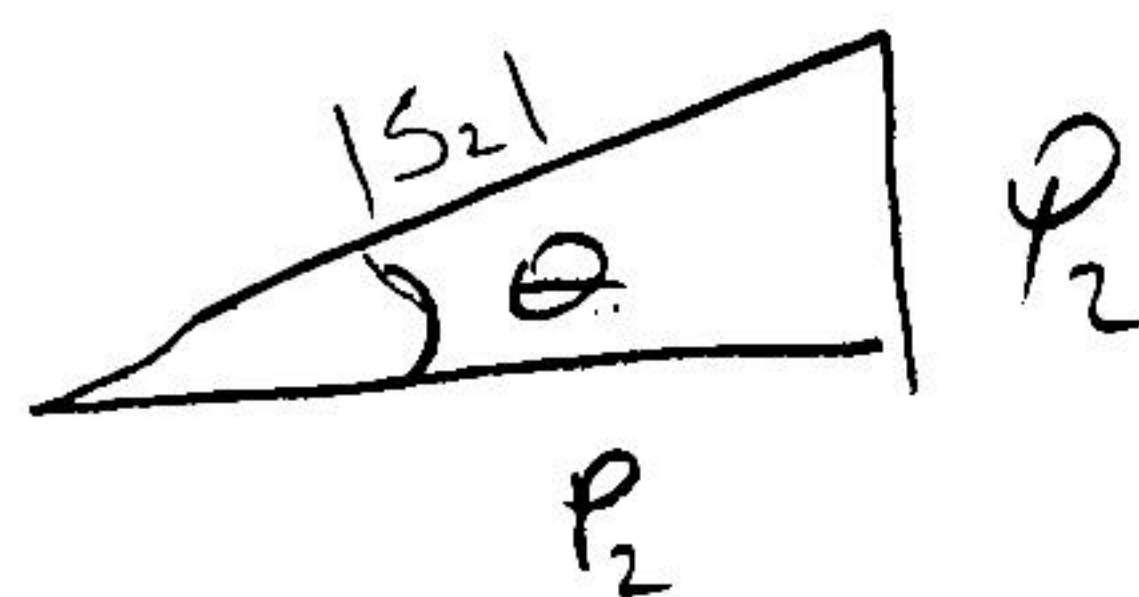

$$\cos \theta = 0.6 \Rightarrow \theta = 53.1 \Rightarrow$$

$$\sin \theta = 0.8$$

$$\cos \theta = \frac{P_2}{|S_2|}$$

$$0.8 = \frac{P_2}{20000} \Rightarrow P_2 = 12000$$

$$\sin \theta = \frac{Q_2}{|S_2|}$$


$$0.8 = \frac{Q_2}{20000} \Rightarrow Q_2 = 16000$$

$$S_2 = P_2 + Q_2 j = 12000 + j16000$$

$$S_1 = 8000 - j6000$$

$$S_{12} = S_1 + S_2 = 20000 + j10000$$

$$= P_{12} + jQ_{12}$$

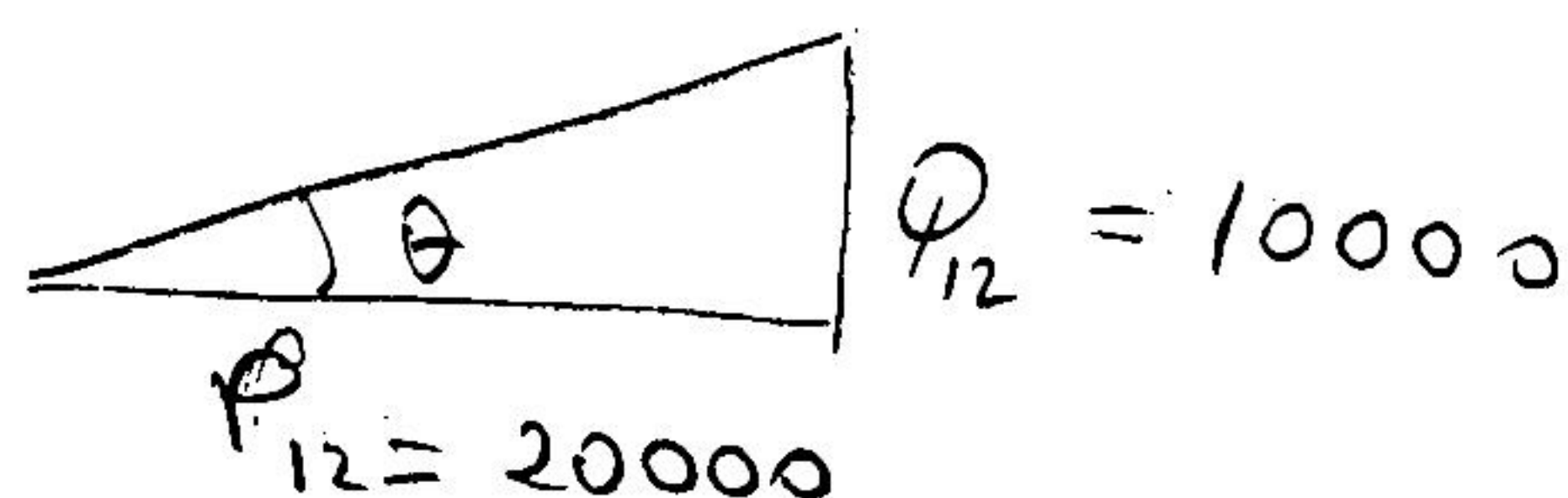

$$\tan \theta = \frac{Q_{12}}{P_{12}} = \frac{10000}{20000} = \frac{1}{2}$$


$$\theta = 26.56 \Rightarrow \cos \theta = 0.894$$

Since θ is positive

power factor is lagging

EP11

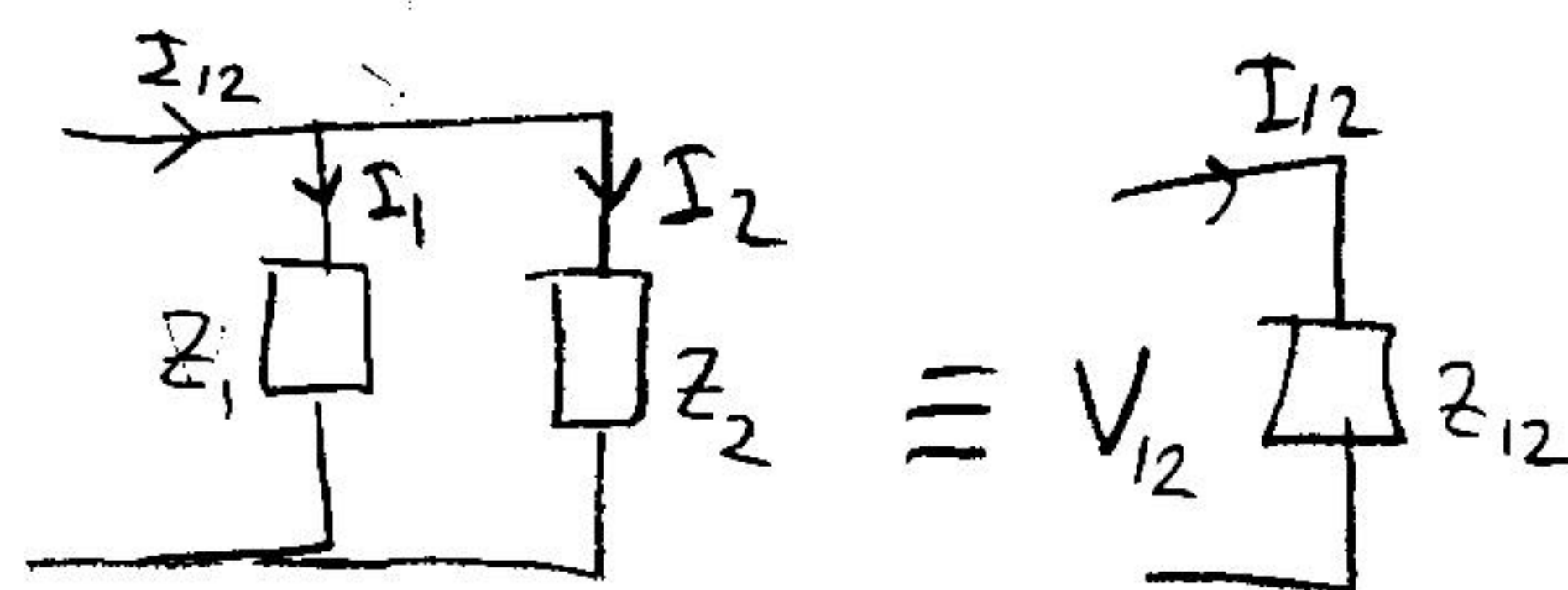b) The apparent power which must be supplied to these loads is



$$S_{12} = 20000 + j10000$$

$$|S_{12}| = \sqrt{20000^2 + 10000^2}$$

$$= 22360 \text{ (apparent power)}$$

$$V_{12} = 250 \angle 0^\circ = 250 + j0$$


given in the figure

$$S_{12} = V_{12} I_{12}^*$$

$$I_{12}^* = \frac{S_{12}}{V_{12}} = \frac{20000 + j10000}{250}$$

$$I_{12}^* = 80 + j40$$

$$I_{12} = 80 - j40$$

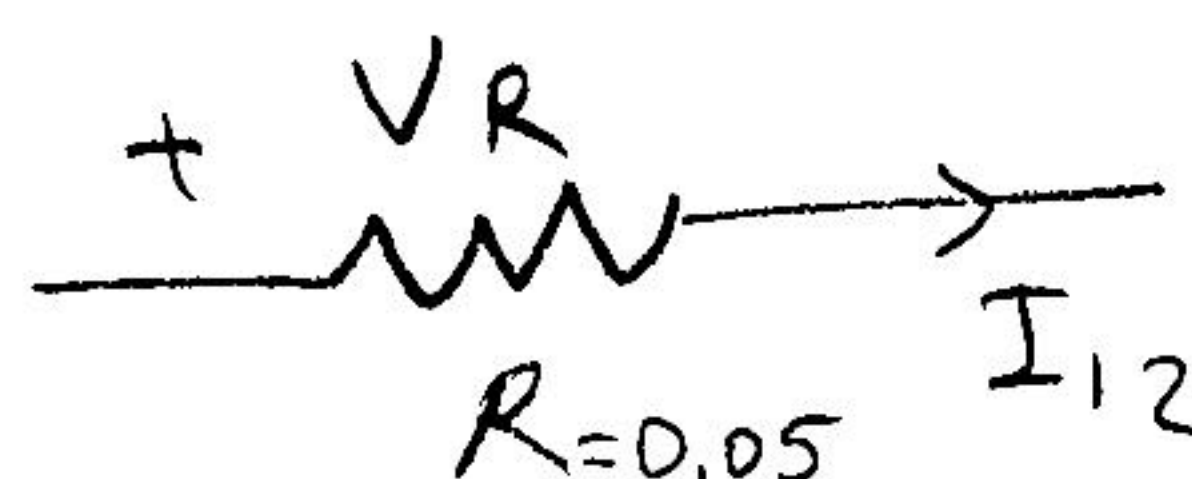

$$V_R = R I_{12}$$

$$P_R = V_R I_{12}^*$$


Note: $P = \frac{1}{2} V_m I_m^* = V_{eff} I_{eff}^*$

$$P_r = V_R I_{12}^*$$

$$= (R I_{12}) I_{12}^*$$


$$= R (80 - j40) (80 + j40)$$

$$= 0.05 (80^2 + 40^2) = 400 \text{ W}$$

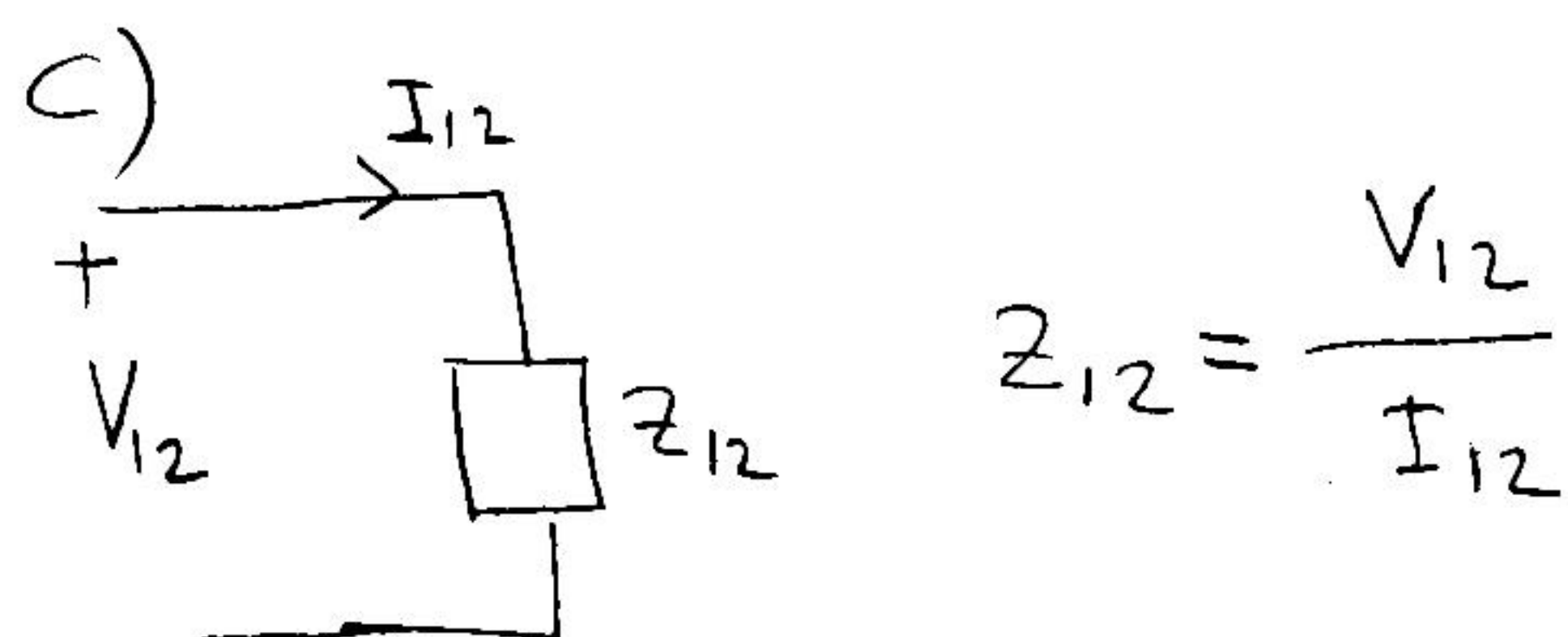

$$Z_{12} = \frac{250}{80 - j40} = \frac{250(80 + j40)}{80^2 + 40^2}$$

$$Z_{12} = 2.5 + j1.25 = a + jb$$

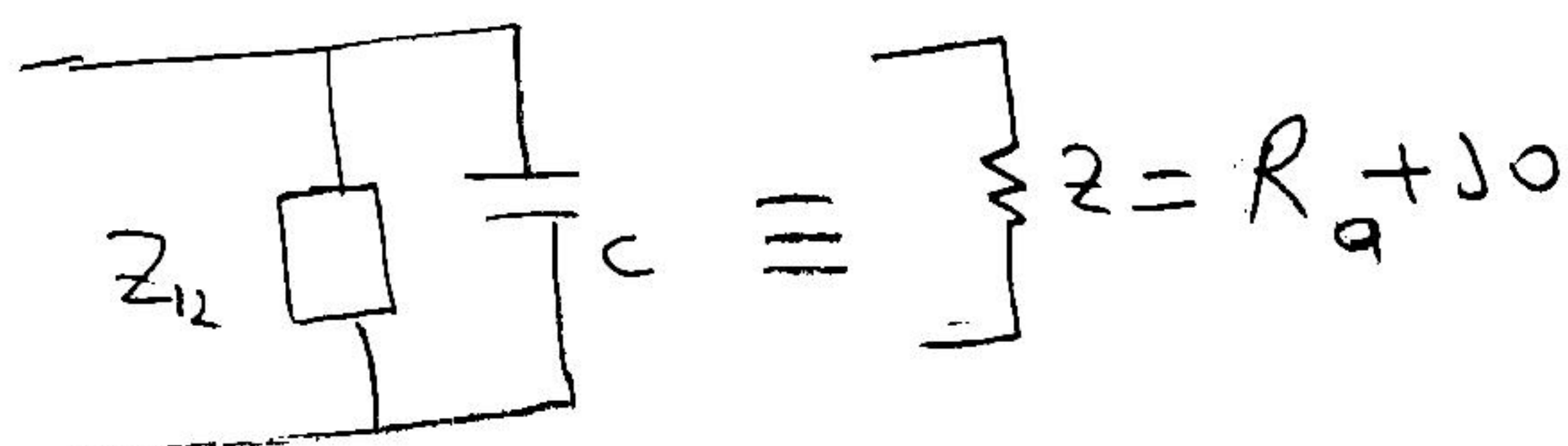

$$Z_{12} = a + bj \quad Z_C = \frac{1}{j\omega C}$$

$$\frac{1}{Z_{12}} + \frac{1}{Z_C} = \frac{1}{R_a} + j0$$

$$\frac{1}{a + bj} + \frac{1}{\frac{1}{j\omega C}} = \frac{1}{R_a} + j0$$

$$\frac{a - bj}{a^2 + b^2} + j\omega C = \frac{1}{R_a} + j0$$

o

EP 12

$$\frac{a}{a^2 + b^2} - j \frac{b}{a^2 + b^2} + j\omega C = \frac{1}{R_a} + j0$$

$$\frac{a}{a^2 + b^2} + j \left(\omega C - \frac{b}{a^2 + b^2} \right) = \frac{1}{R_a} + j0$$


$$\omega C - \frac{b}{a^2 + b^2} = 0$$

$$\omega C = \frac{b}{a^2 + b^2}$$

$$C = \frac{b}{\omega(a^2 + b^2)} = \frac{1.25}{2\pi \times 60 (2.5^2 + 1.25^2)}$$

$$C = 4.246 \times 10^{-4} \text{ F}$$
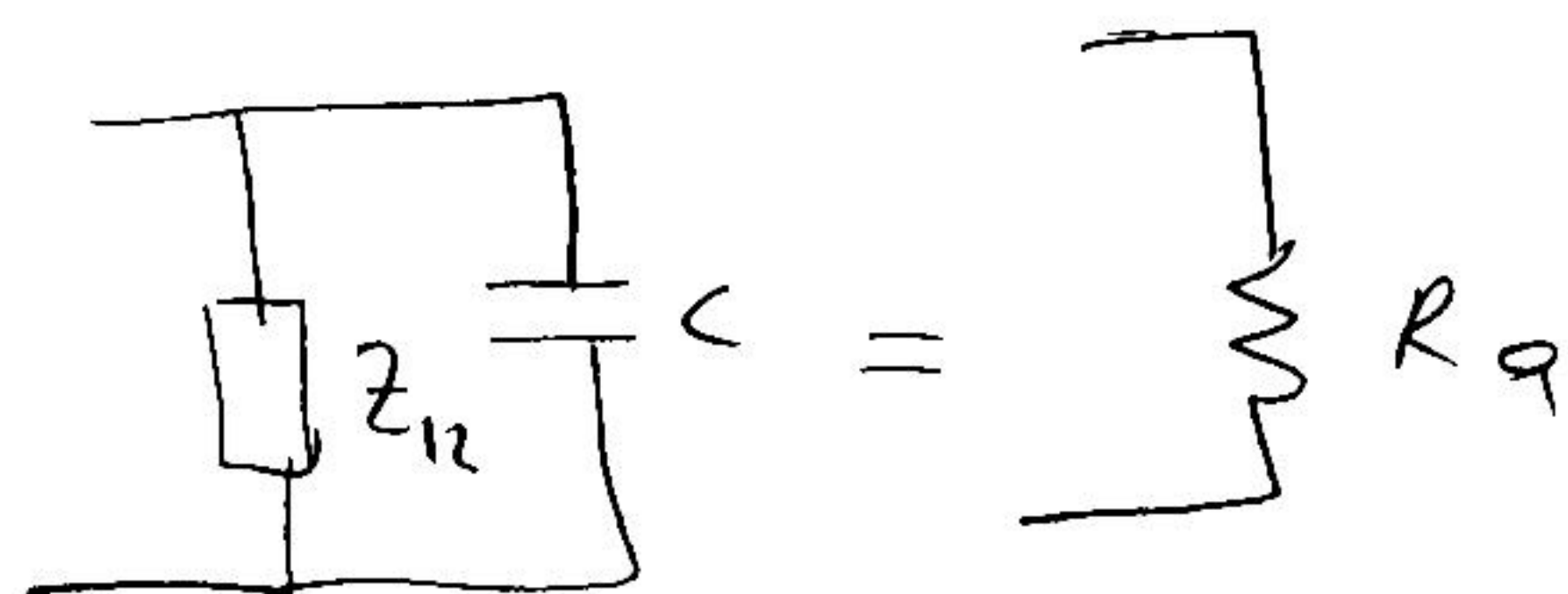
$$= 424 \times 10^{-6} \text{ F} = 424 \text{ pF}$$



$$\frac{1}{Z_{12}} + \frac{1}{\frac{1}{j\omega c}} = \frac{1}{R_q}$$


$$\frac{1}{2.5 + j1.25} + j2\pi 60 \times 4.24 \times 10^{-6} =$$

$$\frac{2.5 - j1.25}{2.5^2 + 1.25^2} + j0.1597$$

$$0.32 - j0.16 + j0.159 =$$


$$0.32 + j0 = \frac{1}{R_q}$$

$$R_q = 3.125 \Omega$$

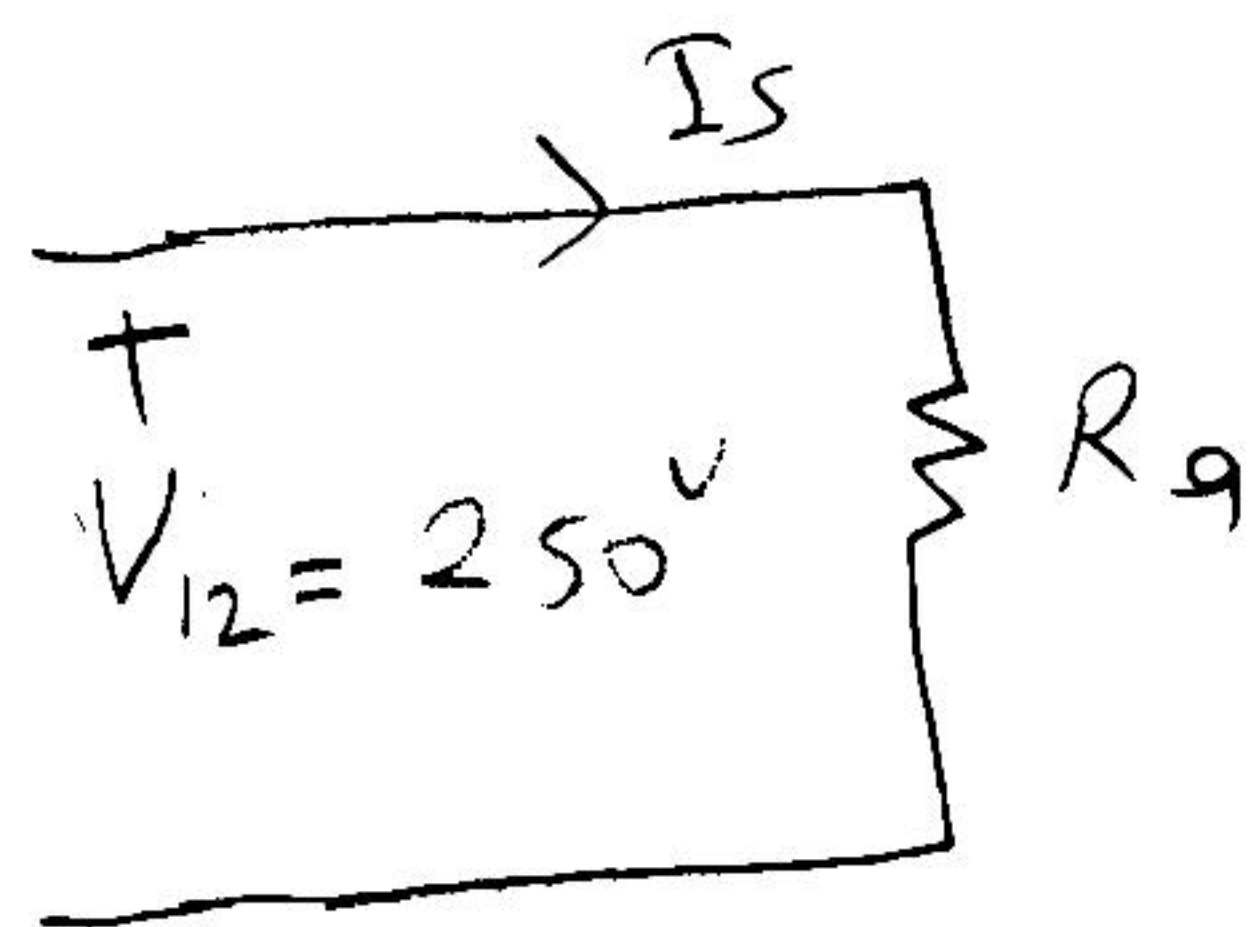


$$V_{12} = R_q I_5$$
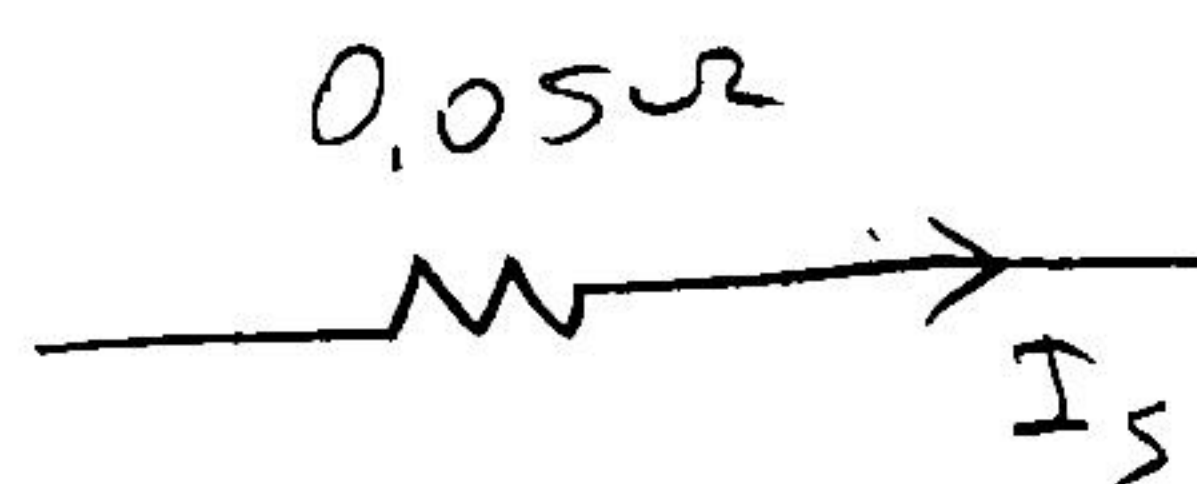
$$I_5 = \frac{V_{12}}{R_q} = \frac{250}{3.125} = 80 A$$




$$P = R I_5^2 = 0.05 \times 80^2 = 320 \text{ watt}$$

Note:





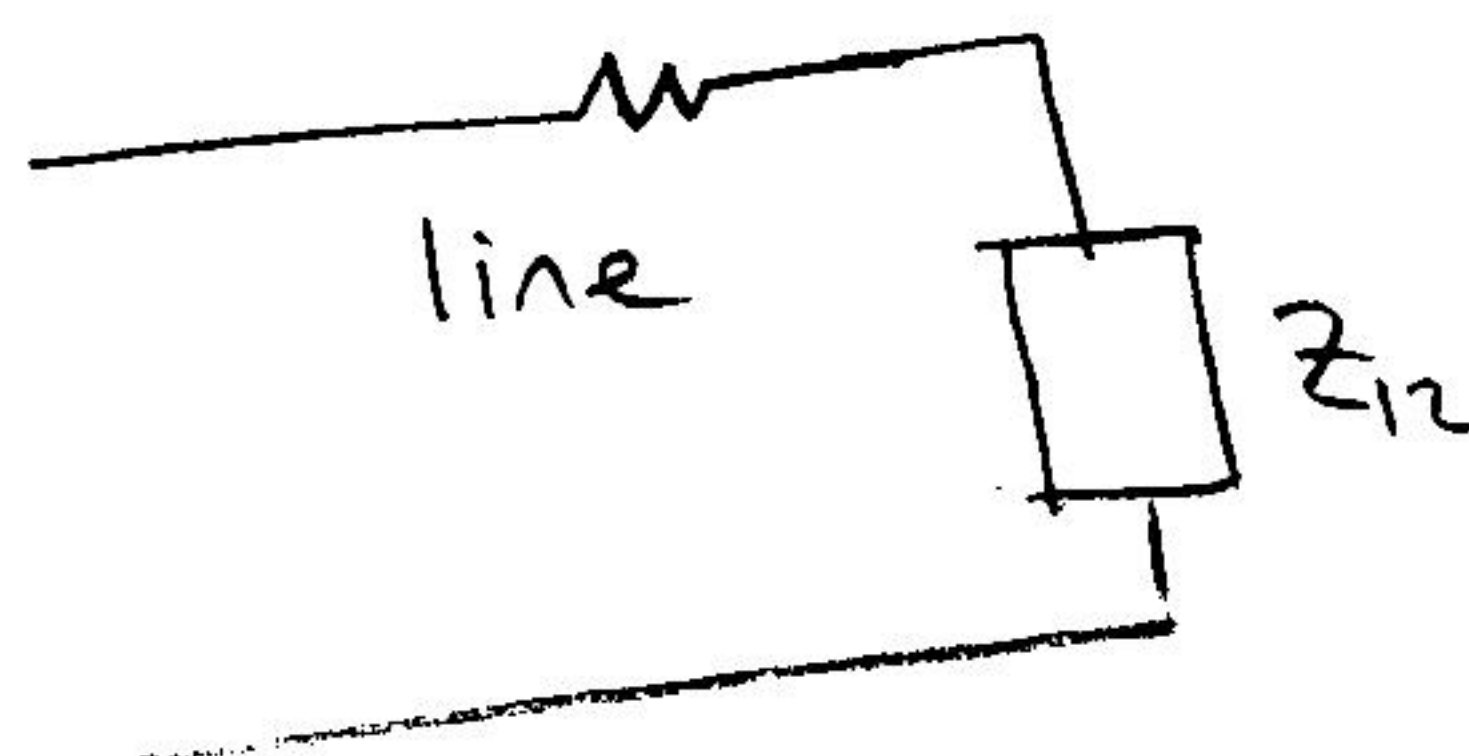


$$P_{\text{line}} = 400 \text{ wr}$$

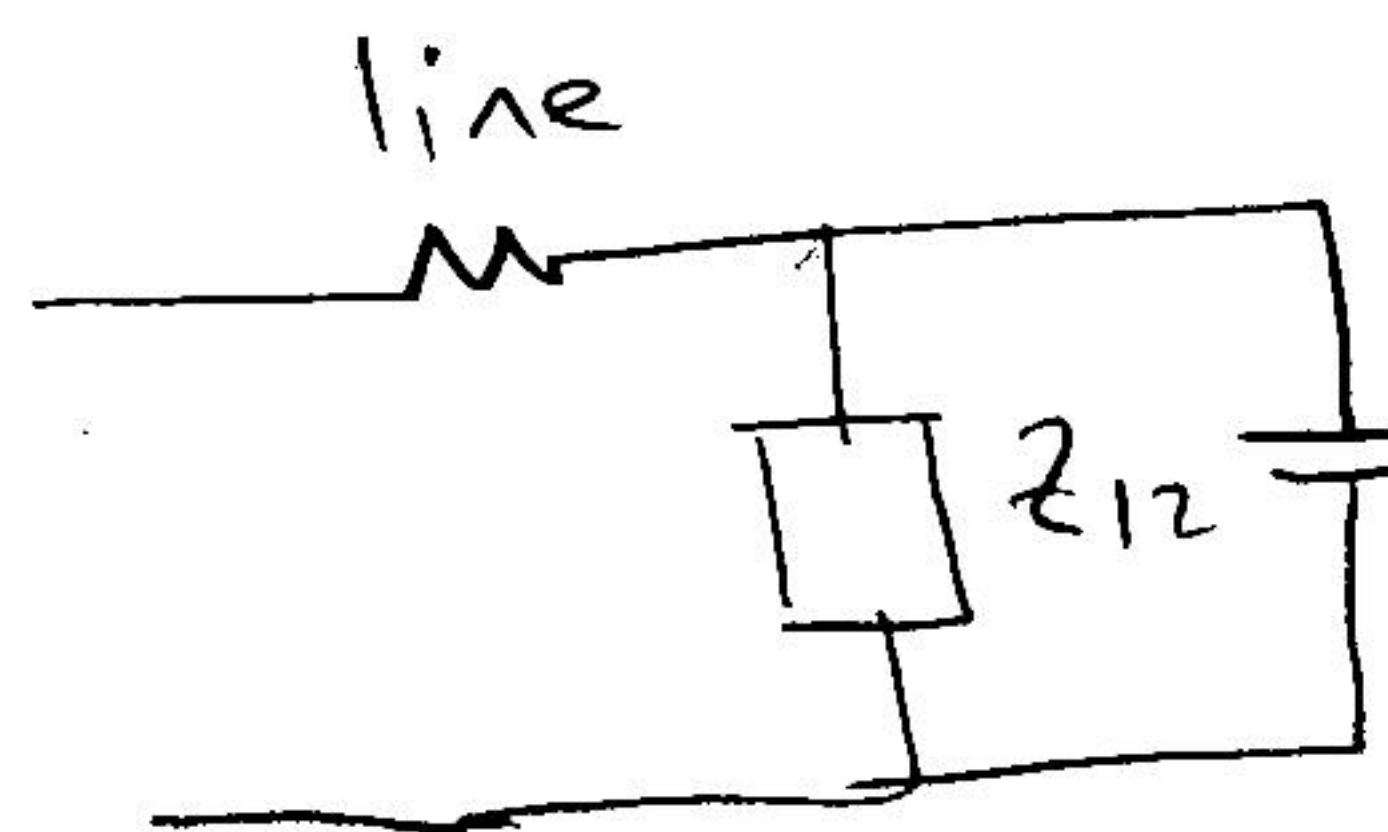


$$P_{\text{line}} = 320 \text{ wr}$$

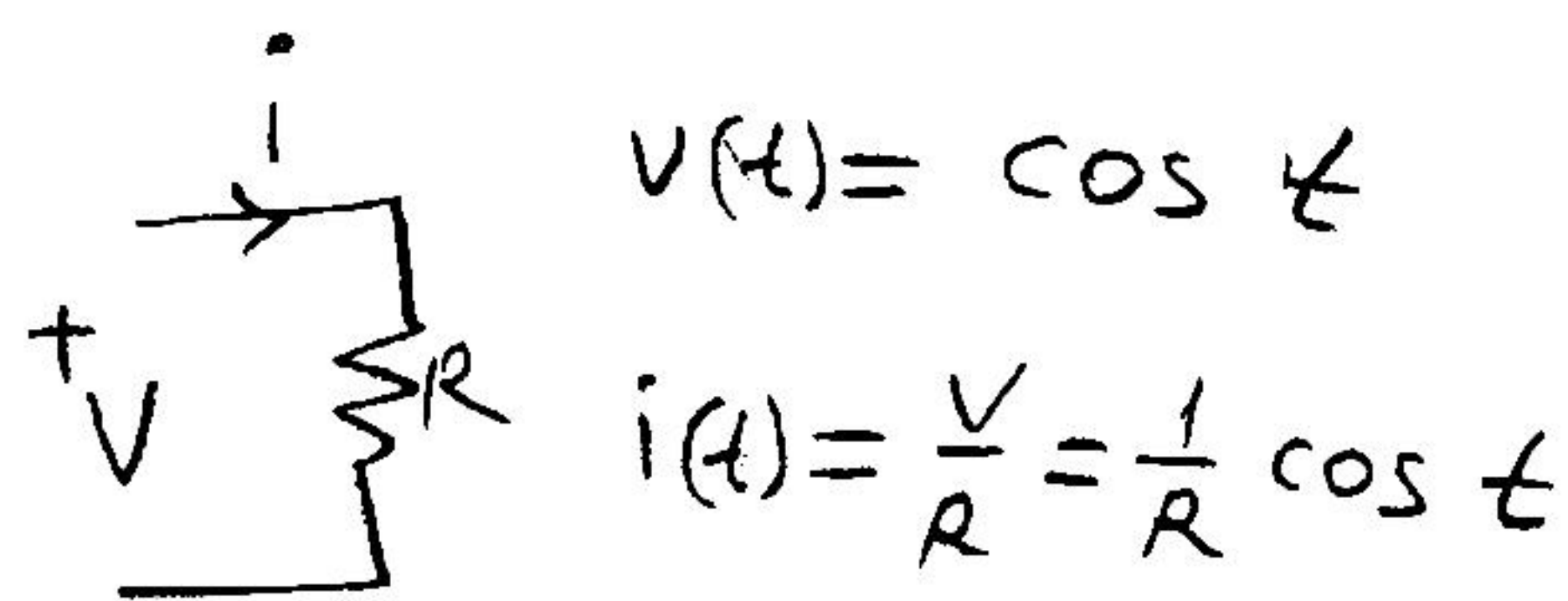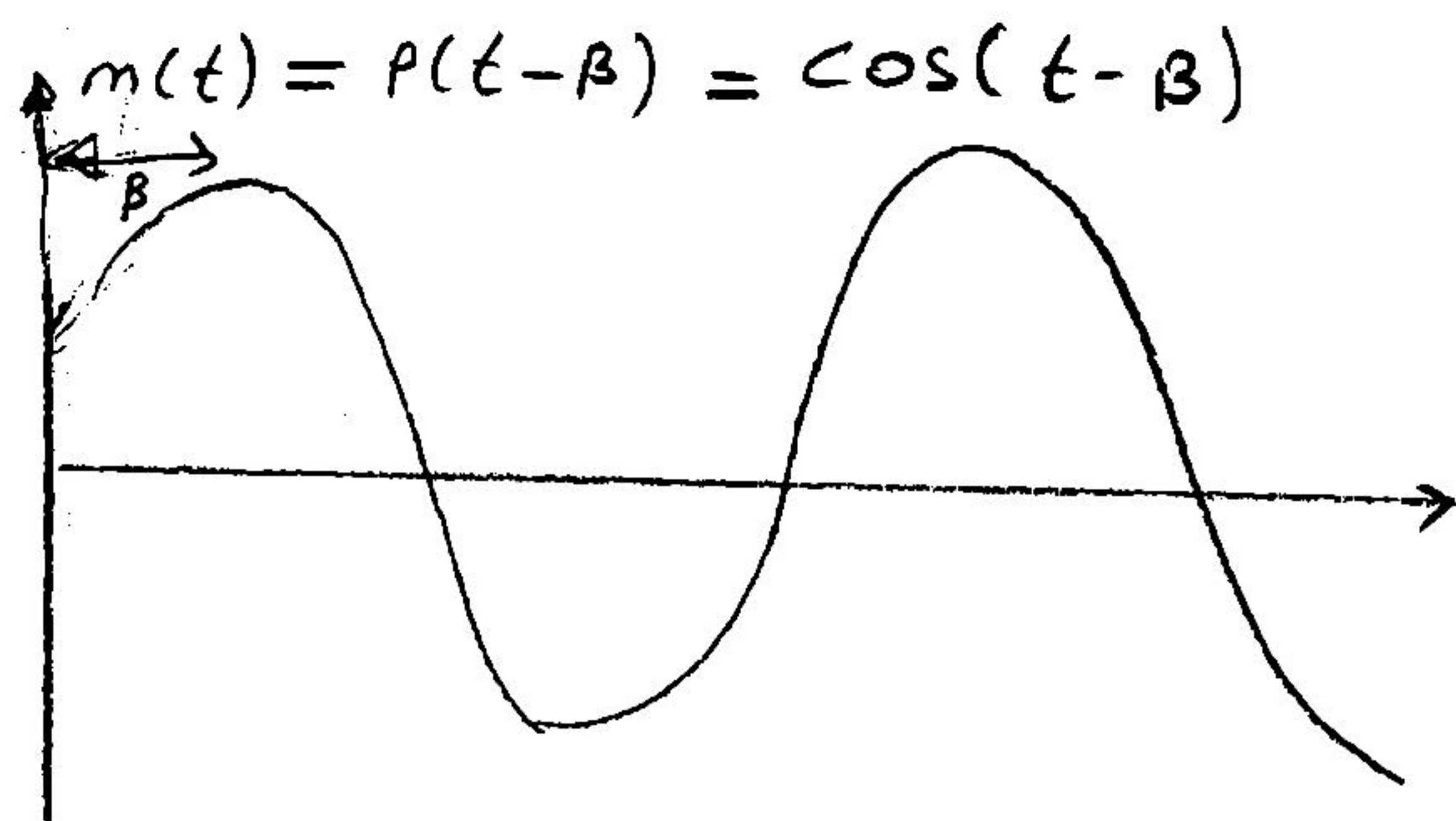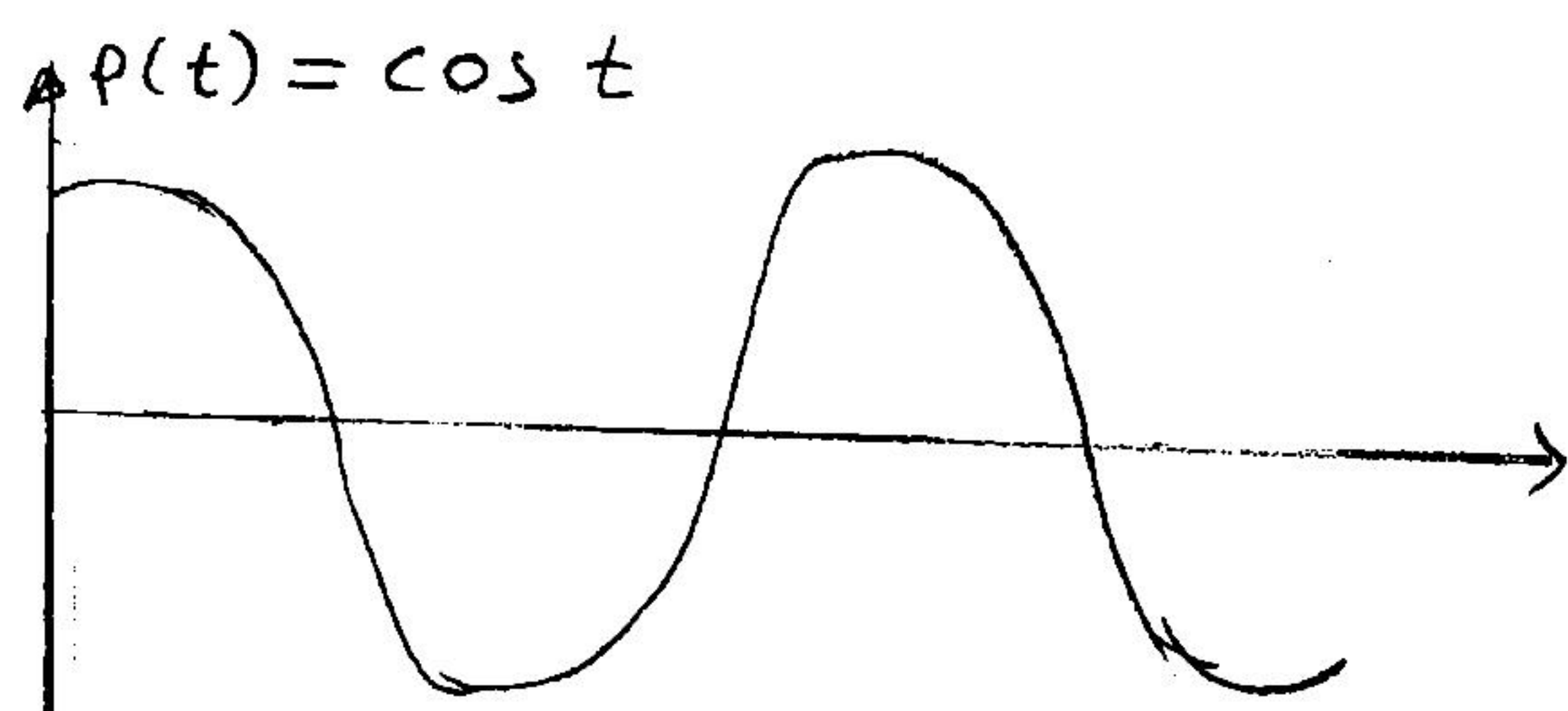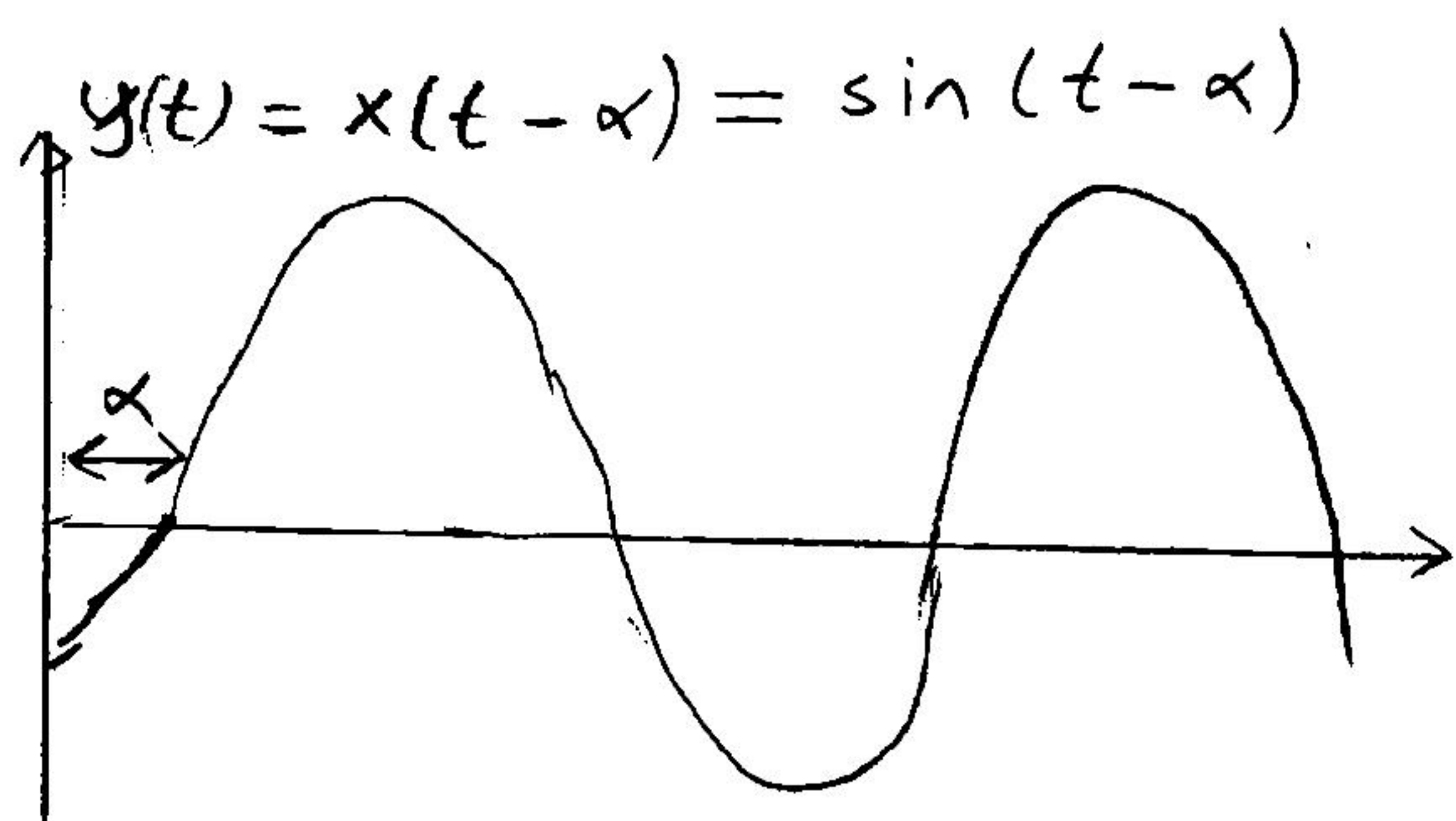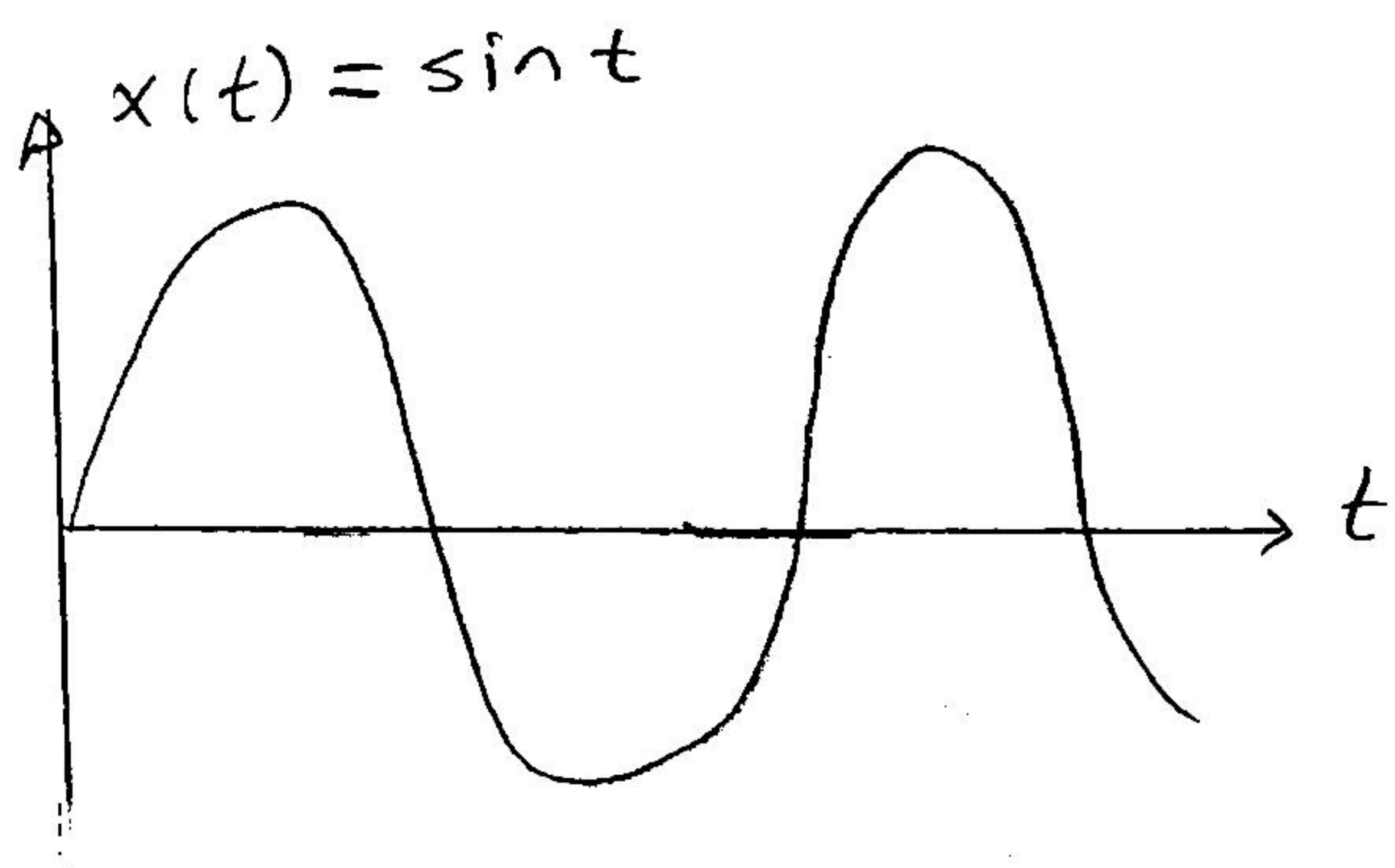line power is reduced
when capacitor is
connected.



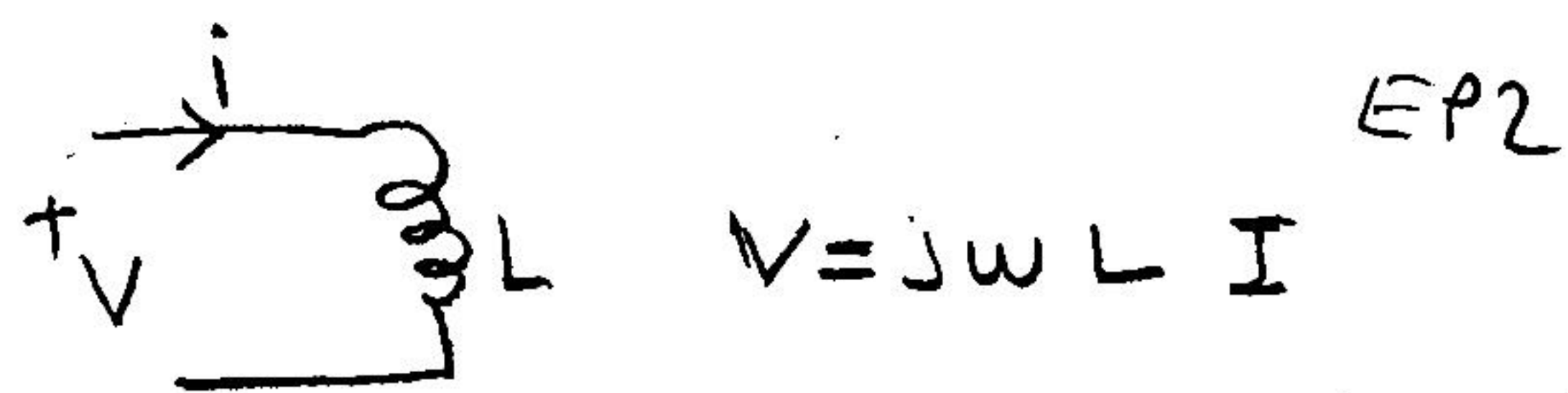
phase difference between $v(t)$ and $i(t)$ is zero



$$i(t) = \cos t$$

$$V(t) = \cos(t + 90^\circ)$$

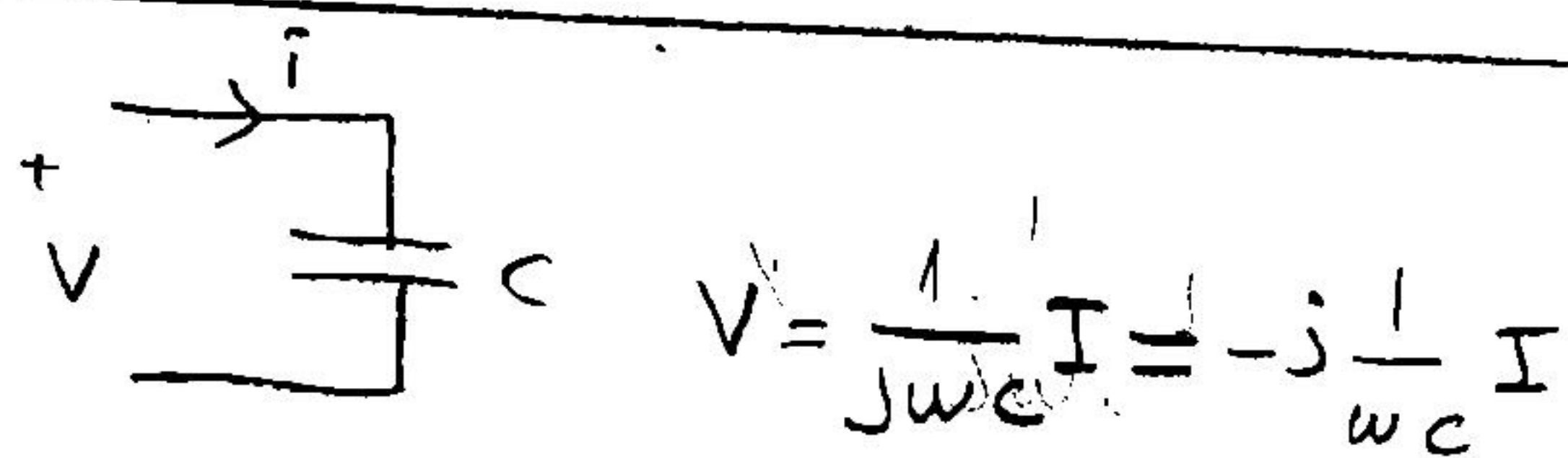In an inductor
 Voltage leads the current
 Current lags the current
 phase difference between
 voltage and current
 is 90° .




$$i(t) = \cos t$$

$$V(t) = \cos(t - 90^\circ)$$

In a capacitor
 Voltage lags the current
 Current leads the current
 phase difference between
 voltage and current $\neq$
 is -90°

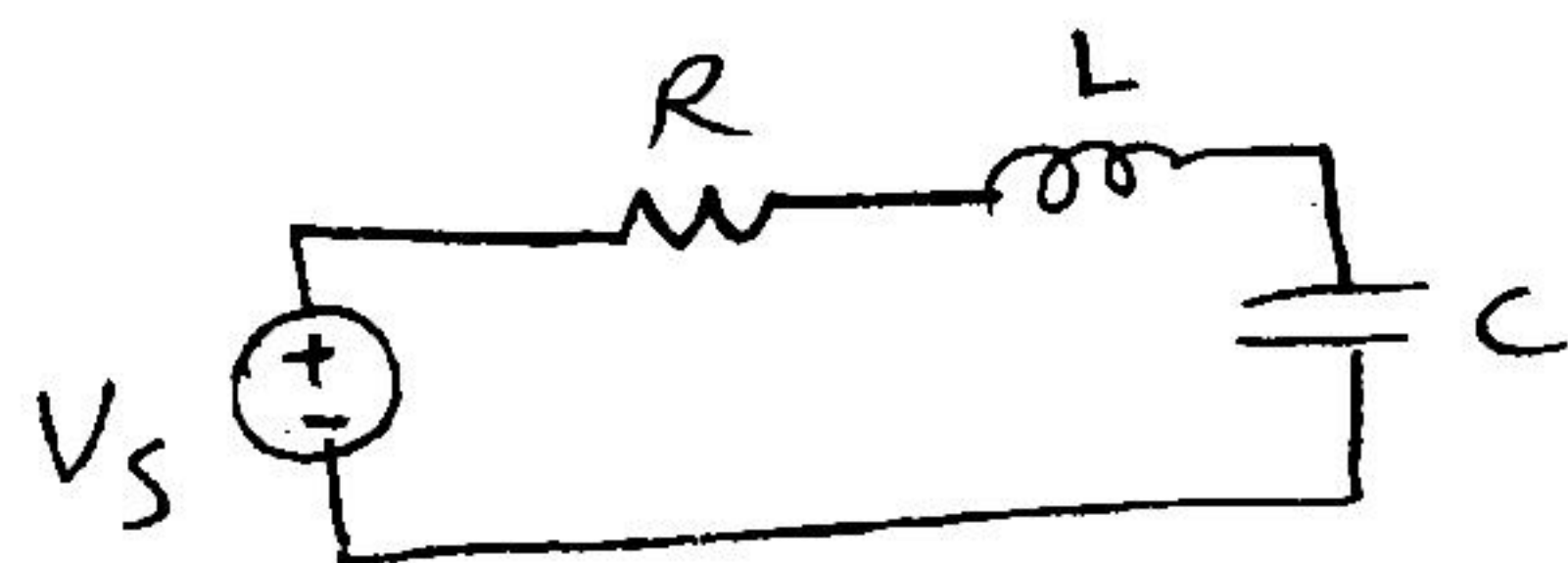Example problem: Calculate power for R, L, C elements.



$$V_s = 750 \cos(5000t + 30)$$

$$R = 90 \Omega$$

$$L = 32 \text{ mH} = 32 \times 10^{-3} \text{ H}$$


$$C = 5 \text{ } \mu\text{F} = 5 \times 10^{-6} \text{ F}$$

solution: we must solve the circuit first

$$j\omega L = j \times 5000 \times 32 \times 10^{-3} = j160 \Omega = Z_L$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j \times 5000 \times 5 \times 10^{-6}} = -j40 \Omega$$
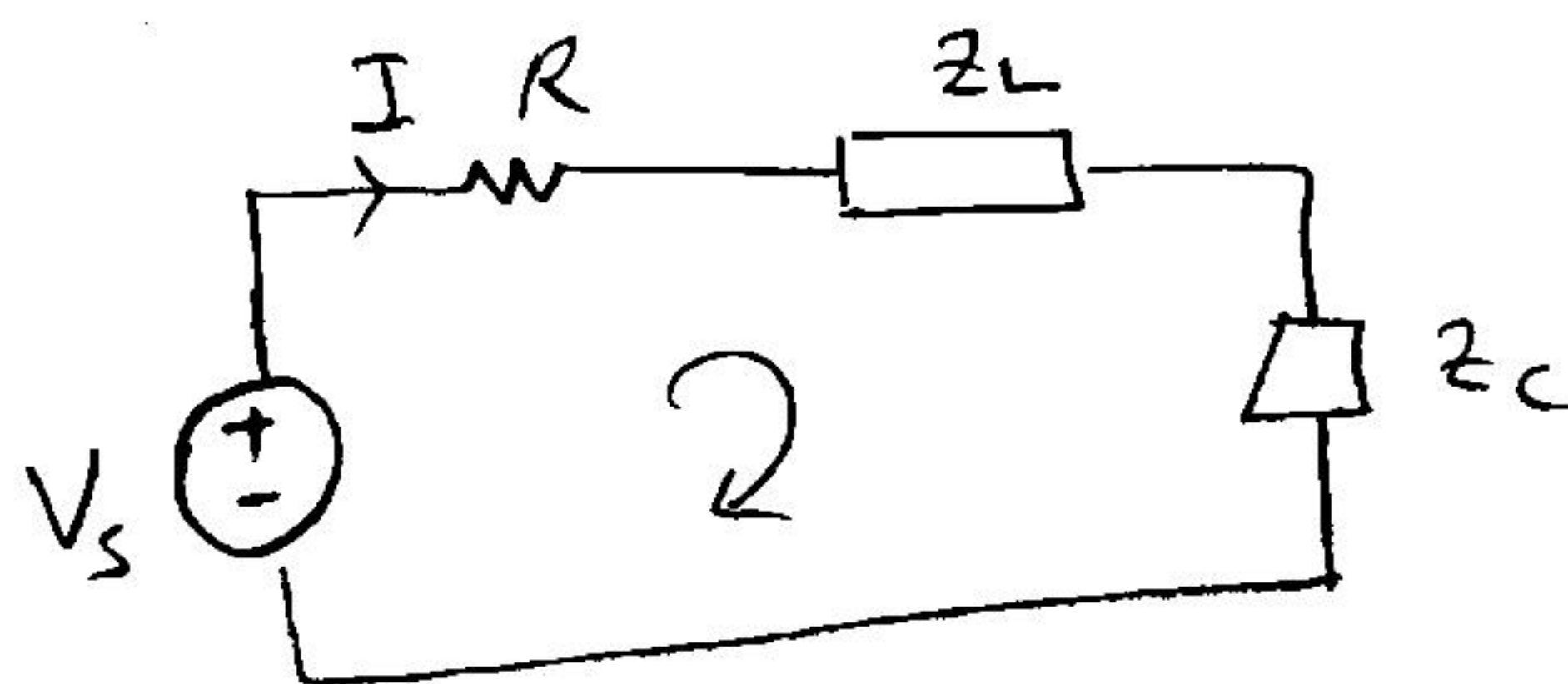
$$V_s = 750 \cos(5000t + 30) \Rightarrow \underline{V_s} = 750 \angle 30 = 750 e^{j30}$$



$$-V_s + RI + Z_L I + Z_C I = 0$$

$$I = \frac{V_s}{R + Z_L + Z_C} = \frac{750 e^{j30}}{90 + j160 - j40}$$

$$90 + j160 - j40 = 90 + j120 = \sqrt{90^2 + 120^2} e^{j\theta} = 150 e^{j\theta}$$

$$\theta = \tan^{-1} \frac{120}{90} = 53.1^\circ$$

$$I = \frac{750 e^{j30}}{150 e^{j53.1}} = \frac{750}{150} e^{j(30-53.1)} = 5 e^{-j23.1}$$

Power for R . $P_R = \frac{1}{2} V_R I_R^*$

$$V_R = R I_R$$

$$\boxed{I_R = I}$$

$$P_R = \frac{1}{2} V_R I_R^* = \frac{1}{2} R I_R I_R^* = \frac{1}{2} R |I_R|^2 = \frac{1}{2} 90 5^2 = 1125$$

Note $|a+bj| = \sqrt{a^2+b^2}$ $\angle a+bj = \tan^{-1} \frac{b}{a}$ (ep22)

$$\{a+bj\} [a+bj]^* = \{a+bj\} \{a-bj\} = a^2+b^2 = |a+bj|^2$$

$$I I^* = |I|^2$$


Power for L $P_L = \frac{1}{2} V_L I_L^*$ $V_L = Z_L I_L$

$$P_L = \frac{1}{2} V_L I_L = \frac{1}{2} Z_L I_L I_L^* = \frac{1}{2} Z_L |I_L|^2 = \frac{1}{2} j160 \text{ s}^2 = 2000j$$

Power for C $P_C = \frac{1}{2} V_C I_C^*$ $V_C = Z_C I_C$

$$P_C = \frac{1}{2} V_C I_C^* = \frac{1}{2} Z_C I_C I_C^* = \frac{1}{2} Z_C |I_C|^2 = \frac{1}{2} (-j40) \text{ s}^2 = -500j$$

Power for the voltage source

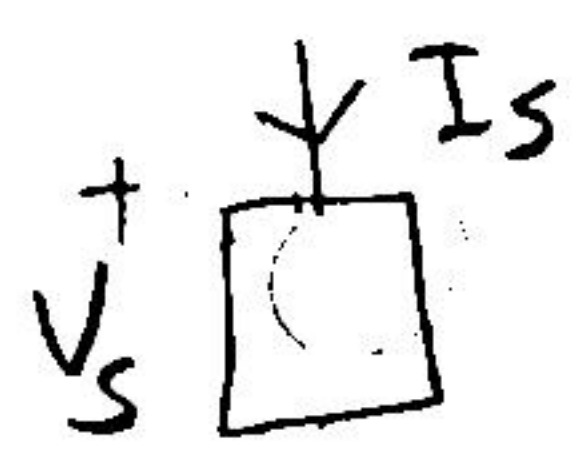

$$P = \frac{1}{2} V_s I_s^* = \frac{1}{2} V_s (-I)^* = \frac{1}{2} 750 e^{j30} (-5 e^{-j23.1})^*$$

$$= \frac{1}{2} 750 e^{j30} (-5 e^{j23.1}) = -\frac{750 \times 5}{2} e^{j(30+23.1)}$$

$$= -1875 e^{j53.1} = -1875 [\cos 53.1 + j \sin 53.1]$$

$$= -(1125 + j1500)$$

Total power of R, L, C

$$P_R + P_L + P_C = 1125 + 2000j - 500j = 1125 + 1500j$$

Voltage source power $P_S = -1125 - j1500j$

$$\boxed{(P_R + P_L + P_C) + P_S = 0}$$

$$P_S = -(P_R + P_L + P_C)$$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

Ep 3

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$$

$$\left. \begin{array}{c} \text{Resistor} \\ \text{Symbol} \end{array} \right\} \theta_v - \theta_i = 0 \Rightarrow \begin{array}{l} \cos(\theta_v - \theta_i) = 1 \\ \sin(\theta_v - \theta_i) = 0 \end{array}$$

$$P = \frac{V_m I_m}{2}$$

$$Q = 0$$

$$\left. \begin{array}{c} \text{Inductor} \\ \text{Symbol} \end{array} \right\} \theta_v - \theta_i = 90^\circ \Rightarrow \begin{array}{l} \cos 90^\circ = 0 \\ \sin 90^\circ = 1 \end{array}$$

$$P = 0$$

$$Q = \frac{V_m I_m}{2}$$

$$\left. \begin{array}{c} \text{Capacitor} \\ \text{Symbol} \end{array} \right\} \theta_v - \theta_i = -90^\circ \Rightarrow \begin{array}{l} \cos(-90) = 0 \\ \sin(-90) = -1 \end{array}$$

$$P = 0$$

$$Q = -\frac{V_m I_m}{2}$$


EXAMPLE 10.1

- a) Calculate the average power and the reactive power at the terminals of the network shown in Fig. 10.6 if

$$v = 100 \cos(\omega t + 15^\circ) \text{ V},$$

$$i = 4 \sin(\omega t - 15^\circ) \text{ A}.$$

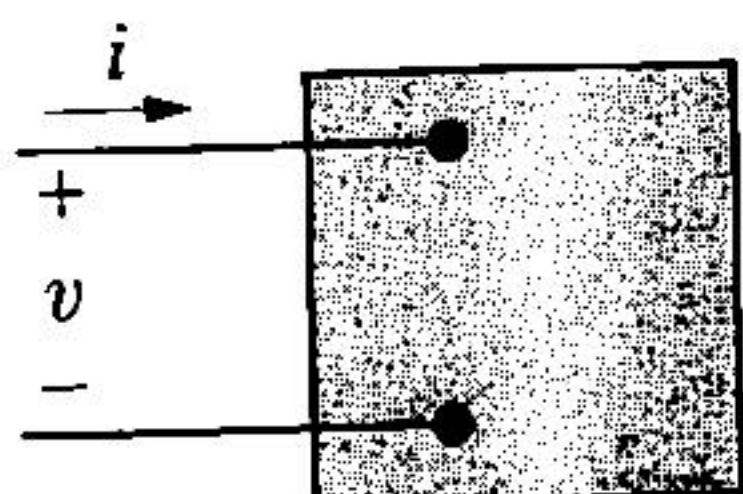- b) State whether the network inside the box is absorbing or delivering average power.
c) State whether the network inside the box is absorbing or supplying magnetizing vars.



A pair of terminals used for calculating power.

SOLUTION

$$\sin(x) = \cos(x - 90)$$

$$\sin(\omega t - 15) = \cos(\omega t - 15 - 90)$$

$$i = 4 \cos(\omega t - 105^\circ) \text{ A}.$$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$$

$$\theta_v = 15^\circ$$

$$\theta_i = -105^\circ$$


$$P = \frac{1}{2}(100)(4) \cos[15 - (-105)] = -100 \text{ W},$$

$$Q = \frac{1}{2}100(4) \sin[15 - (-105)] = 173.21 \text{ VAR}.$$

- b) Note from Fig. 10.6 the use of the passive sign convention. Because of this, the negative value of -100 W means that the network inside the box is delivering average power to the terminals.
c) The passive sign convention means that, because Q is positive, the network inside the box is absorbing magnetizing vars at its terminals.

10.3 ♦ The rms Value and Power Calculations

EP 4

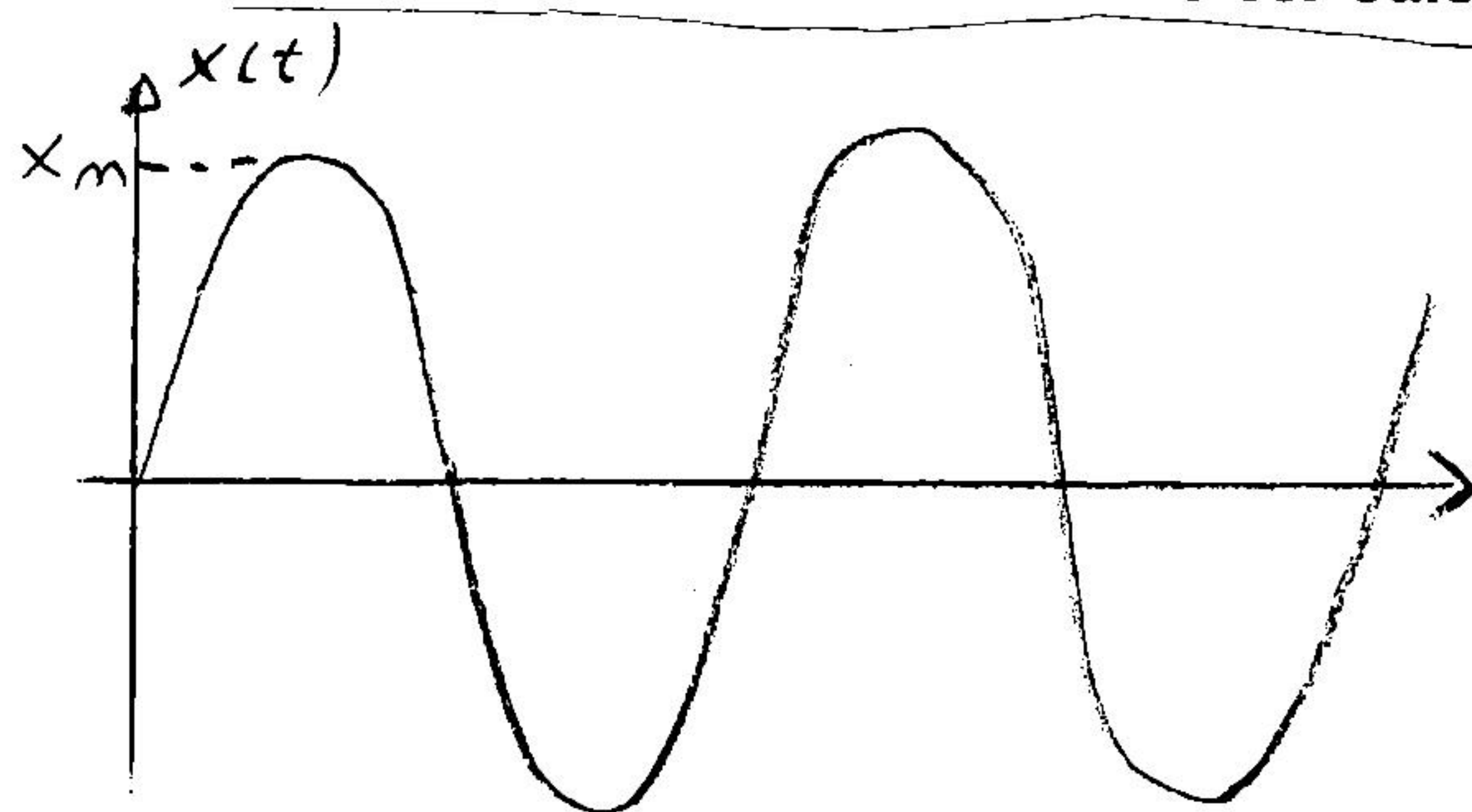

$$x(t) = x_m \cos(\omega t + \theta)$$

$x_m = \text{maximum value}$

$$x_{\text{eff}} = \frac{x_m}{\sqrt{2}} \text{ effective value}$$

$$\begin{aligned} P &= \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \\ &= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i) \\ &= V_{\text{eff}} I_{\text{eff}} \cos(\theta_v - \theta_i); \end{aligned} \quad (10.21)$$

and, by similar manipulation,

$$Q = V_{\text{eff}} I_{\text{eff}} \sin(\theta_v - \theta_i). \quad (10.22)$$

EXAMPLE 10.3

- A sinusoidal voltage having a maximum amplitude of 625 V is applied to the terminals of a 50 Ω resistor. Find the average power delivered to the resistor.
- Repeat (a) by first finding the current in the resistor.

SOLUTION

- The rms value of the sinusoidal voltage is $625/\sqrt{2}$, or approximately 441.94 V. From

$$\begin{aligned} \left. \begin{aligned} v(t) &= V_m \cos(\omega t + \alpha) \\ i(t) &= \frac{V_m}{R} \cos(\omega t + \alpha) \end{aligned} \right\} \end{aligned}$$

$$\theta_v - \theta_i = \alpha - \alpha = 0$$

$$P = \frac{V_m I_m}{2} = \frac{V_m V_m / R}{2} = \frac{625 \times 625}{2} \cdot \frac{1}{50} = 3906.25 \text{ W}$$

$$P = \frac{V_m}{\sqrt{2}} \frac{V_m}{\sqrt{2}} \frac{1}{R} =$$

$$= V_{\text{eff}} \cdot V_{\text{eff}} \frac{1}{R} = (441.94)^2 \frac{1}{50} = 3906.25 \text{ W}$$

10.4 ♦ Complex Power

EPS


$$S = P + jQ.$$

(10.23)

TABLE 10.2 Three Power Quantities and Their Units

QUANTITY	UNITS
Complex power	volt-amps
Average power	watts
Reactive power	vars

Another advantage of using complex power is the geometric interpretation it provides. When working with Eq. 10.23, think of P , Q , and $|S|$ as the sides of a right triangle, as shown in Fig. 10.9. It is easy to show that

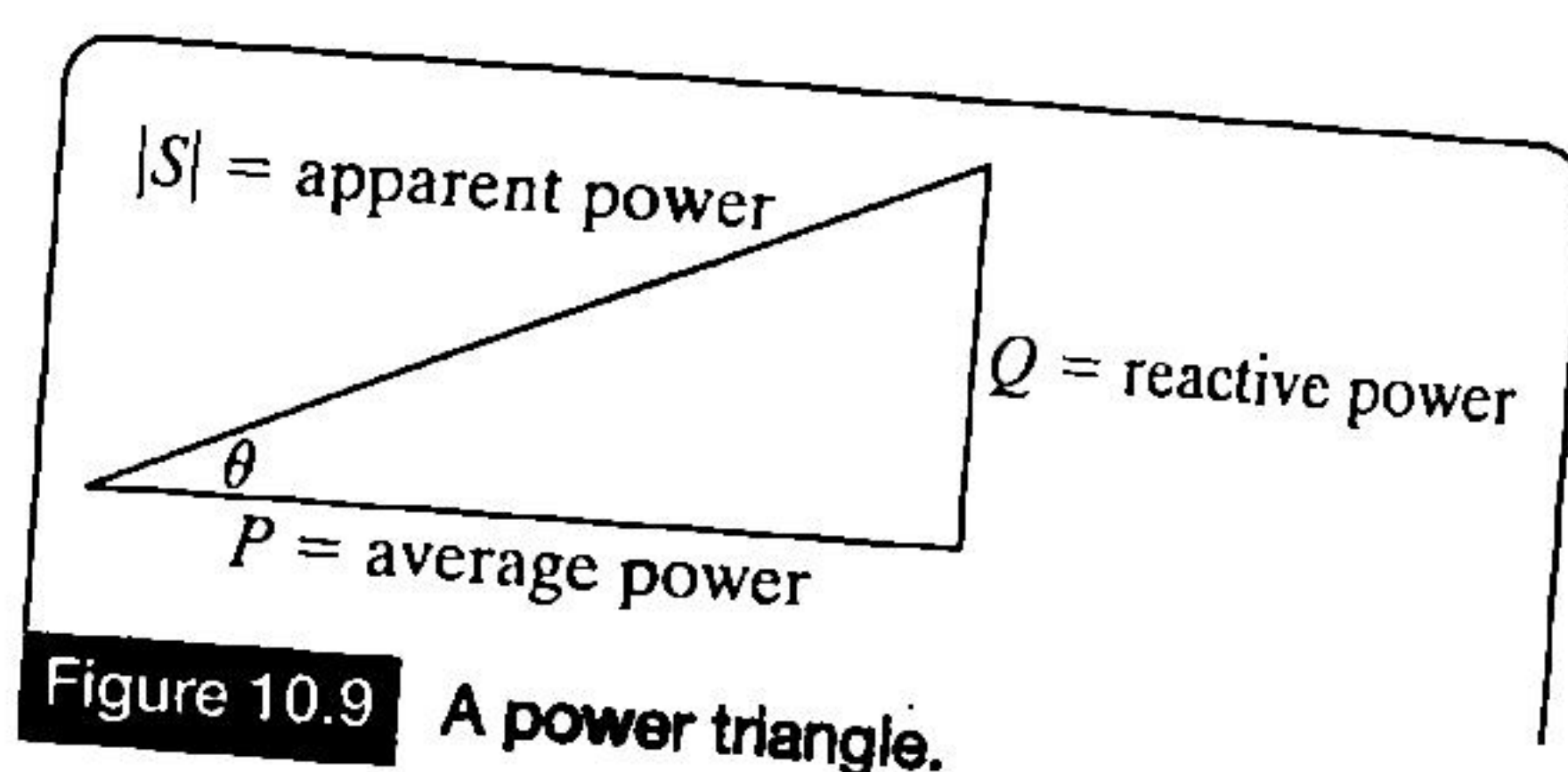

$$\cos \theta = \frac{P}{|S|}$$

$$\sin \theta = \frac{Q}{|S|}$$

$$\tan \theta = \frac{Q}{P}$$

$$\frac{Q}{P} = \frac{(V_m I_m / 2) \sin(\theta_v - \theta_i)}{(V_m I_m / 2) \cos(\theta_v - \theta_i)} = \tan(\theta_v - \theta_i).$$

The magnitude of complex power is referred to as **apparent power**. Specifically,


APPARENT POWER

$$|S| = \sqrt{P^2 + Q^2}.$$

$$\cos \theta = \text{power factor}$$

$$\text{rms value} = \text{effective value} = \frac{\text{maximum (sinusoidal)}}{\sqrt{2}}$$

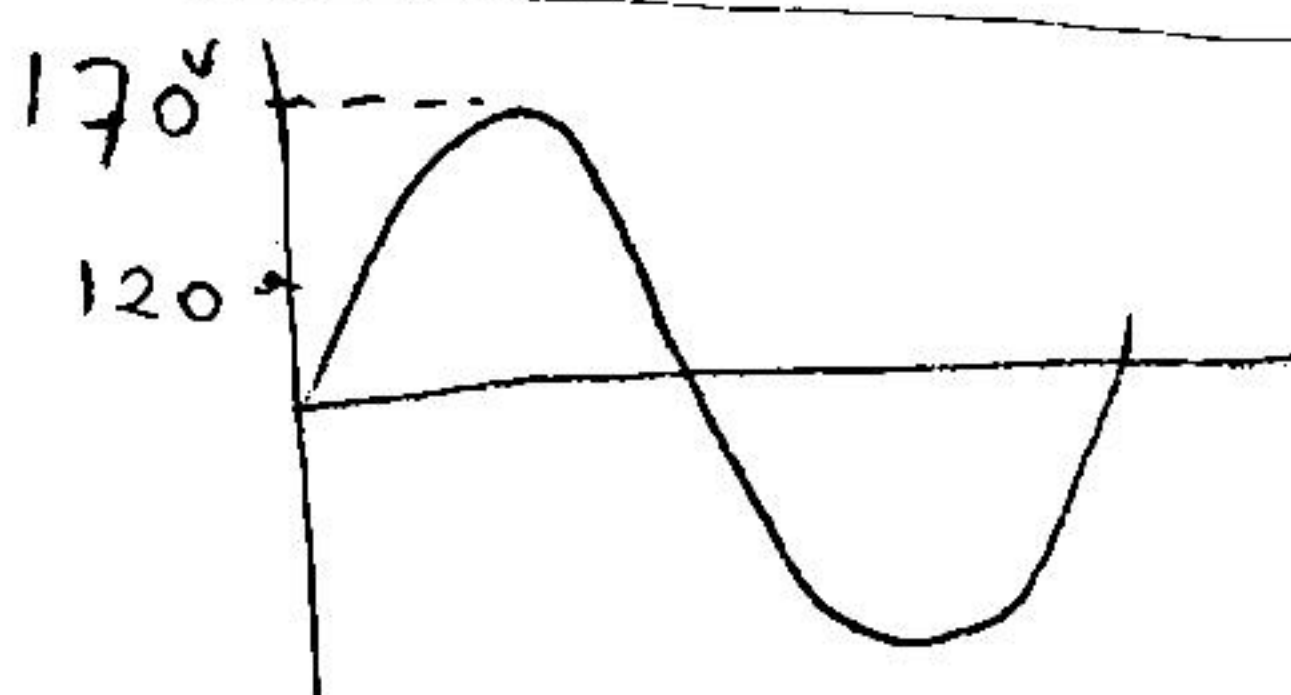Appliances such as electric lamps, irons, and toasters all carry rms ratings on their nameplates. For example, a 120 V, 100 W lamp has a resistance of $120^2/100$, or 144Ω , and draws an rms current of $120/144$, or 0.833 A . The peak value of the lamp current is $0.833\sqrt{2}$, or 1.18 A .



$$V_{\max} = 170 \text{ V}$$

$$V_{\text{rms}} = V_{\text{eff}} = 120 \text{ V}$$

EXAMPLE 10.4

EP 6

An electrical load operates at 240 V rms. The load absorbs an average power of 8 kW at a lagging power factor of 0.8.

- Calculate the complex power of the load.
- Calculate the impedance of the load.



SOLUTION

Figure 10.10 A power triangle.

$$240\text{ V rms} \Rightarrow V_{\text{eff}} = 240$$

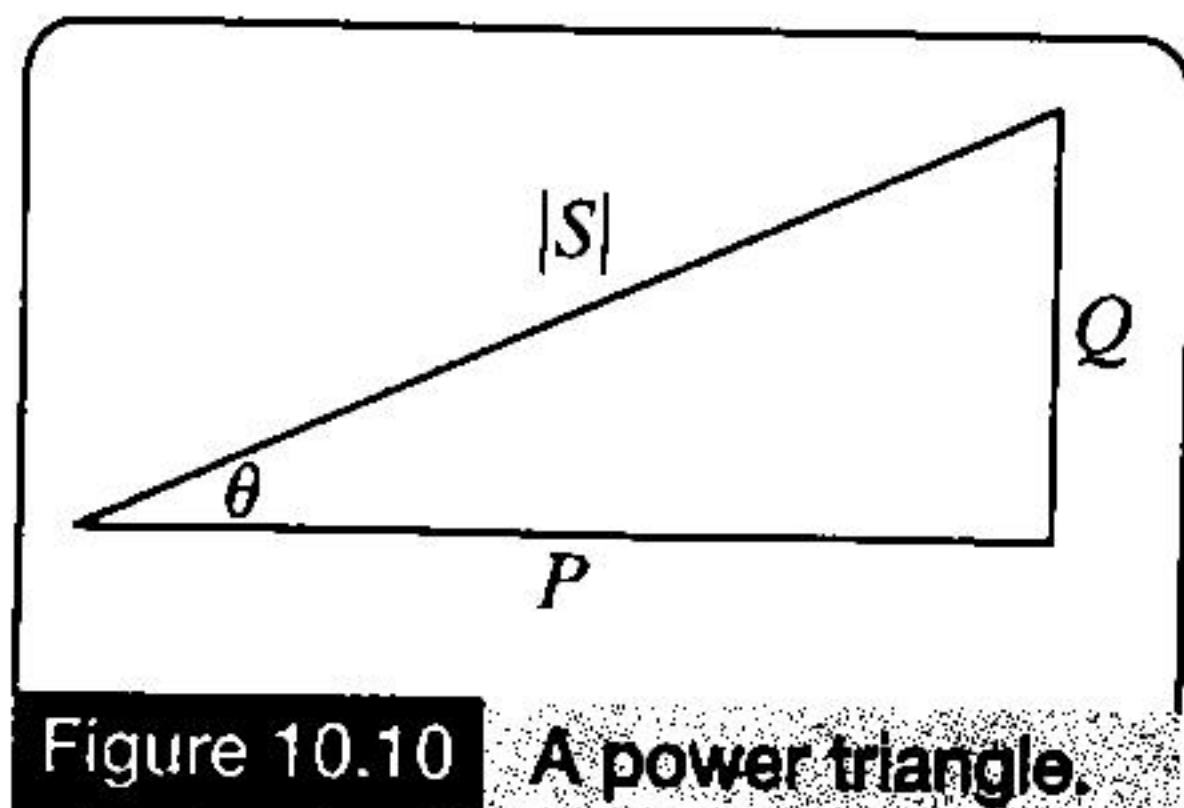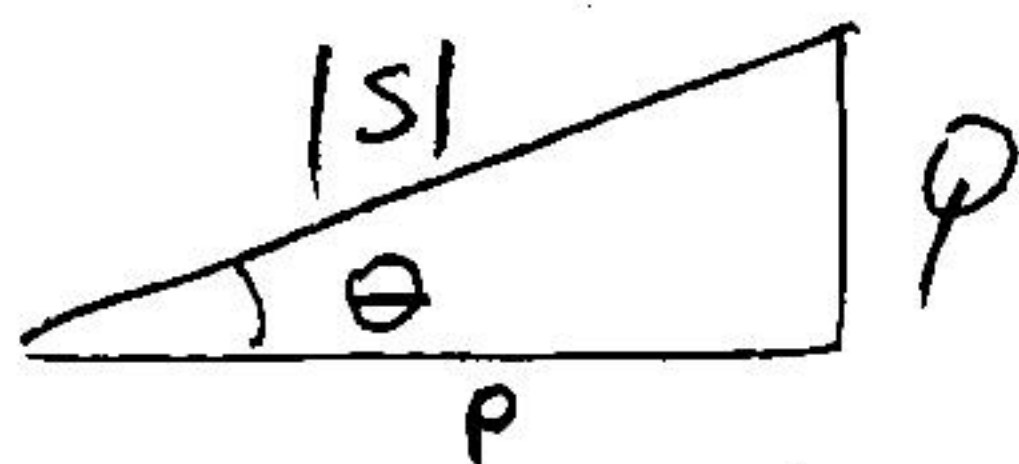Average power $P = 8\text{ kW} = 8000\text{ W}$
lagging power factor 0.8



$$\sin \theta = \sqrt{1 - \cos^2 \theta} = \sqrt{1 - 0.8^2} = 0.6$$

a)

$$P = |S| \cos \theta,$$

$$Q = |S| \sin \theta.$$

Now, because $\cos \theta = 0.8$, $\sin \theta = 0.6$. Therefore

$$|S| = \frac{P}{\cos \theta} = \frac{8\text{ kW}}{0.8} = 10\text{ kVA},$$

$$Q = 10 \sin \theta = 6\text{ kVAR},$$

and

$$S = 8 + j6\text{ kVA}.$$

- From the computation of the complex power of the load, we see that $P = 8\text{ kW}$. Using Eq. 10.21,

$$P = V_{\text{eff}} I_{\text{eff}} \cos(\theta_v - \theta_i)$$

$$= (240) I_{\text{eff}} (0.8)$$

$$= 8000\text{ W}.$$

$$I_{\text{eff}} = \frac{8000}{240 \times 0.8} = 41.67$$

$$\theta = \cos^{-1}(0.8) = 36.87^\circ.$$

$$V = Z \cdot I$$

$$|V| = |Z| |I|$$

$$\downarrow \quad \quad \downarrow$$

$$V_{\text{eff}} = |Z| \quad I_{\text{eff}}$$

$$\downarrow \quad \quad \downarrow$$

$$240 = |Z| \quad 41.67$$

$$|Z| = \frac{240}{41.67} = 5.76$$

$$Z = R + jX = |R + jX| \angle \tan^{-1} \frac{X}{R}$$

$$\downarrow$$

$$Z = 5.76 \angle 36.87^\circ$$

$$Z = 5.76 (\cos 36.87 + j \sin 36.87)$$

$$= 5.76 (0.8 + j0.6)$$

$$Z = 4.608 + j3.45$$

Power Calculations

Ep7

$$S = P + jQ$$

$$S = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + j \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$$

$$= \frac{V_m I_m}{2} [\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i)]$$

$$= \frac{V_m I_m}{2} e^{j(\theta_v - \theta_i)} = \frac{1}{2} V_m I_m \angle (\theta_v - \theta_i) = \frac{1}{2} V_m I_m e^{j(\theta_v - \theta_i)}$$

$$= \frac{1}{2} \underbrace{V_m e^{j\theta_v}}_{\underline{V}} \underbrace{I_m e^{-j\theta_i}}_{\underline{I}^*} = \frac{1}{2} \underline{V} \underline{I}^*$$

$$(a + bj)^* = a - bj$$

$$(e^{jx})^* = e^{-jx}$$

Example $V = 100 \cos(\omega t + 15^\circ)$ $I = 4 \cos(\omega t - 105^\circ)$

$$\underline{V} = 100 e^{j15^\circ}$$

$$\underline{I} = 4 e^{-j105^\circ}$$

$$\underline{I}^* = 4 e^{+j105^\circ}$$

$$S = \frac{1}{2} \underline{V} \underline{I} = \frac{1}{2} 100 e^{j15^\circ} 4 e^{-j105^\circ} = \frac{1}{2} 400 e^{-j90^\circ}$$

$$= 200 e^{-j90^\circ} = 200 [\cos 90^\circ + j \sin 90^\circ]$$

$$= 200 [-0.5 + j 0.866]$$

$$= -100 + j 173.2$$

$P = -100$ Watt (active power, average power)

$Q = 173.2$ VAR (reactive power)


$S = -100 + j 173.2$ (Complex power)

$|S| = \sqrt{100^2 + 173.2^2} = 200 \rightarrow$ apparent power

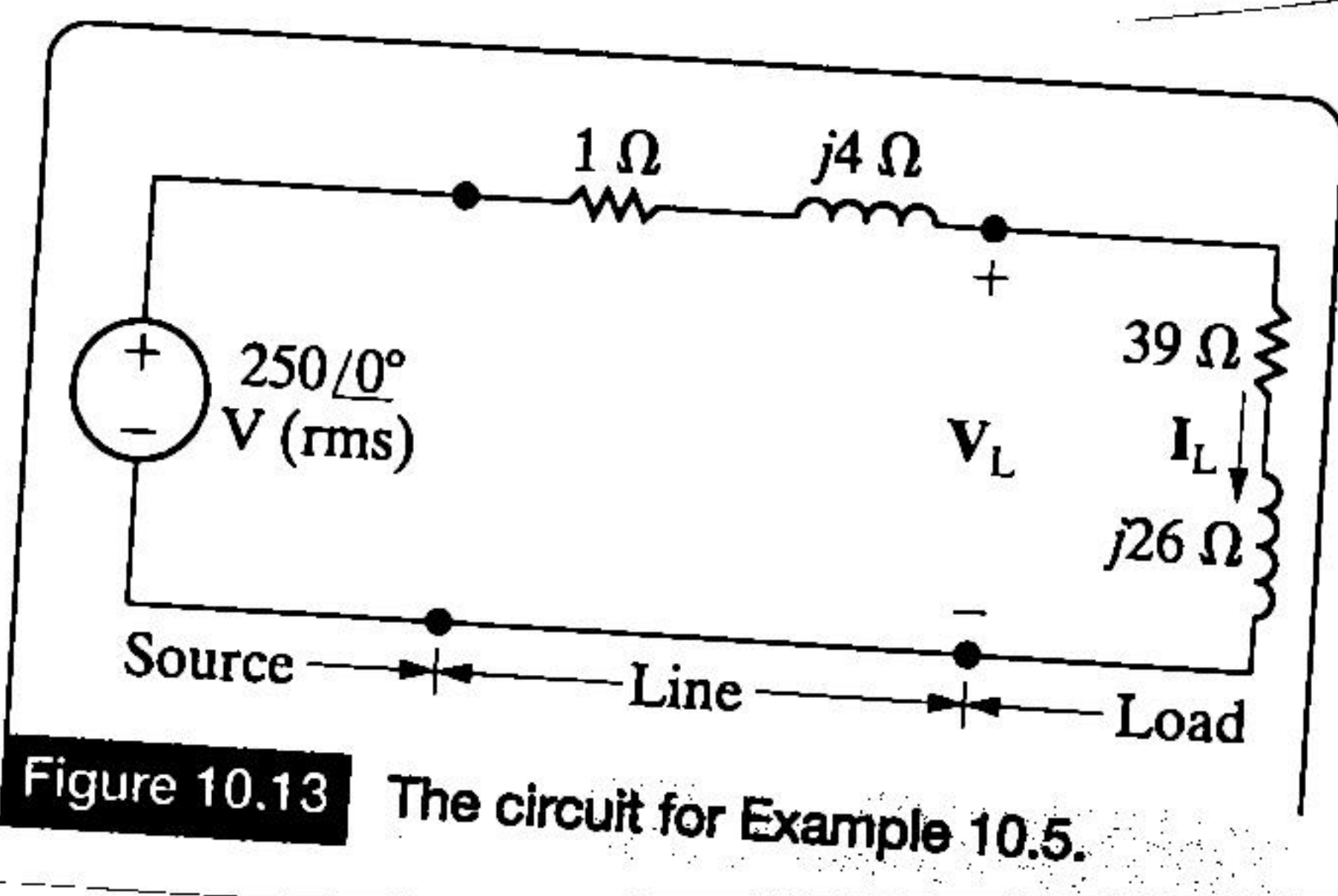
EXAMPLE 10.5

In the circuit shown in Fig. 10.13, a load having an impedance of $39 + j26 \Omega$ is fed from a voltage source through a line having an impedance of $1 + j4 \Omega$. The effective, or rms, value of the source voltage is 250 V.

- Calculate the load current I_L and voltage V_L .
- Calculate the average and reactive power delivered to the load.
- Calculate the average and reactive power delivered to the line.
- Calculate the average and reactive power supplied by the source.



SOLUTION

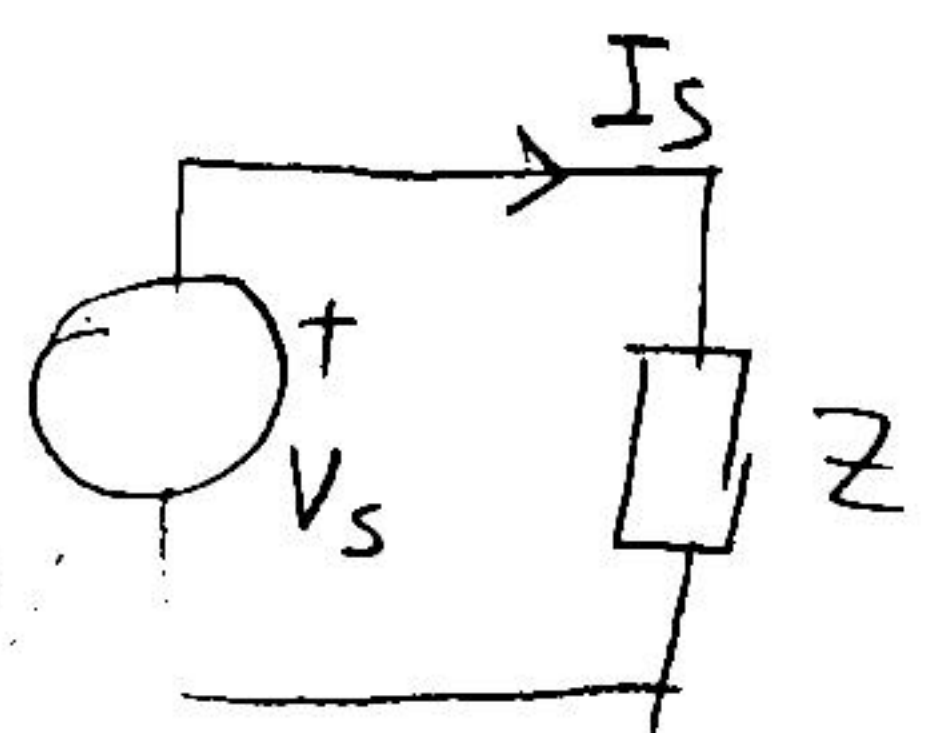

$$250\sqrt{2} = 354$$

$$\underline{V_s} = 354 \cos(\omega t + 0)$$

$$= 354 e^{j0}$$


$$\underline{Z} = (1 + j4) + (39 + j26)$$

$$= 40 + j30$$

$$\underline{I_L} = \frac{\underline{V_s}}{\underline{Z}} = \frac{354}{40 + j30} = \frac{354(40 - j30)}{40^2 + 30^2}$$

$$= \frac{14160 - j10620}{2500}$$

$$= 5.664 - j4.248$$

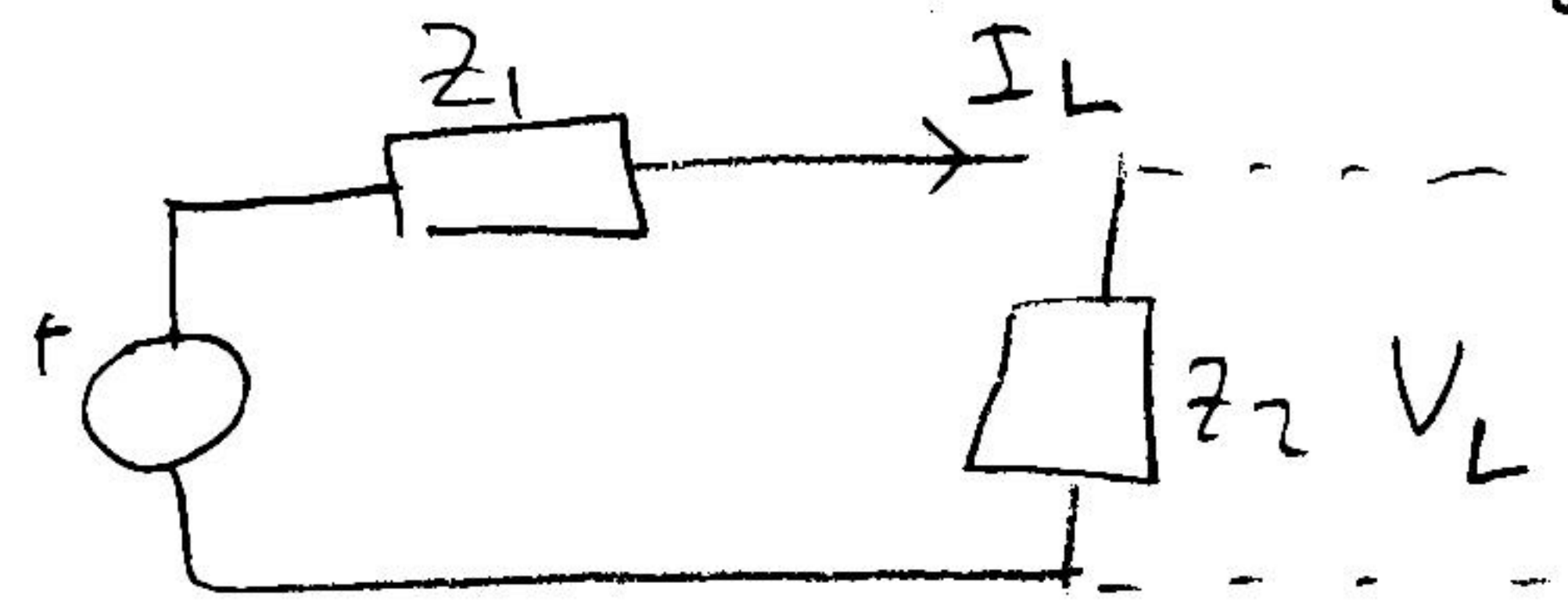

$$\underline{V_L} = \underline{Z_2} \underline{I_s} = (39 + j26)(5.66 - j4.24)$$

Power of Z_2 is

$$S = \frac{1}{2} \underline{V_L} \underline{I_L}^*$$

$$= \frac{1}{2} \underbrace{(39 + j26)(5.66 - j4.24)}_{\underline{V_L}} \underbrace{(5.66 + j4.24)}_{\underline{I_L}^*}$$

$$= \frac{1}{2} (39 + j26)(5.66^2 + 4.24^2)$$

$$= \frac{1}{2} (39 + j26) 50$$

$$= 975 + j650$$

$$P = 975 \text{ watt}$$

$$Q = 650 \text{ VAR}$$

Power of Z_1 is

$$S = \frac{1}{2} \underline{V_1} \underline{I_L}^* = \frac{1}{2} (1 + j4) \underline{I_L} \underline{I_L}^*$$

$$\underline{I_L} \underline{I_L}^* = 50$$

$$S = \frac{1}{2} (1 + j4) 50 = 25 + j100$$

$$P = 25 \text{ watt}$$

$$Q = 100 \text{ VAR}$$

Note:


$$(a+bj)(a-bj) = a^2 - abj + abj + b^2 = a^2 + b^2$$

$$|a+bj| = \sqrt{a^2 + b^2}$$

$$(a+bj)(a-bj) = |a+bj|^2$$

$$\phi \phi^* = |\phi|^2$$

Example: calculate P, ϕ, S

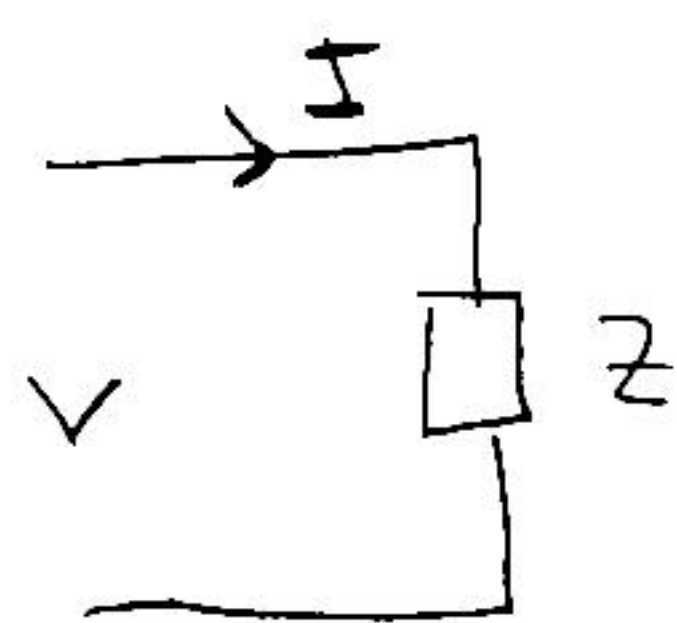

$$V_{eff} = 3 + 4j$$

$$Z = 8 + 6j$$

Solution: $S = V_{eff} I_{eff}^*$

$$V = Z \cdot I$$

$$S = V I^* = V \left(\frac{V}{Z} \right)^* = \frac{V V^*}{Z^*} = \frac{|V|^2}{Z^*}$$

$$= \frac{|3+4j|^2}{(8+6j)^*} = \frac{3^2+4^2}{8-6j} = \frac{25}{8-6j}$$

$$= \frac{25(8+6j)}{(8-6j)(8+6j)} = \frac{200+150j}{8^2+6^2}$$

$$= 2 + 1.5j$$

$$\downarrow \quad \downarrow$$


$$P \quad \phi$$

$$P = 2 \quad \phi = 1.5$$

Apparent power $|S|$

$$|S| = |2 + 1.5j| = \sqrt{2^2 + 1.5^2} = 2.5$$

Example: Calculate P, ϕ, S ^{Ex 9}

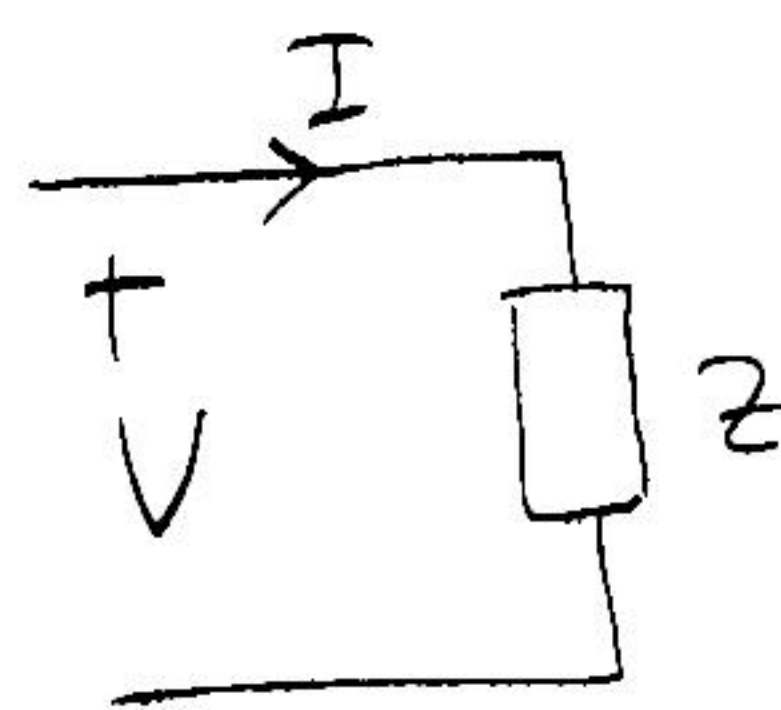

$$I = 4 + 3j$$

$$Z = 8 + 6j$$

solution $S = \frac{1}{2} V I^*$

$$V = Z I$$

$$S = \frac{1}{2} (Z I) I^* = \frac{1}{2} Z |I|^2$$


$$= \frac{1}{2} (8 + 6j) |4 + 3j|^2$$

$$= \frac{1}{2} (8 + 6j) 25 = 100 + 75j$$

$$P = 100 \text{ W} \quad \phi = 75 \text{ VAR}$$

$$|S| = \sqrt{100^2 + 75^2} = 125$$

Example: calculate power factor

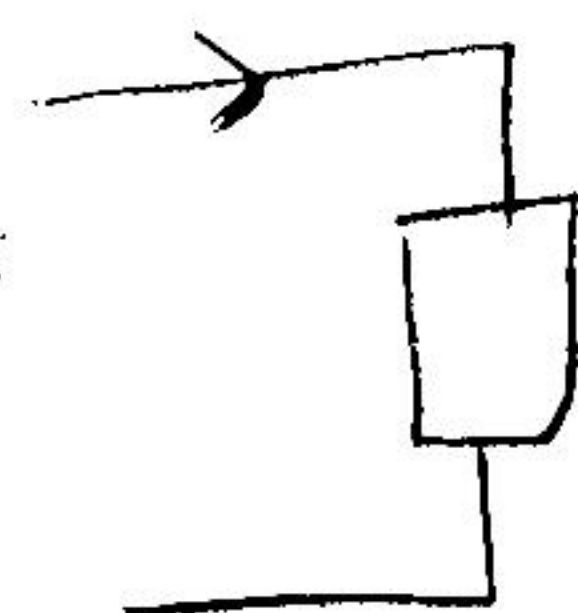


$$Z = 10 + 15j$$

$$\tan \theta = \frac{\phi}{P} = \frac{\text{Im}\{Z\}}{\text{Re}\{Z\}} = \frac{15}{10} = 1.5$$

$$\theta = 56.3^\circ$$

$$\cos \theta = 0.55 = \text{Power factor}$$

Example: calculate power factor

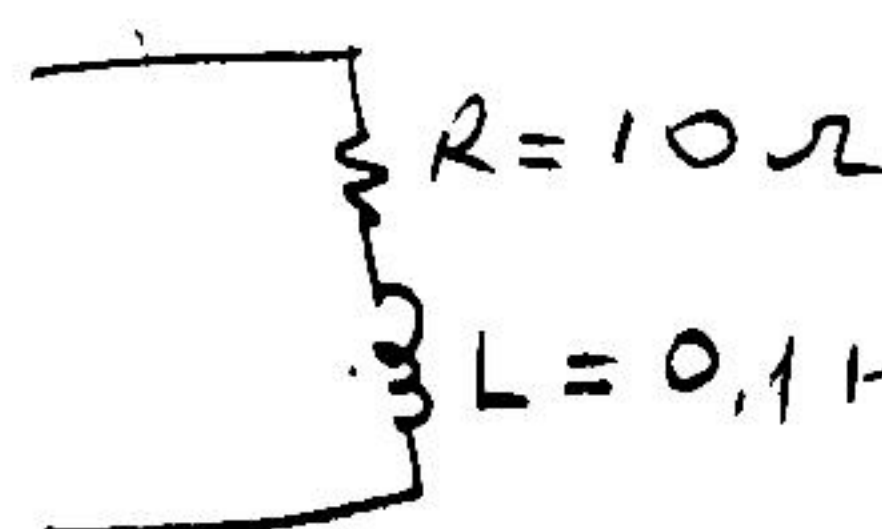

$$R = 10 \Omega$$

$$L = 0.1 \text{ H}$$

$$\omega = 10000$$

$$Z = R + j\omega L = 10 + 0.1 \cdot 10^4 j = 10 + 10j$$

$$\theta = \tan^{-1} \frac{10}{10} = 45^\circ \quad \cos \theta = 0.707$$