
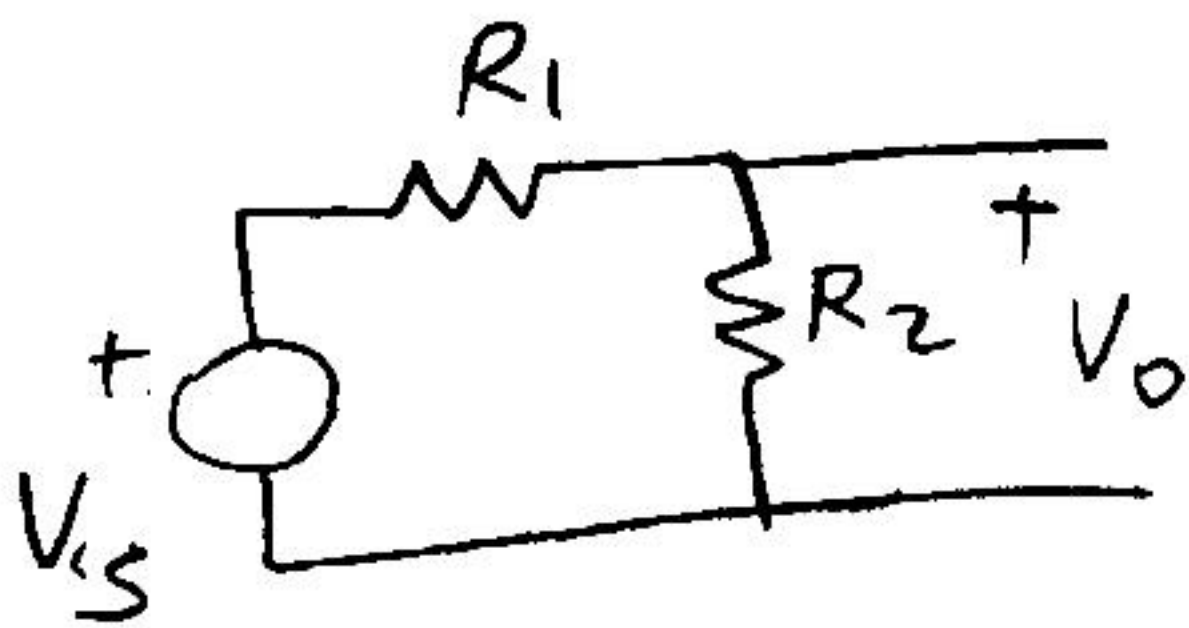


TRANSFER FUNCTION


e211

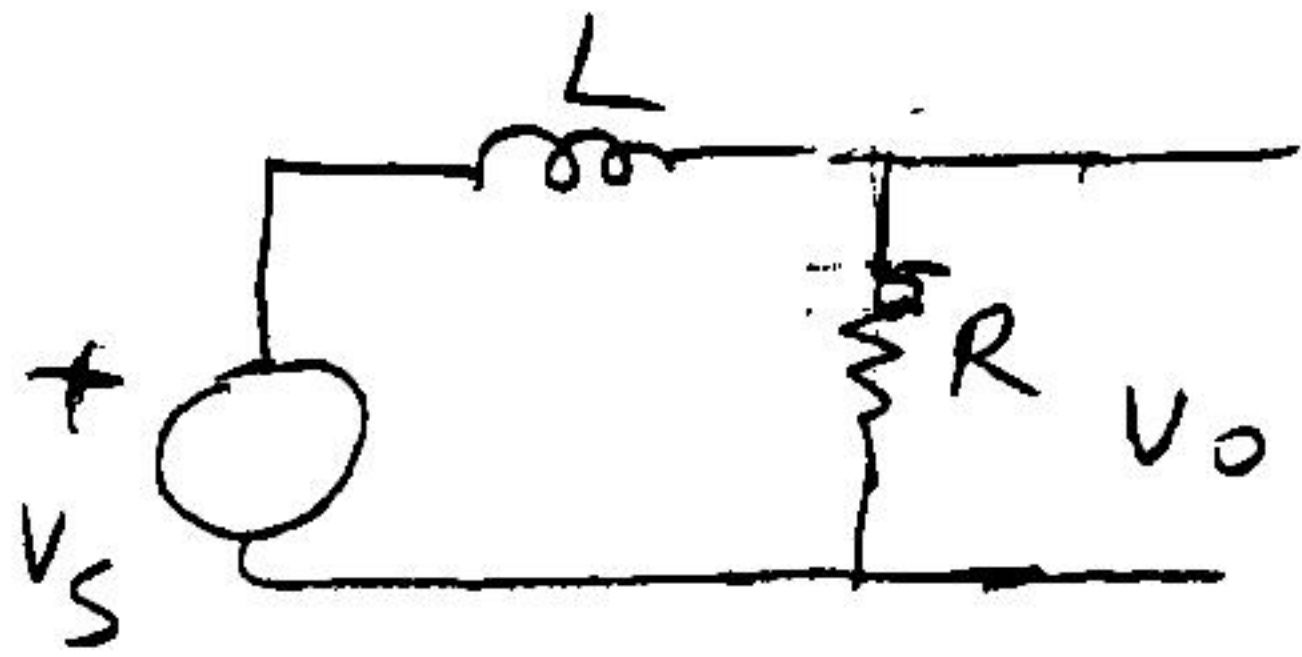


$$\frac{V_o}{V_s} = \frac{R_2}{R_2 + R_1}$$


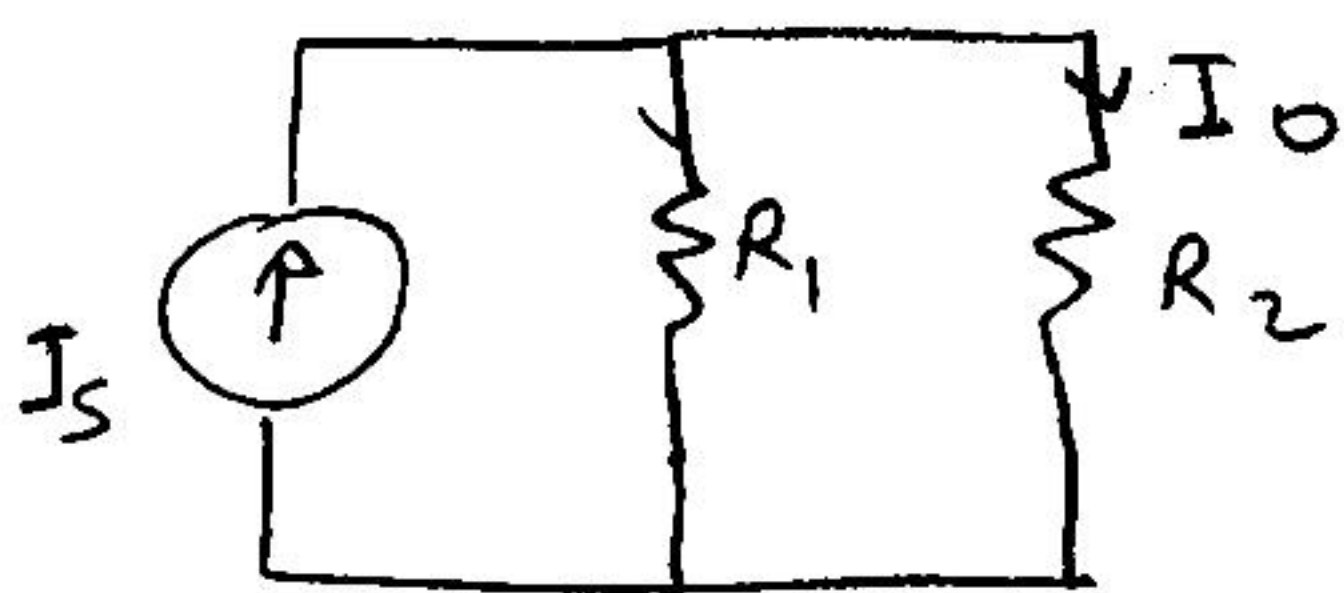
$$\frac{V_o}{V_s} = \frac{R}{R + j\omega L}$$



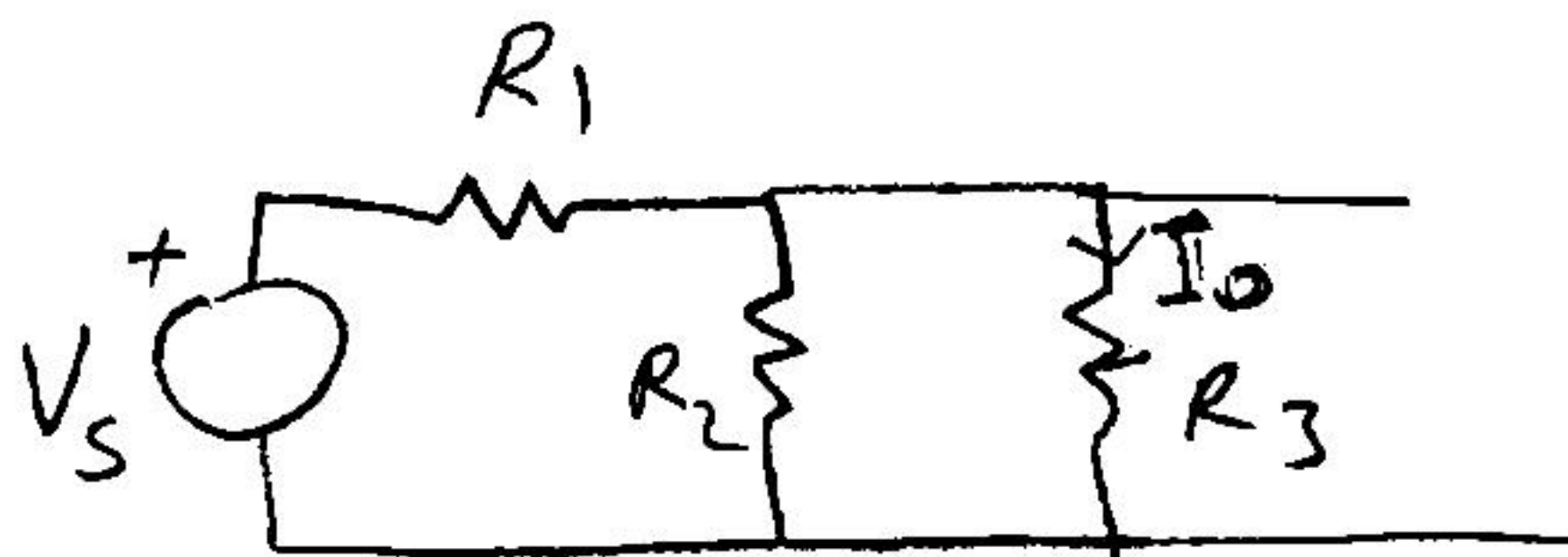
$$\frac{I_o}{I_s} = \frac{R_1}{R_1 + R_2}$$



$$\frac{I_o}{V_s} = \frac{R_{23}}{R_{23} + R_1} \cdot \frac{1}{R_3}$$

$$(R_{23} = R_2 \parallel R_3)$$

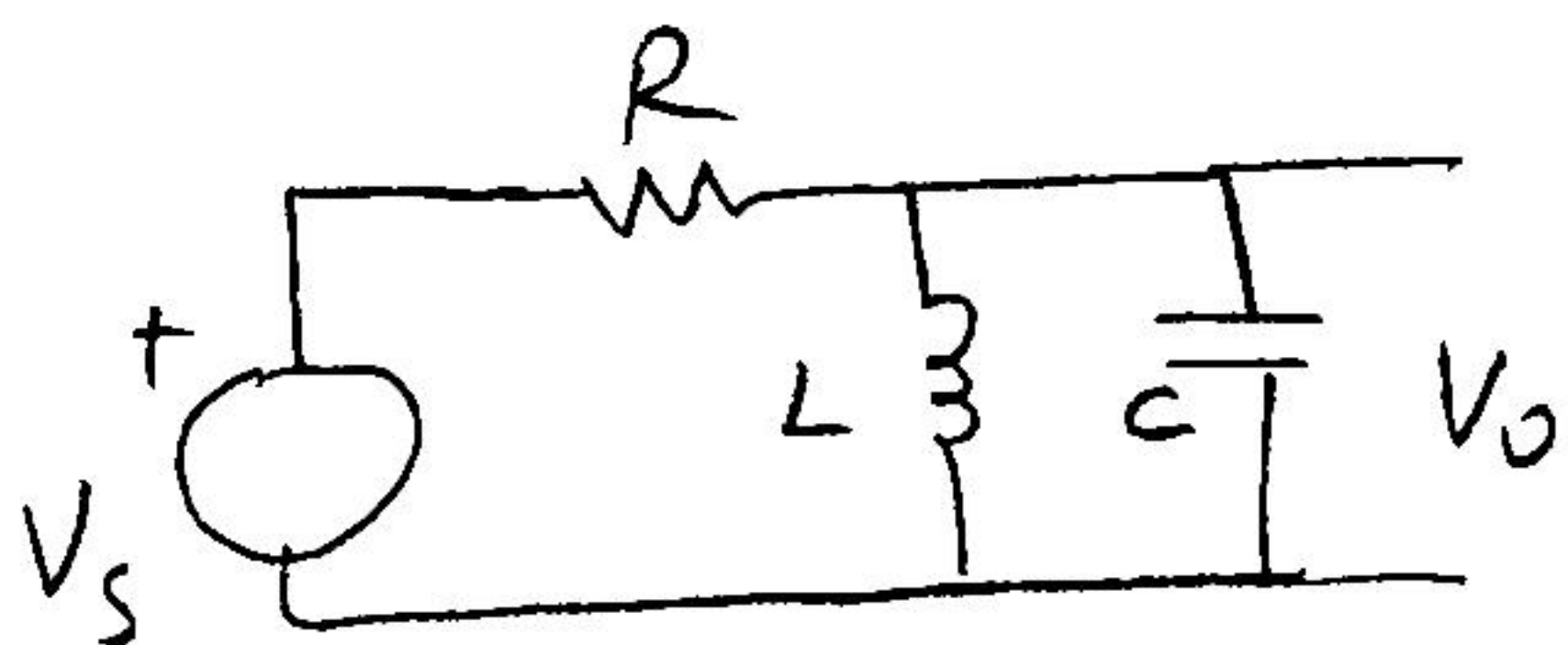


$$\frac{V_o}{V_s} = \frac{Z}{Z + R}$$

$$Z = j\omega L \parallel \frac{1}{j\omega C} = \frac{j\omega L}{1 - \omega^2 LC}$$

Transfer function = $\frac{\text{Output Voltage (or current)}}{\text{Input Voltage (or current)}}$

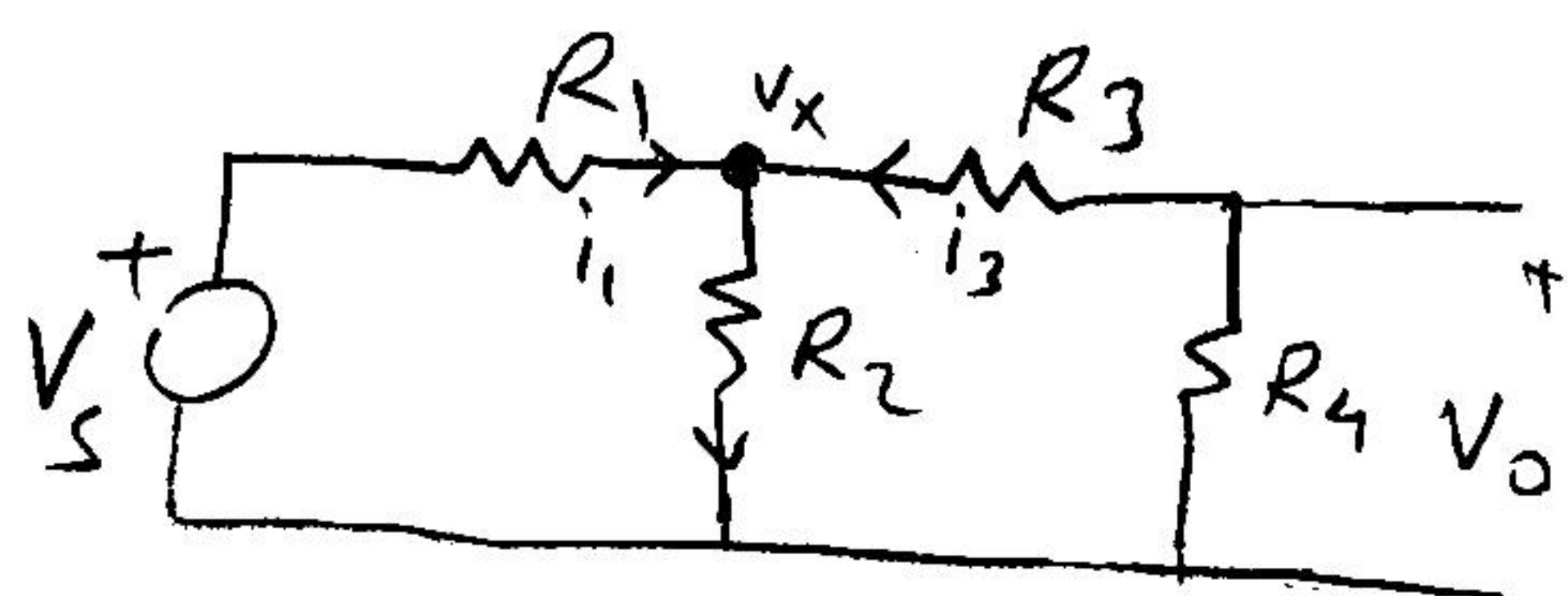Example: find the transfer function E212


$\frac{V_o}{V_s}$ and fill the table. $R_1=10$ $R_2=20$ $R_3=15$ $R_4=25$



V_s	10	20	100	-20
V_o	?	?	?	?

Solution $i_2 = i_1 + i_3$
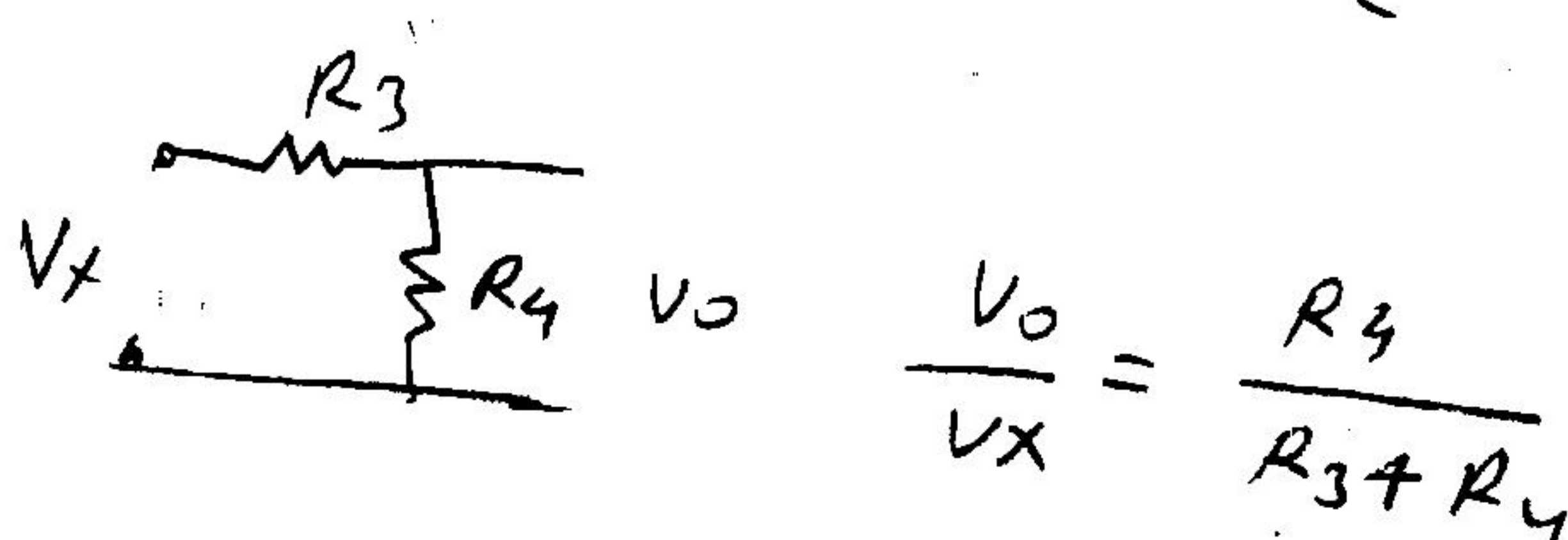
$$\frac{V_s - V_x}{R_1} + \frac{V_o - V_x}{R_3} = \frac{V_x}{R_2}$$



$$\frac{V_o}{V_x} = \frac{R_4}{R_3 + R_4}$$

$$V_x = \underbrace{\frac{R_3 + R_4}{R_4}}_{\alpha} V_o = \alpha V_o$$

$$\frac{V_s - \alpha V_o}{R_1} + \frac{V_o - \alpha V_o}{R_3} = \frac{\alpha V_o}{R_2}$$

$$\frac{V_s}{R_1} - \frac{\alpha V_o}{R_1} + \frac{(1-\alpha)}{R_3} V_o = \frac{\alpha V_o}{R_2}$$

$$\frac{V_s}{R_1} = V_o \left(\underbrace{\frac{\alpha}{R_1} + \frac{\alpha-1}{R_3} + \frac{\alpha}{R_2}}_M \right) \Rightarrow V_o = \frac{1}{M R_1} V_s \Rightarrow \frac{V_o}{V_s} = \frac{1}{M R_1}$$


$$\alpha = \frac{R_3 + R_4}{R_4} = \frac{15 + 25}{25} = \frac{40}{25} = 1.6$$

$$M = \frac{1.6}{10} + \frac{1.6-1}{15} + \frac{1.6}{20} = 0.28$$

$$V_o = \frac{1}{0.28 \times 10} V_s = 0.357 V_s$$

V_s	10	20	100	-20
V_o	3.57	7.14	35.7	-7.14

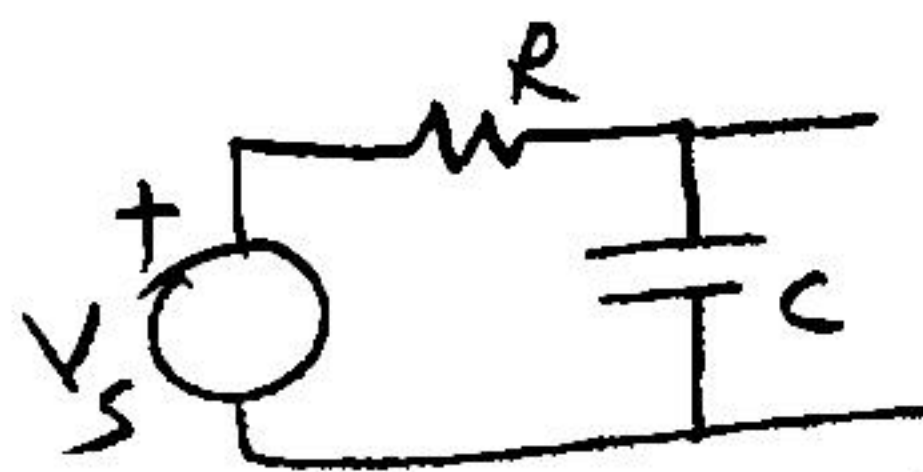
Example Problem calculate output voltage e221
 if a) $V_s = 10 \cos t$ b) $V_s = 10 \cos 2t$ c) $V_s = 10 \cos(2t + 30^\circ)$



d) $V_s = 10 \sin 3t$

$R = 2\Omega$ $C = 0.1\text{F}$

Solution

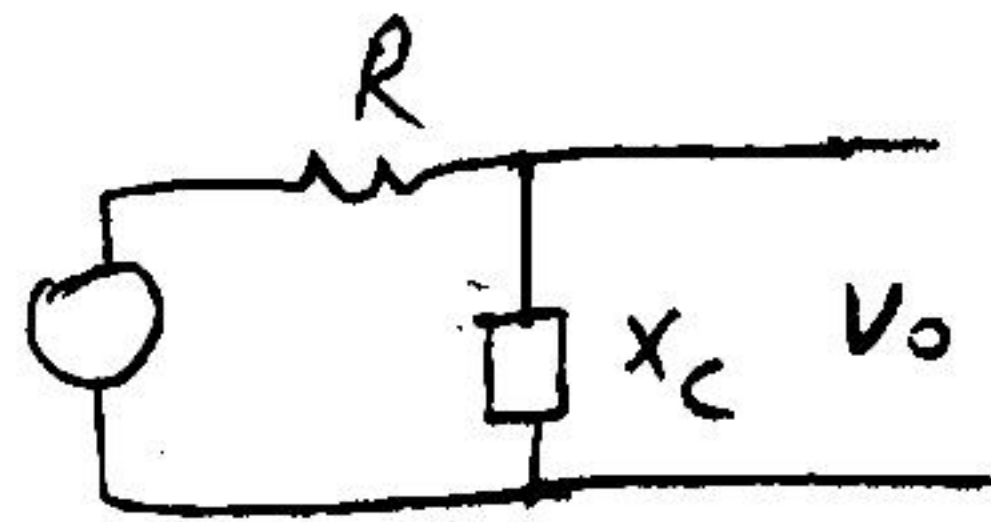

$\frac{V_o}{V_s} = \frac{X_c}{R + X_c}$ (Voltage divider)

$$V_o = \frac{X_c}{R + X_c} V_s = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} V_s = \frac{1}{j\omega CR + 1} V_s = \frac{1}{j\omega 0.1 \times 2 + 1} V_s$$

a) $V_s = 10 \cos t \Rightarrow \underline{V_s} = 10$ $\omega = 1$

$$V_o = \frac{1}{j\omega 0.2 + 1} V_s = \frac{1}{j \times 1 \times 0.2 + 1} 10 = \frac{1}{1 + 0.2j} 10 = \frac{10}{\sqrt{1^2 + 0.2^2}} e^{j\theta}$$

$$V_o = \frac{10}{\sqrt{1.04}} e^{j11} = \frac{10}{1.019} e^{-j11.3} = 9.80 e^{-j11.3^\circ}$$

$\theta = \tan^{-1} \frac{0.2}{1} = 11.3^\circ$

$V_o(t) = 9.80 \cos(t - 11.3^\circ)$

b) $V_s = 10 \cos 2t$ $\underline{V_s} = 10$ $\omega = 2$

$$V_o = \frac{1}{j\omega 0.2 + 1} V_s = \frac{1}{j \times 2 \times 0.2 + 1} 10 = \frac{10}{1 + 0.4j} = \frac{10}{\sqrt{1 + 0.4^2}} e^{j\theta}$$

$\theta = \tan^{-1} \frac{0.4}{1} = 21.8^\circ$

$$V_o = \frac{10}{\sqrt{1.16}} e^{j21.8} = 9.28 e^{-j21.8}$$

$V_o(t) = 9.28 \cos(2t - 21.8^\circ)$

$$c) V_s = 10 \cos(2t + 30) \quad \underline{V_s} = 10 e^{j30} \quad \omega = 2$$

$$V_o = \frac{V_s}{j\omega 0.2 + 1} = \frac{V_s}{j2 \times 0.2 + 1} = \frac{10 e^{j30}}{1 + 0.4j} = \frac{10 e^{j30}}{\sqrt{1.16} e^{j21.8}}$$

$$= \frac{10}{\sqrt{1.16}} e^{j(30 - 21.8)} = 9.28 e^{j8.2^\circ}$$

$$V_o(t) = 9.28 \cos(2t + 8.2^\circ)$$

$$d) V_s = 10 \sin 3t = 10 \cos(3t - 90) \quad \underline{V_s} = 10 e^{-j90} \quad \omega = 3$$

$$V_o = \frac{V_s}{j\omega 0.2 + 1} = \frac{10 e^{-j90}}{j \times 3 \times 0.2 + 1} = \frac{10 e^{-j90}}{1 + j0.6} = \frac{10 e^{-j90}}{\sqrt{1^2 + 0.6^2} e^{j\theta}}$$

$$\theta = \tan^{-1} \frac{0.6}{1} = 30.9^\circ$$

$$V_o = \frac{10}{\sqrt{1.36}} e^{j(-90 - 30.9)} = 8.57 e^{-j120.9}$$


$$V_o(t) = 8.57 \cos(3t - 120.9)$$

or


$$V_o(t) = 8.57 \sin(3t - 120.9 + 90) = 8.57 \sin(3t - 30.9)$$

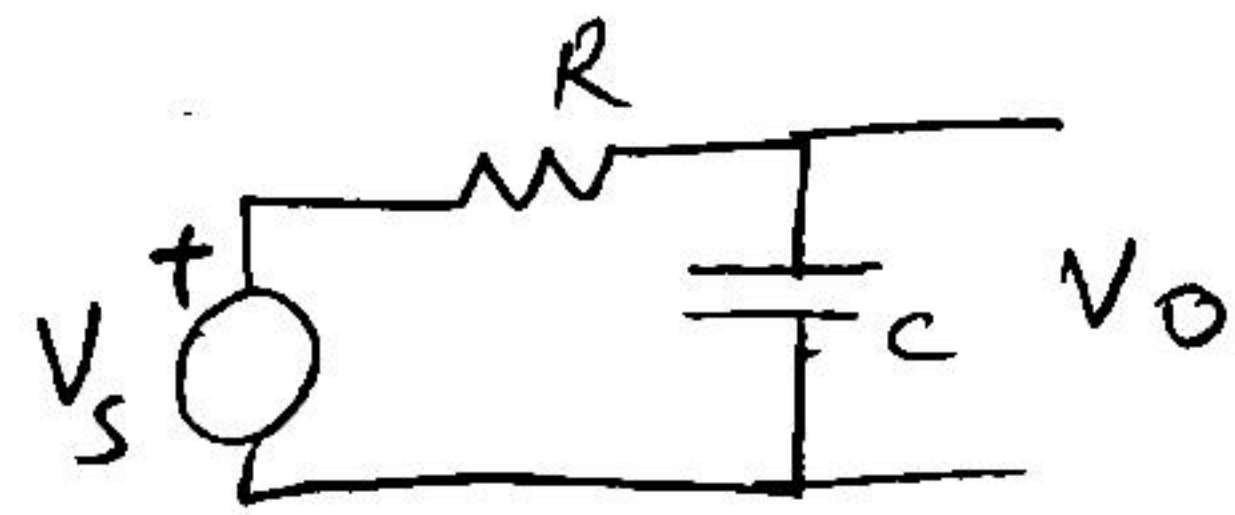Example problem: Calculate output voltage ^{e223}

- if a) $V_s = 10 \cos t$ b) $V_s = 10 \cos 2t$ c) $V_s = 10 \cos(2t + 30)$
 d) $V_s = 10 \sin 3t$ e) $V_s = 10 \cos 10t$



$$R = 2\Omega \quad C = 0.1 \text{ F}$$

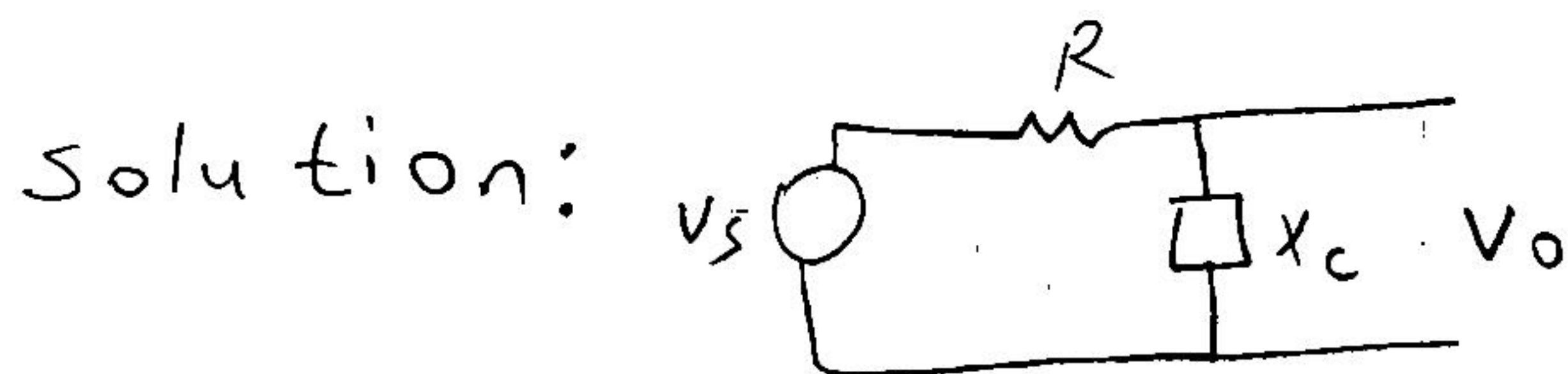

$$V_o = \frac{X_c}{R + X_c} V_s \quad (\text{Voltage divider})$$

$$\frac{V_o}{V_s} = \frac{X_c}{R + X_c} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{j\omega CR + 1} = \frac{1}{j\omega \cdot 0.1 \cdot 2 + 1} = \frac{1}{j\omega 0.2 + 1}$$

$$V_s = 10 \cos t \Rightarrow \underline{V_s} = 10 e^{j0} = 10 \quad \omega = 1$$

$$V_s = 10 \cos 2t \Rightarrow V_s = 10 \quad \omega = 2$$

$$V_s = 10 \cos 3t \Rightarrow V_s = 10 \quad \omega = 3$$

⋮

$$V_s = 10 \cos 10t \Rightarrow V_s = 10 \quad \omega = 10$$

$$\frac{V_o}{V_s} = \frac{1}{j\omega 0.2 + 1} \quad \left| \frac{V_o}{V_s} \right| = \frac{1}{|j\omega 0.2 + 1|} = \frac{1}{\sqrt{(0.2\omega)^2 + 1^2}}$$

$$\angle \frac{V_o}{V_s} = \angle 1 - \angle j\omega 0.2 + 1$$

$$= 0 - \tan^{-1} \frac{0.2\omega}{1}$$

$$\omega = 1 \Rightarrow \left| \frac{V_o}{V_s} \right| = \frac{1}{\sqrt{(0.2 \times 1)^2 + 1^2}} = \frac{1}{\sqrt{1.04}} = 0.98$$

$$\angle \frac{V_o}{V_s} = -\tan^{-1} 0.2\omega = -\tan^{-1} 0.2 = -11.3^\circ$$

$$\left| \frac{V_o}{V_s} \right| = \frac{1}{\sqrt{(0,2\omega)^2 + 1}}$$

$$\omega = 2 \quad \left| \frac{V_o}{V_s} \right| = \frac{1}{\sqrt{(0,2 \times 2)^2 + 1}} = \frac{1}{\sqrt{1,46}} = 0,928$$

$$\angle \frac{V_o}{V_s} = -\tan^{-1} 0,2\omega = -\tan^{-1} 0,2 \times 2 = -\tan^{-1} 0,4 = -21,8$$

$$\omega = 3 \quad \left| \frac{V_o}{V_s} \right| = \frac{1}{\sqrt{(0,2 \times 3)^2 + 1}} = \frac{1}{\sqrt{1,36}} = 0,857$$

$$\angle \frac{V_o}{V_s} = -\tan^{-1} 0,2 \times 3 = -30,9^\circ$$

$$\omega = 4 \Rightarrow \left| \frac{V_o}{V_s} \right| = \quad \angle \frac{V_o}{V_s} =$$

$$\omega = 5 \Rightarrow \left| \frac{V_o}{V_s} \right| = \quad \angle \frac{V_o}{V_s} =$$

$$\omega = 10 \Rightarrow \left| \frac{V_o}{V_s} \right| = \quad \angle \frac{V_o}{V_s} =$$

ω	1	2	3	4
$\left \frac{V_o}{V_s} \right $	0,98	0,928	0,857	
$\angle \frac{V_o}{V_s}$	-11,3	-21,8	-30,9	

$$a) V_s = 10 \cos t \Rightarrow V_o = 10 \times 0,98 \cos(t - 11,9) = 9,8 \cos(t - 11,9)$$

$$b) V_s = 10 \cos 2t \Rightarrow V_o = 10 \times 0,928 \cos(2t - 21,8) = 9,28 \cos(2t - 21,8)$$


$$c) V_s = 10 \cos(2t + 30) \Rightarrow V_o = 10 \times 0,928 \cos(2t + 30 - 21,8) = 9,28 \cos(2t + 8,2)$$

$$d) V_s = 10 \sin 3t \Rightarrow V_o = 10 \times 0,857 \sin(3t - 30,9) = 8,57 \sin(3t - 30,9)$$


SPECTRUM

e225


ω	0	1	2	3	4	5	6	8	10	100
$\left \frac{V_o}{V_s} \right $	1	0.98	0.92	0.85	0.78	0.707	0.64	0.53	0.44	0.05
$\angle \frac{V_o}{V_s}$	0	-11.9	-21.8	-30.9	-38	-45	-50	-54	-63	-87

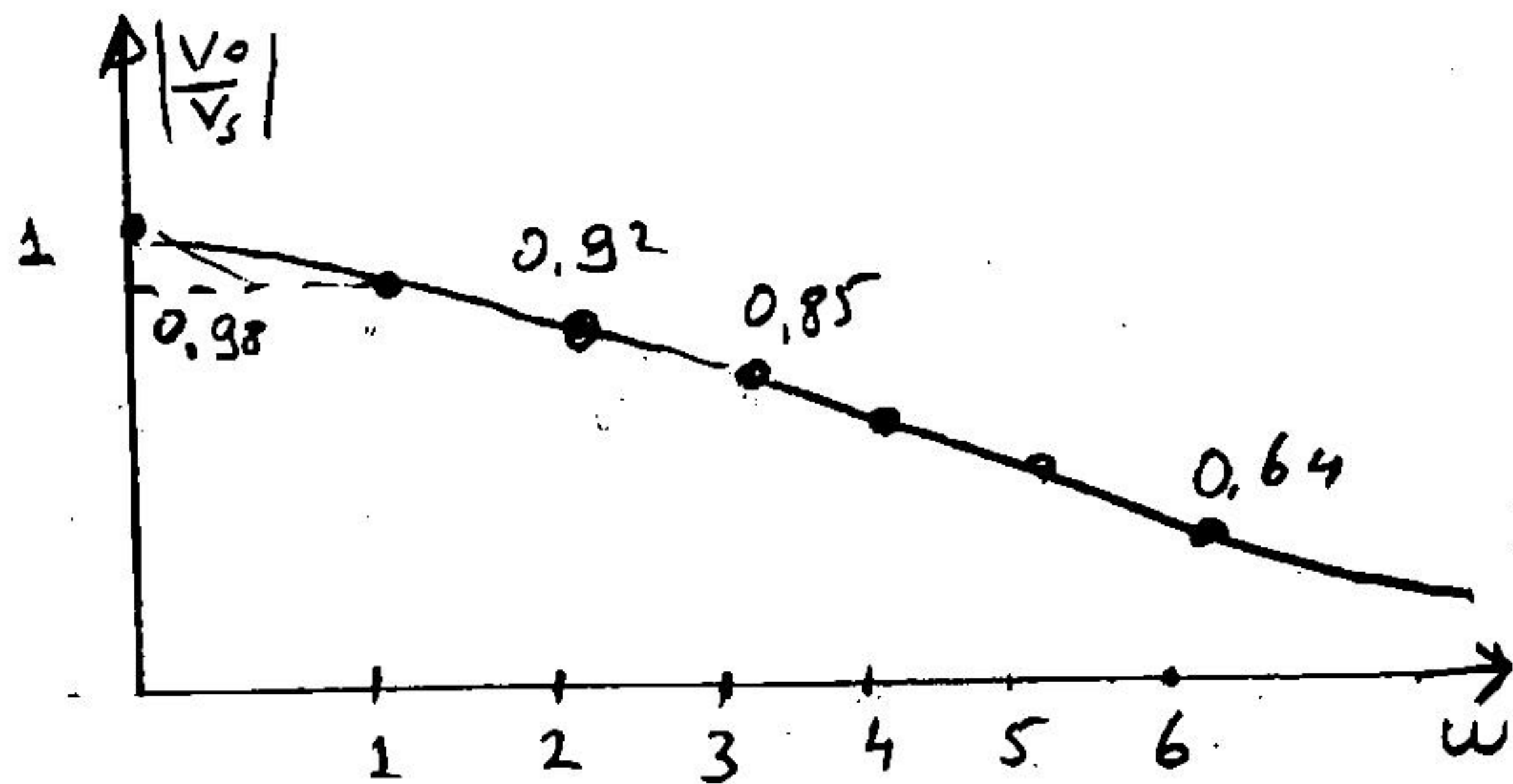

Amplitude spectrum

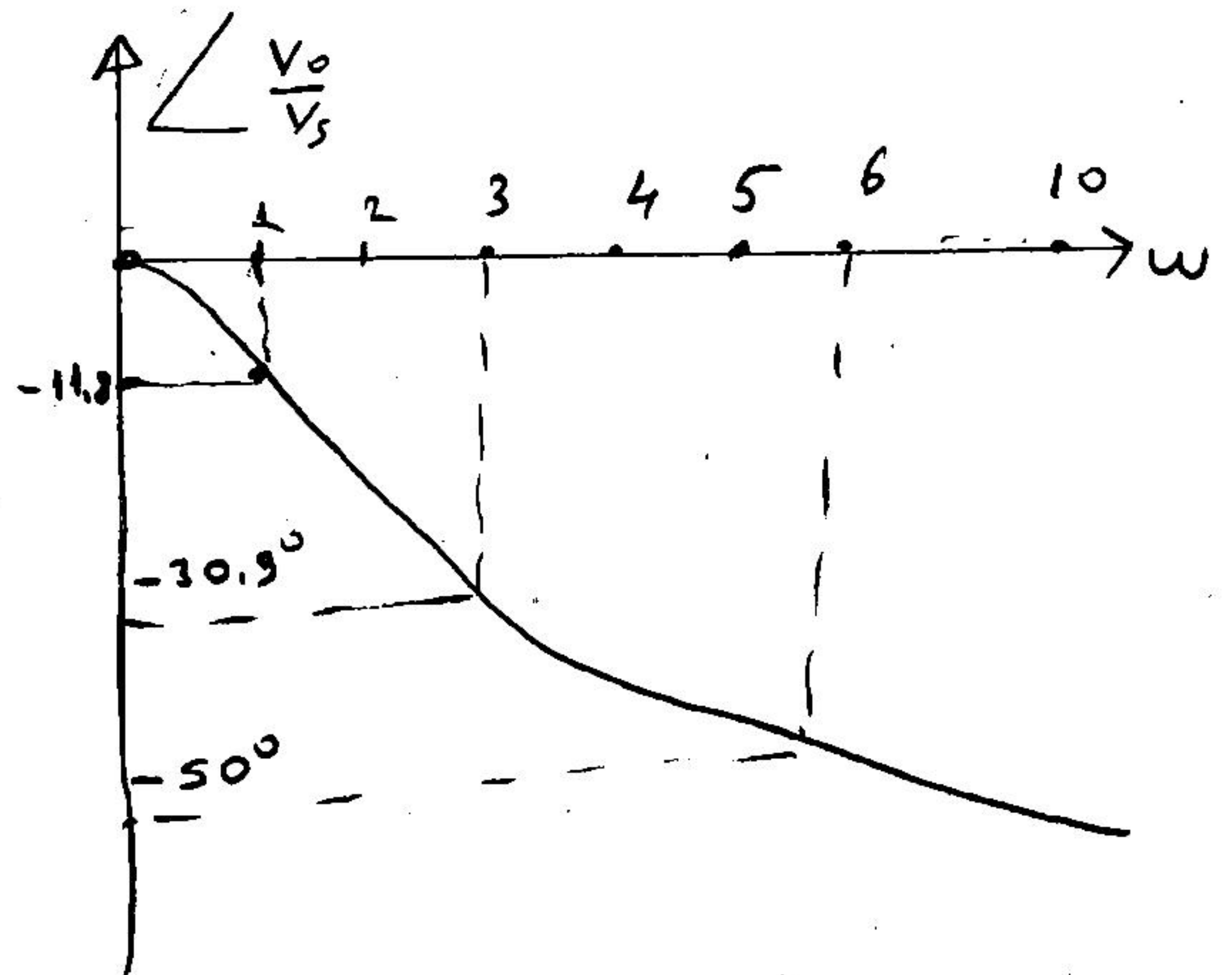


phase spectrum

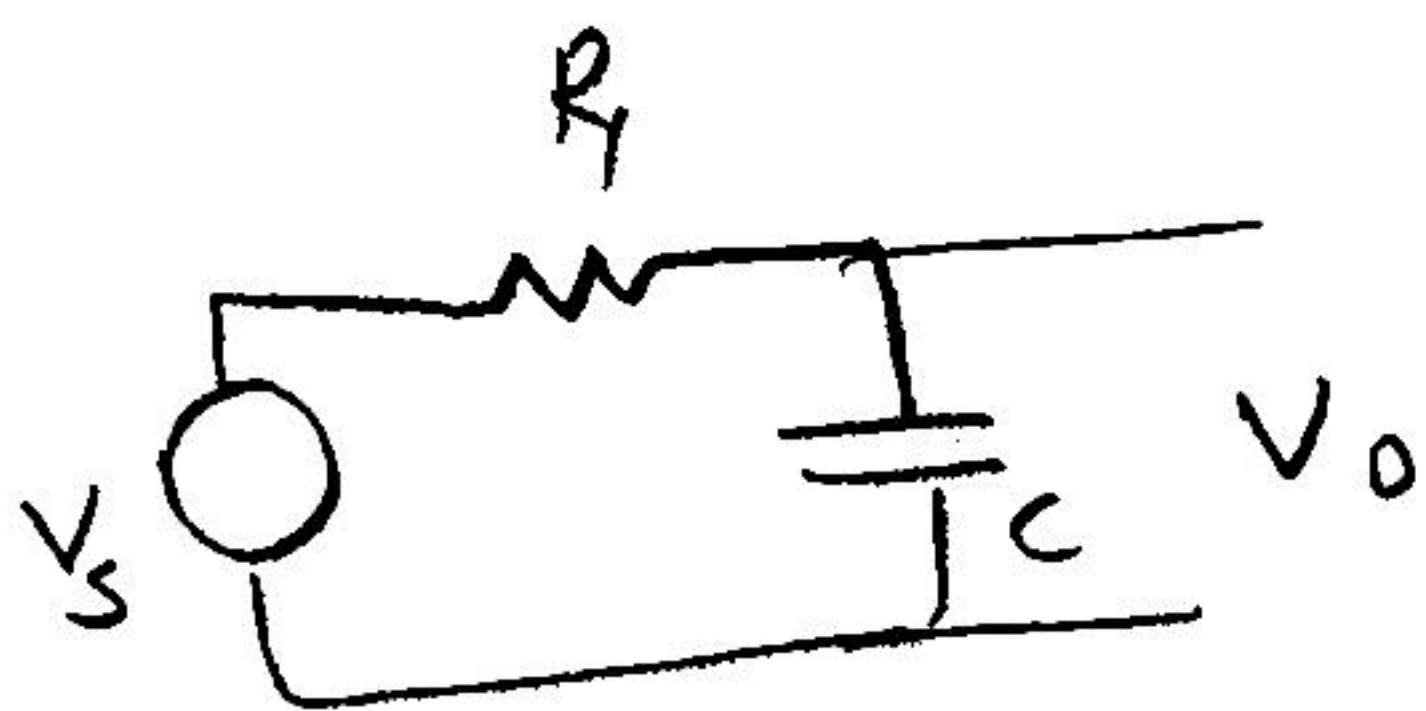


$$\frac{V_o}{V_s} = \frac{1}{j\omega CR + 1} = \frac{1}{0.2j\omega + 1}$$

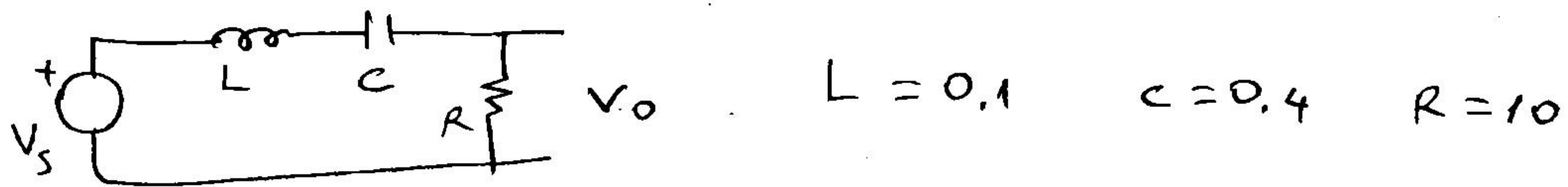Example problem: calculate transfer function²²⁶ and draw amplitude and phase spectrum



Solution:

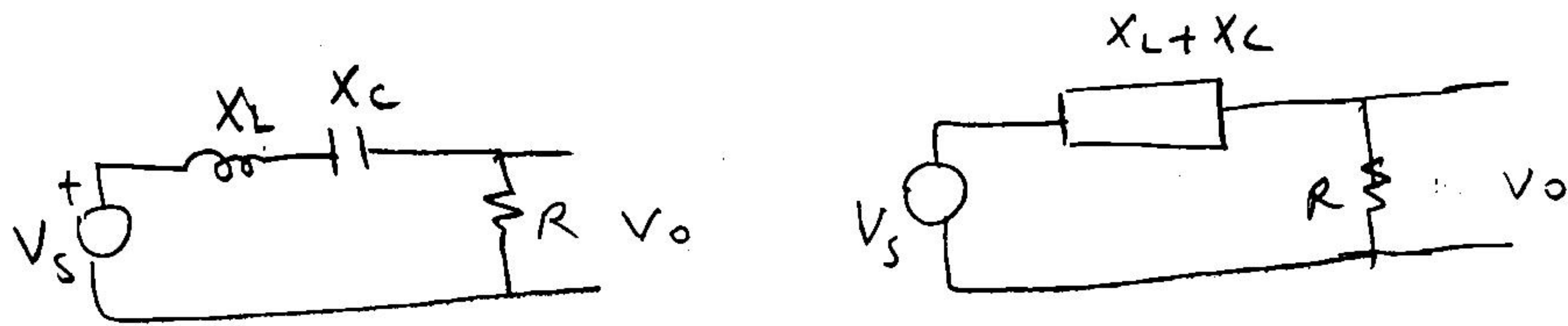

$$\frac{V_o}{V_s} = \frac{R}{R + X_L + X_C} = \frac{R}{R + j\omega L + \frac{1}{j\omega C}} = \frac{R}{R + j(\omega L - \frac{1}{\omega C})}$$

$$= \frac{10}{10 + j(0.1\omega - \frac{1}{0.4\omega})}$$

$$\left| \frac{V_o}{V_s} \right| = \frac{10}{\sqrt{10^2 + (0.1\omega - \frac{1}{0.4\omega})^2}}$$

$$\angle \frac{V_o}{V_s} = \angle 10 - \angle (10 + j(0.1\omega - \frac{1}{0.4\omega}))$$

$$\downarrow$$

$$= 0 - \tan^{-1} \left(\frac{0.1\omega - \frac{1}{0.4\omega}}{10} \right)$$

$$\omega = 1 \Rightarrow \left| \frac{V_o}{V_s} \right| = \frac{10}{\sqrt{10^2 + (0.1 \times 1 - \frac{1}{0.4 \times 1})^2}} =$$



$$\angle \frac{V_o}{V_s} = -\tan^{-1} \left(\frac{0.1 \times 1 - \frac{1}{0.4 \times 1}}{10} \right) =$$

$$\omega = 2 \Rightarrow \left| \frac{V_o}{V_s} \right| = \frac{10}{\sqrt{10^2 + \left(0.1\omega - \frac{1}{0.4\omega}\right)^2}} = \frac{10}{\sqrt{10^2 + \left(0.1 \times 2 - \frac{1}{0.4 \times 2}\right)^2}} =$$

e227



$$\angle \frac{V_o}{V_s} = -\tan^{-1}\left(0.1 \times 2 - \frac{1}{0.4 \times 2}\right) =$$

ω	1	2	3	4	5	6	7	8	9	10	20	30	40	50	100	∞
$\left \frac{V_o}{V_s} \right $	0.97	0.99	0.99	0.99	1	0.99	0.99	0.99	0.99	0.99	0.98	0.96	0.93	0.89	0.7	0
$\angle \frac{V_o}{V_s}$	13°	5.9°	3°	1.2°	0	-1°	-1.9°	-2.7°	-3.5°	-4.2°	-10°	-16°	-21°	-26°	-44°	-90°

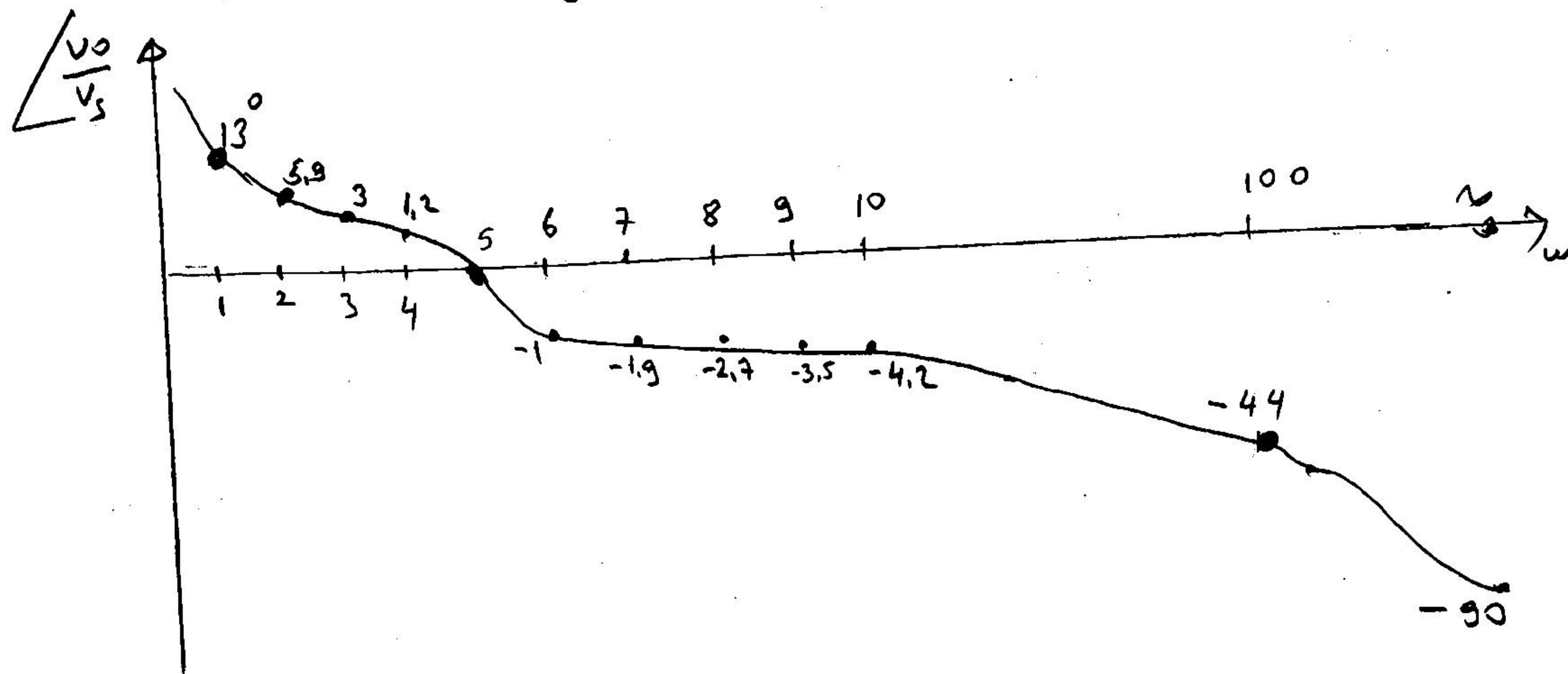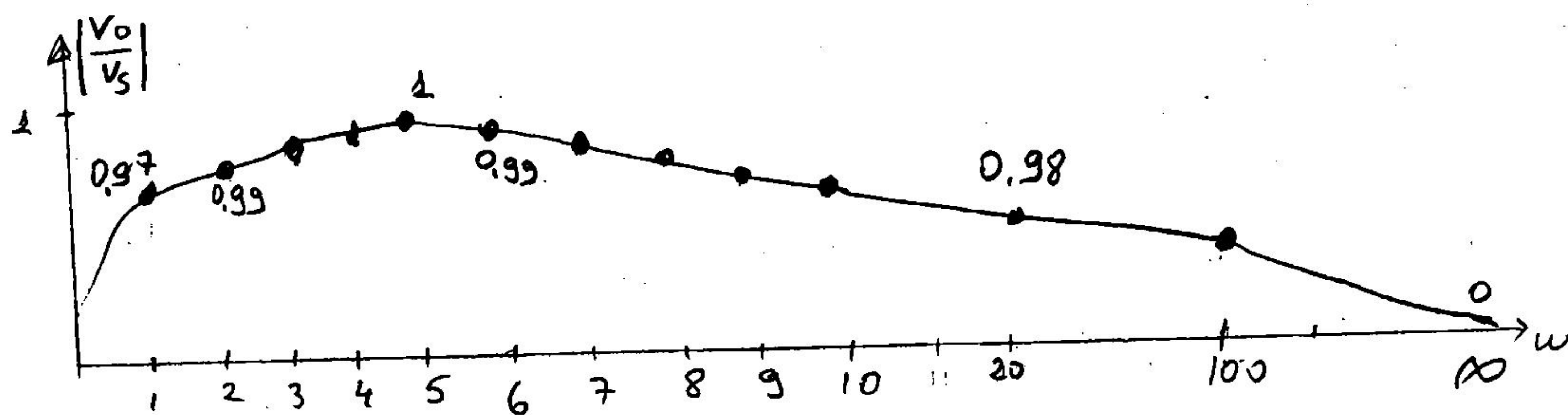


Example Problem: Calculate the output

e228

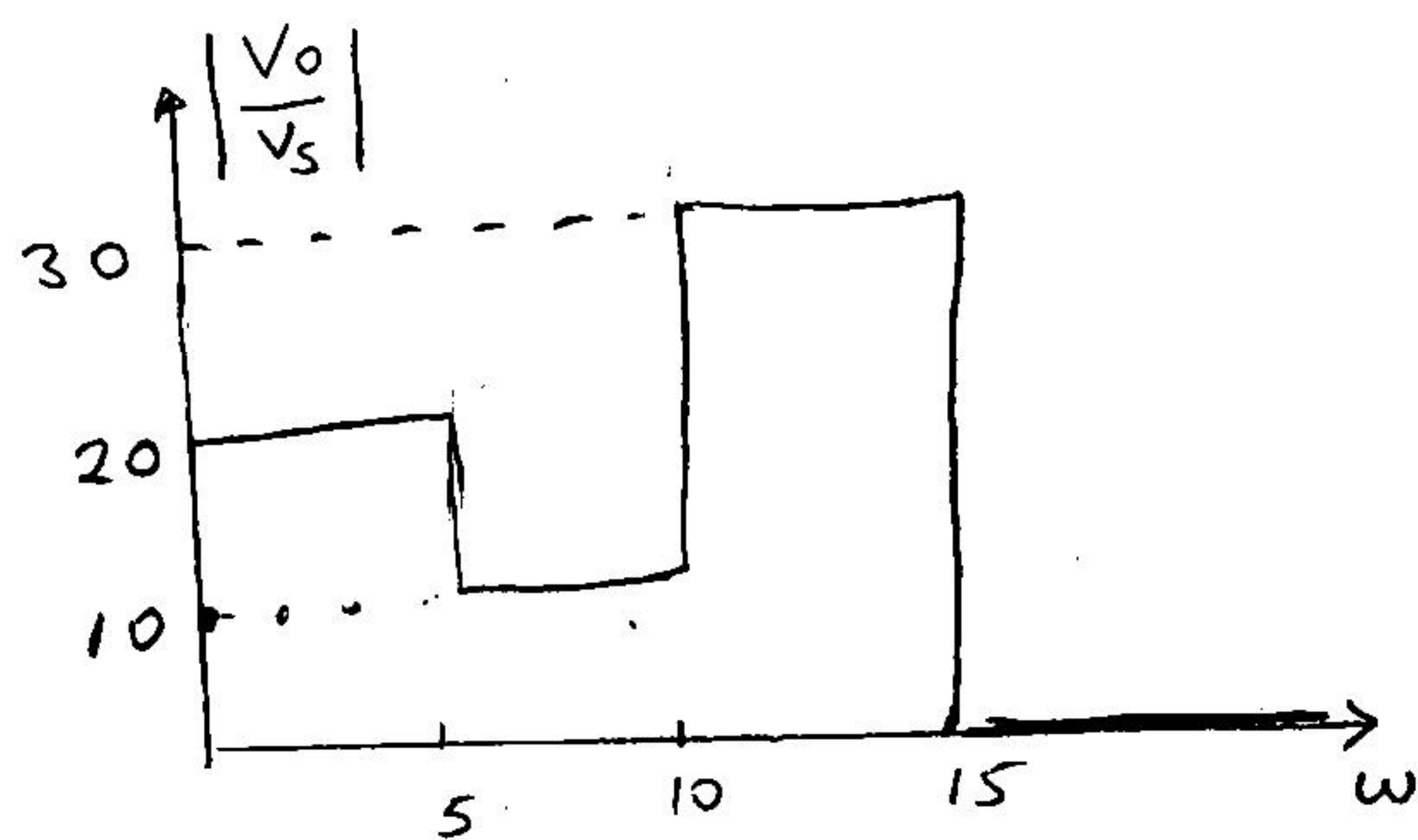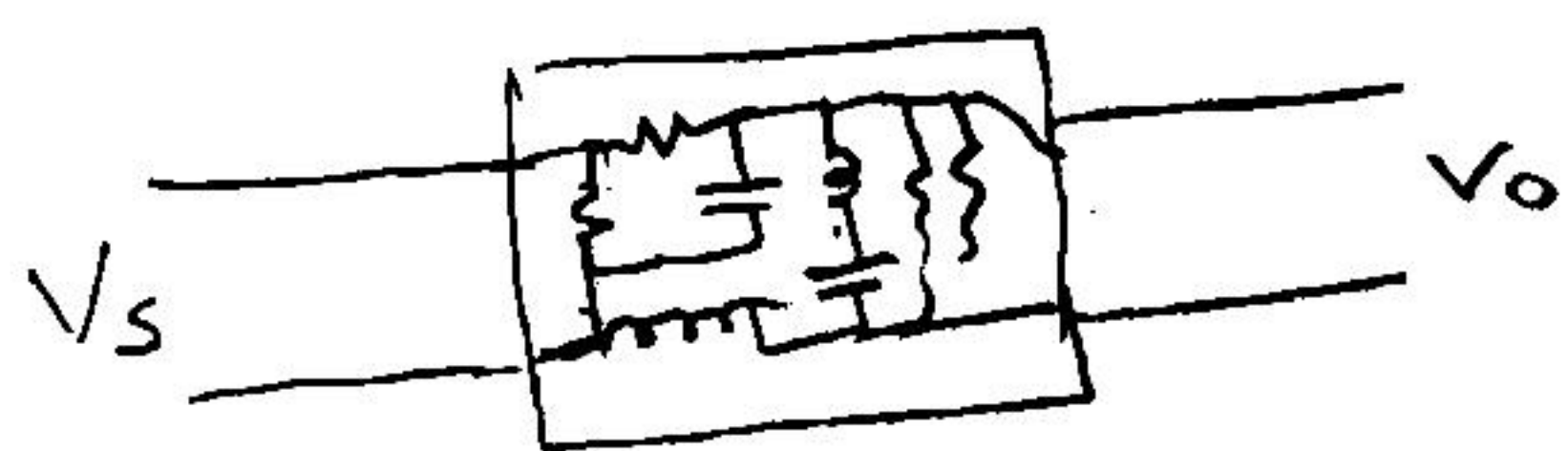

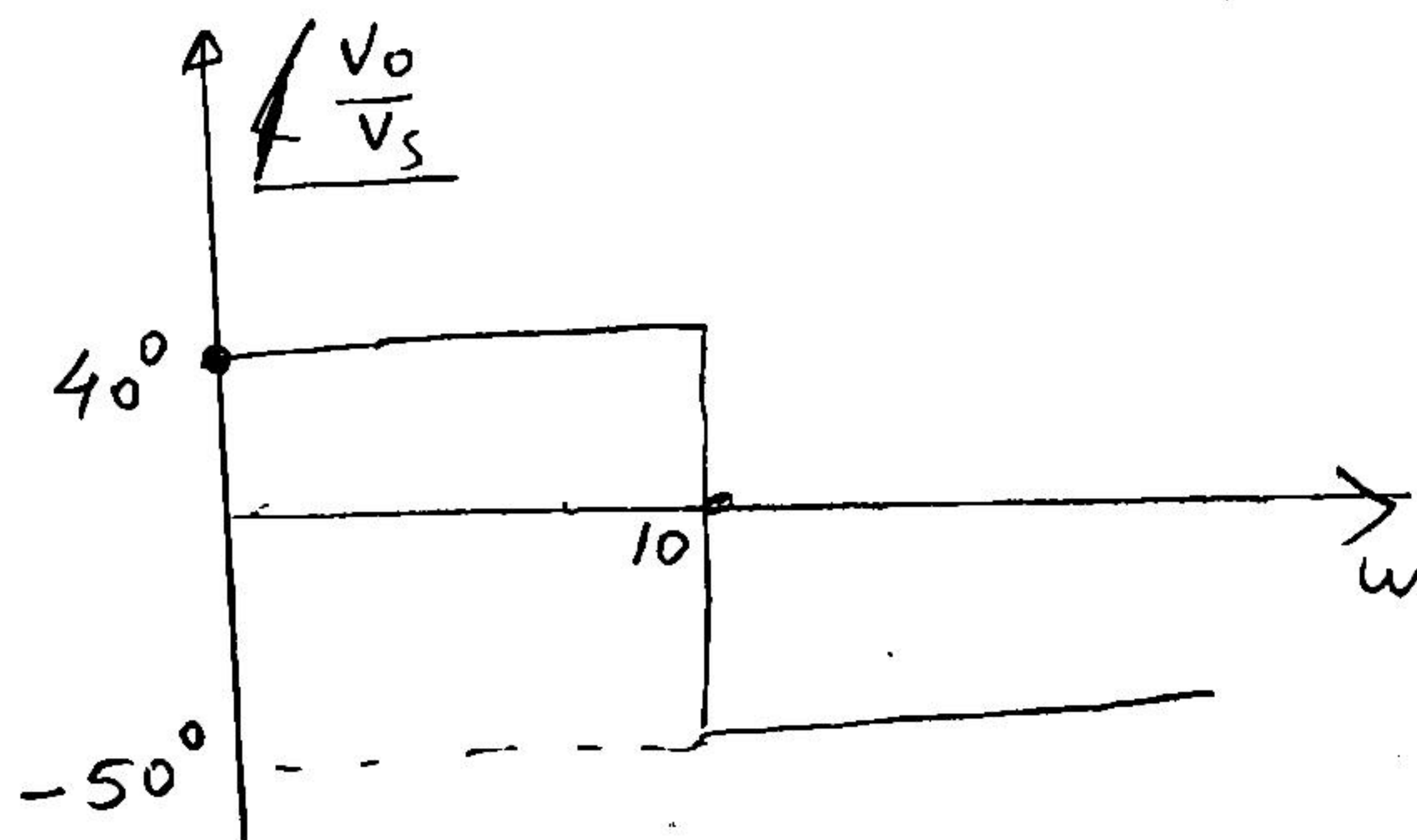- a) $V_s = 4 \cos 2t$
- b) $V_s = 5 \cos(6t + 20^\circ)$
- c) $V_s = 2 \cos(13t + 60^\circ)$
- d) $V_s = 10 \cos 25t$



a) $V_s = 4 \cos 2t$ $\omega = 2$ $\left| \frac{V_o}{V_s} \right| = 20$ $\angle \frac{V_o}{V_s} = 40^\circ$

$$V_o = 4 \times 20 \cos(2t + 40^\circ) = 80 \cos(2t + 40^\circ)$$

b) $V_s = 5 \cos(6t + 20^\circ)$ $\omega = 6$ $\left| \frac{V_o}{V_s} \right| = 10$ $\angle \frac{V_o}{V_s} = 40^\circ$

$$V_o = 5 \times 10 \cos(6t + 20^\circ + 40^\circ) = 50 \cos(6t + 60^\circ)$$

c) $V_s = 2 \cos(13t + 60^\circ)$ $\omega = 13$ $\left| \frac{V_o}{V_s} \right| = 30$ $\angle \frac{V_o}{V_s} = -50^\circ$

$$V_o = 2 \times 30 \cos(13t + 60^\circ - 50^\circ) = 60 \cos(13t + 10^\circ)$$


d) $V_s = 10 \cos 25t$ $\omega = 25$ $\left| \frac{V_o}{V_s} \right| = 0$ $\angle \frac{V_o}{V_s} = -50^\circ$

$$V_o = 10 \times 0 \cos(25t - 50^\circ) = 0$$



Filters

e22g


$$V_s = \cos 5t + \cos 50t + \cos 500t$$

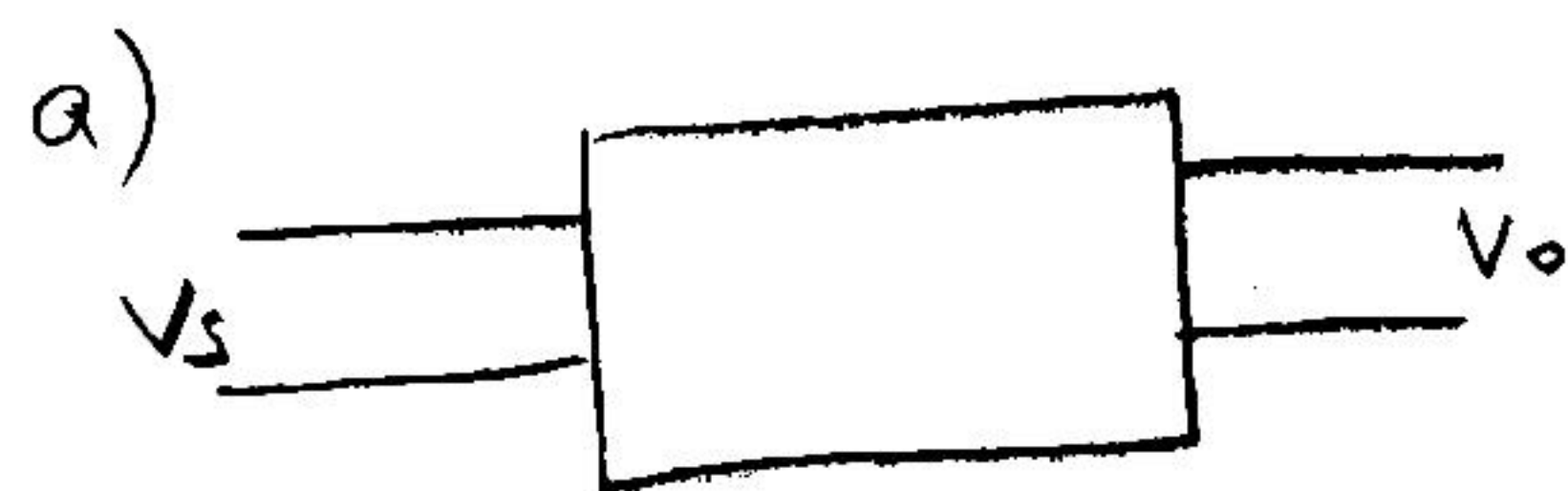



$$H_1(j\omega) = \frac{V_o}{V_s}$$

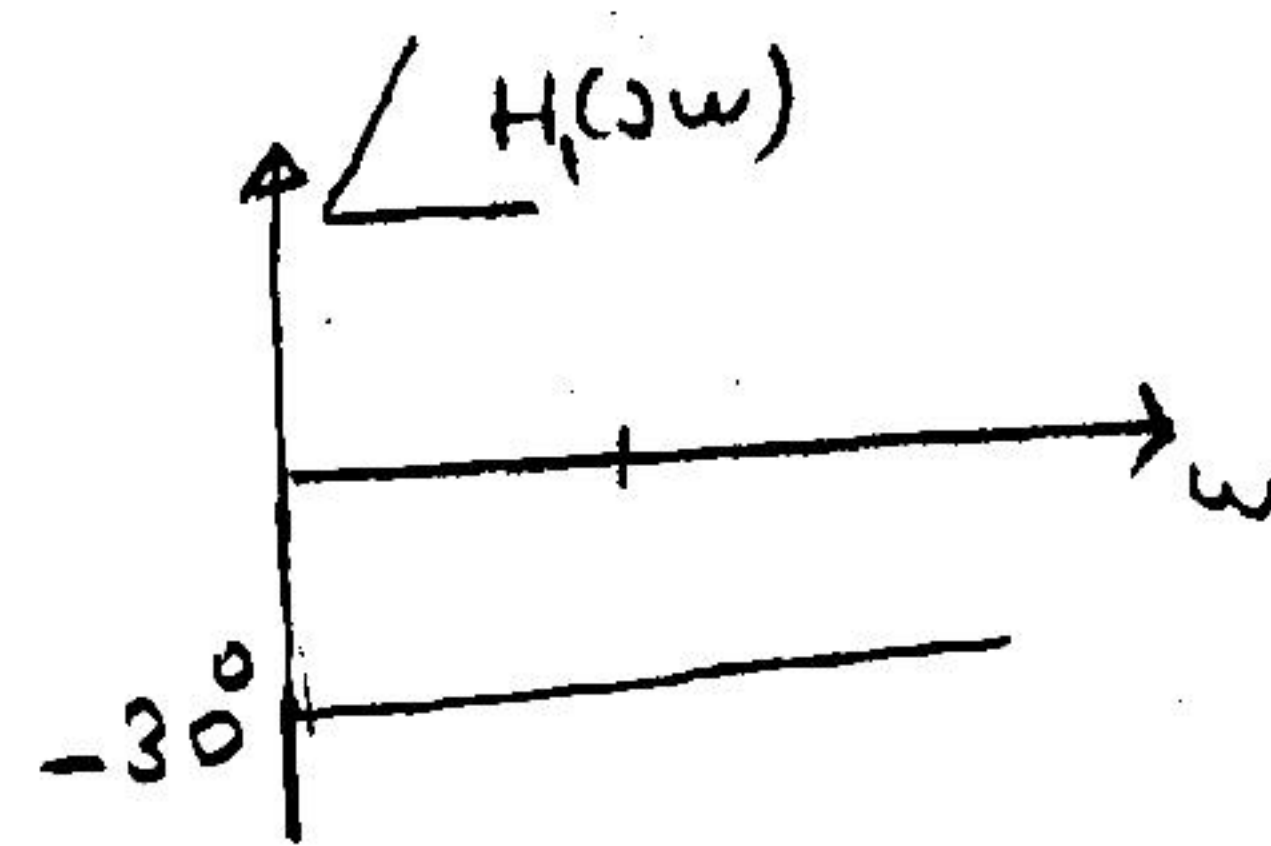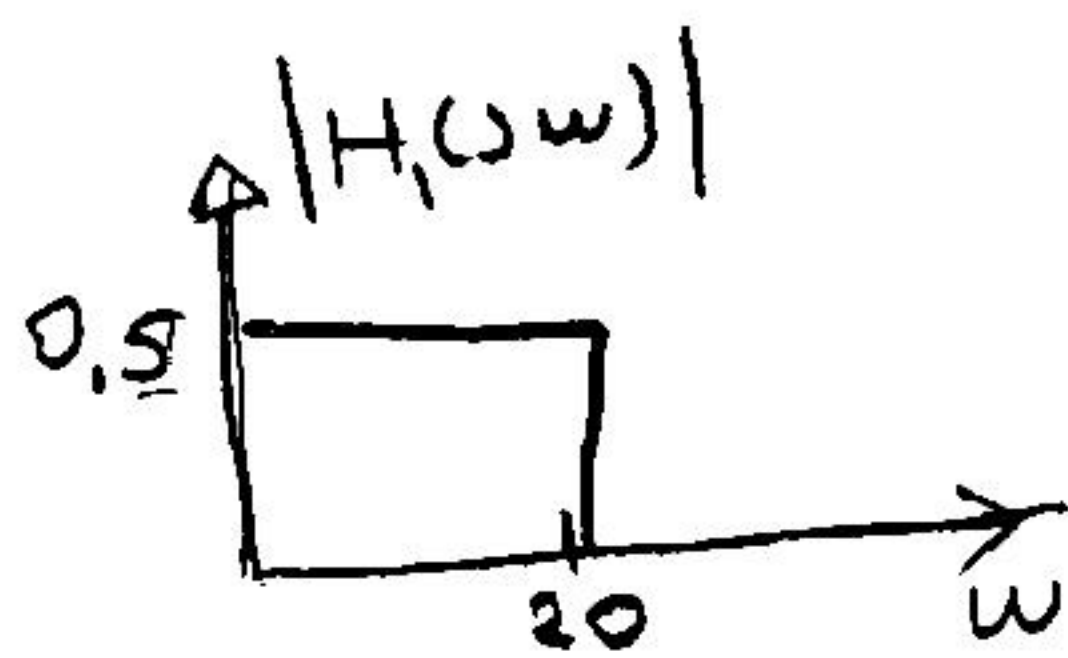


$$V_o = 0.5 \cos(5t + 30) + 0 + 0$$

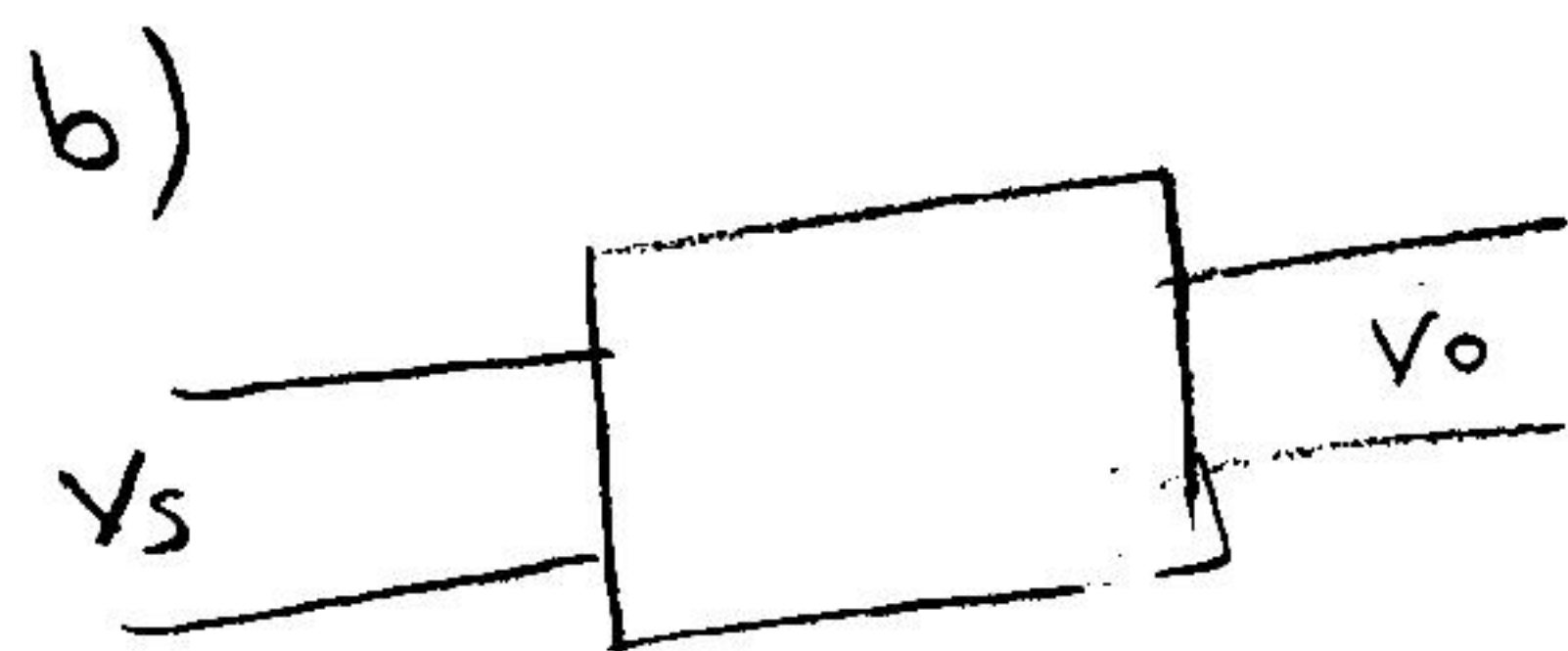



$$H_2(j\omega) = \frac{V_o}{V_s}$$

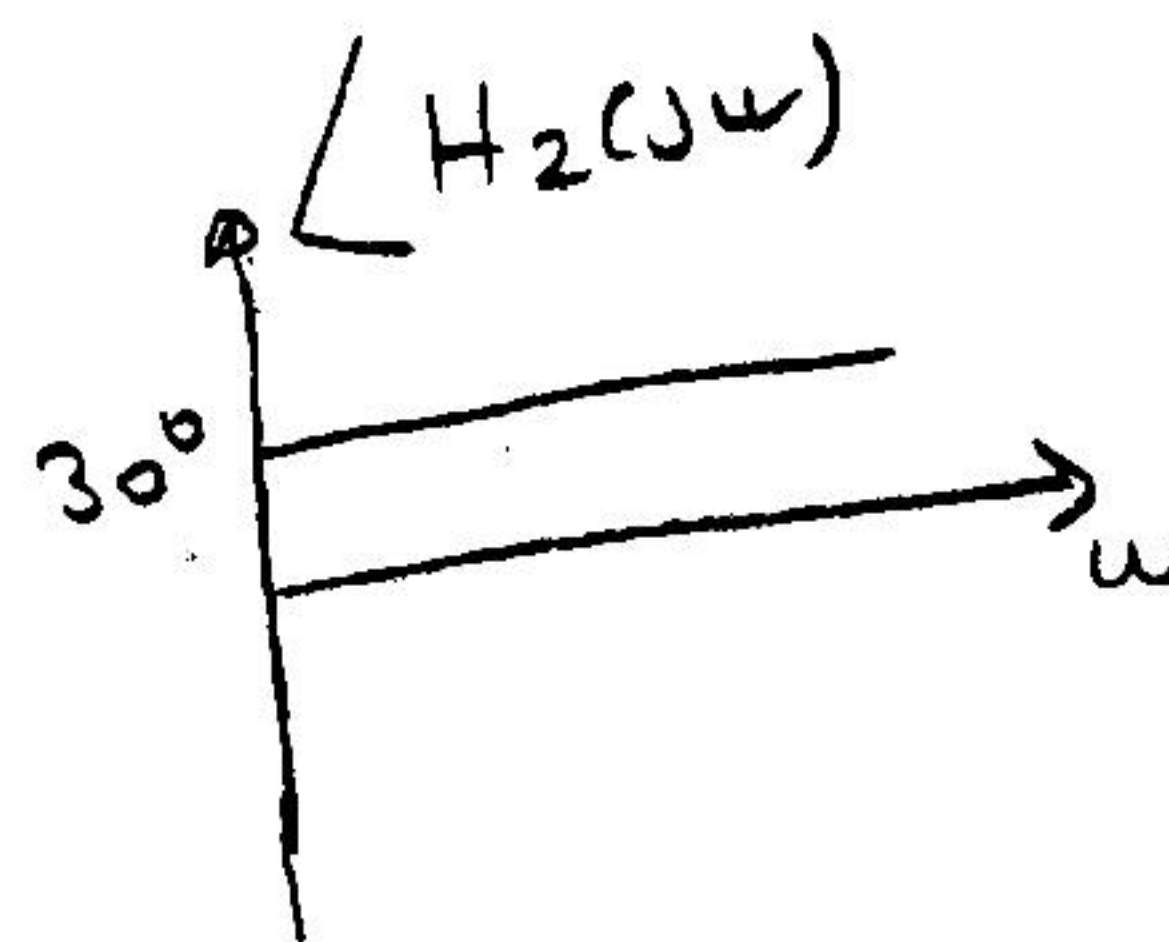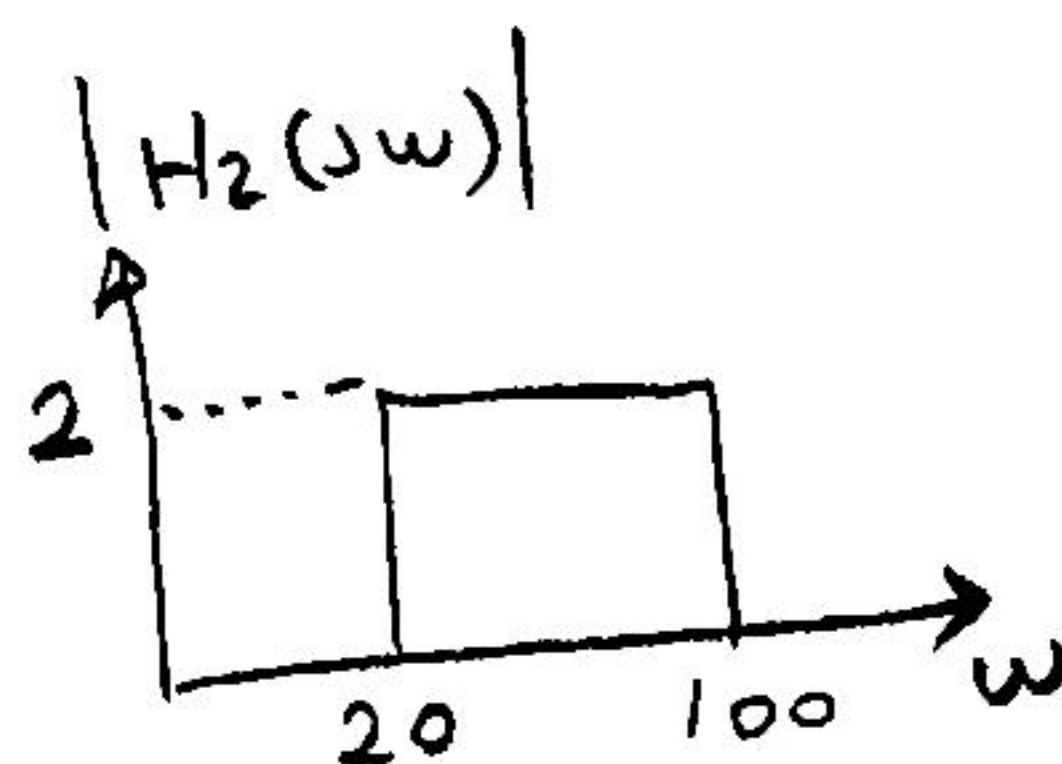


$$V_o = 0 + 2 \cos(50t + 30) + 0$$

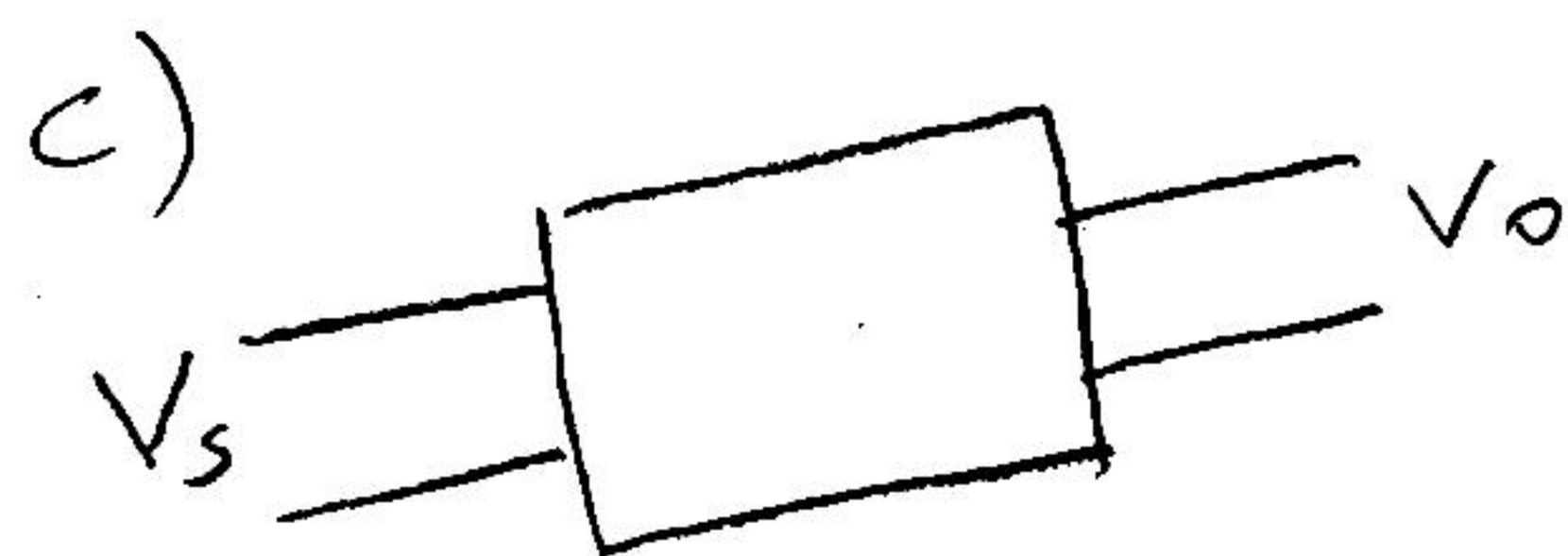

$$H_3(j\omega) = \frac{V_o}{V_s}$$

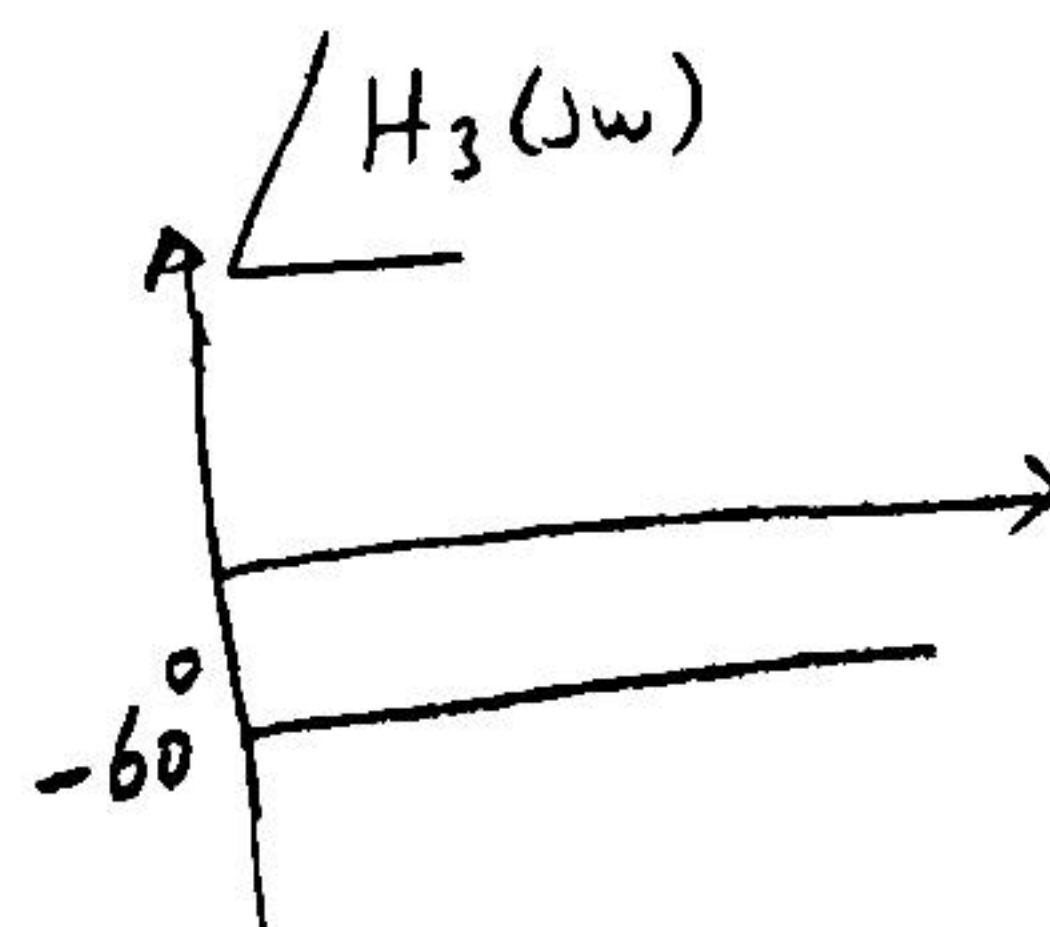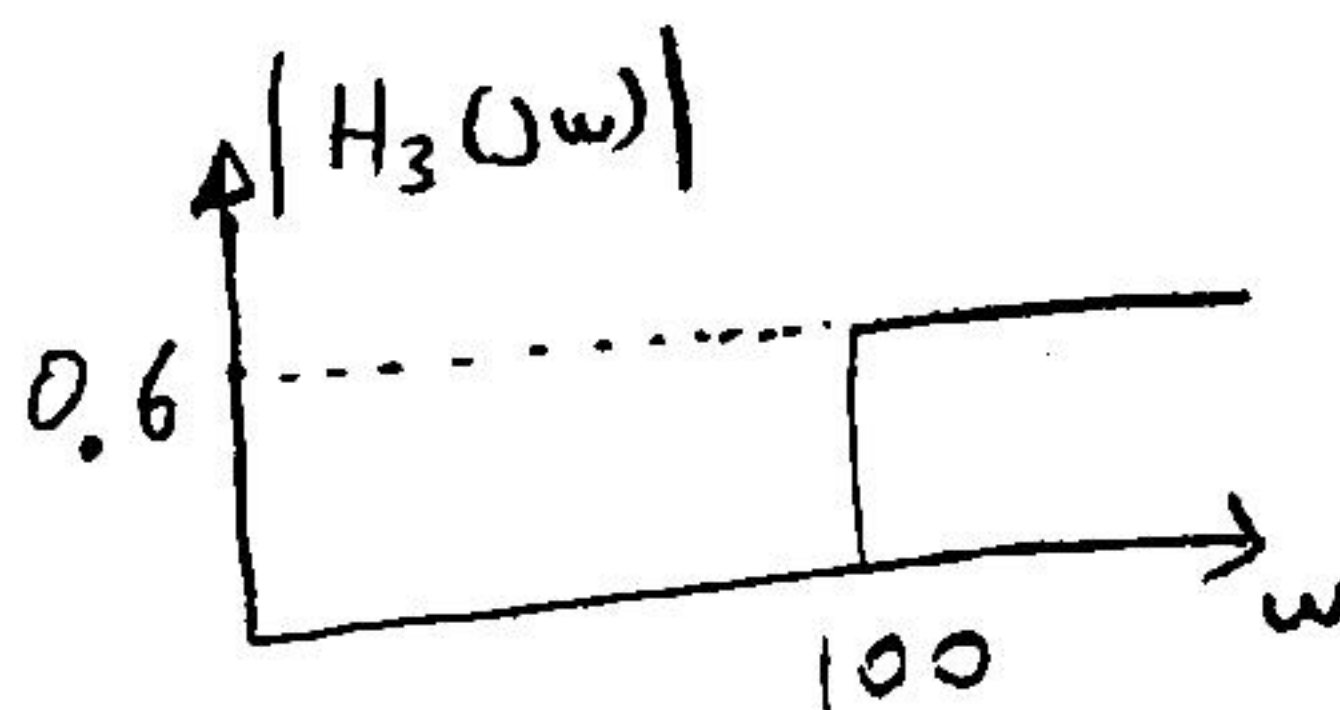

$$V_o = 0 + 0 + 0.6 \cos(500t - 60)$$

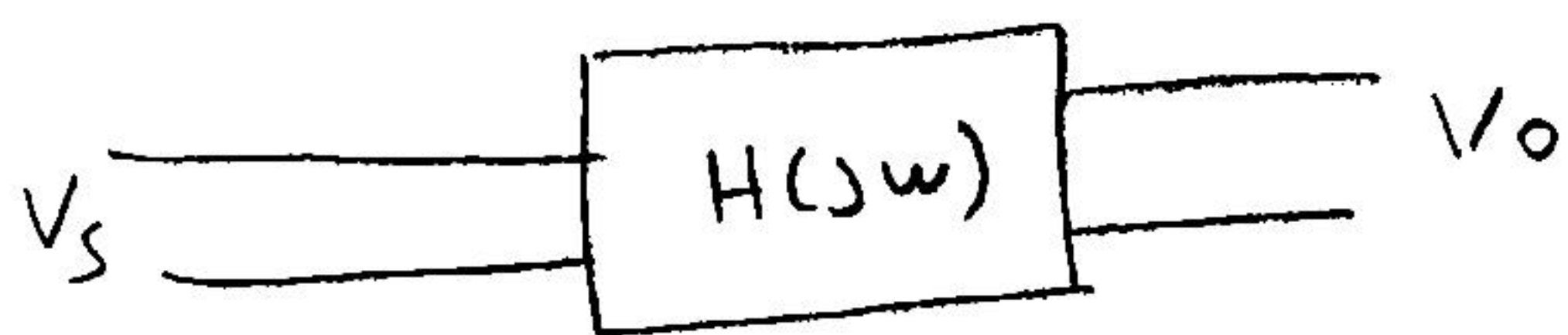


$$H(j\omega) = \frac{V_o}{V_s}$$


E230




ideal low pass filter
amplitude spectrum

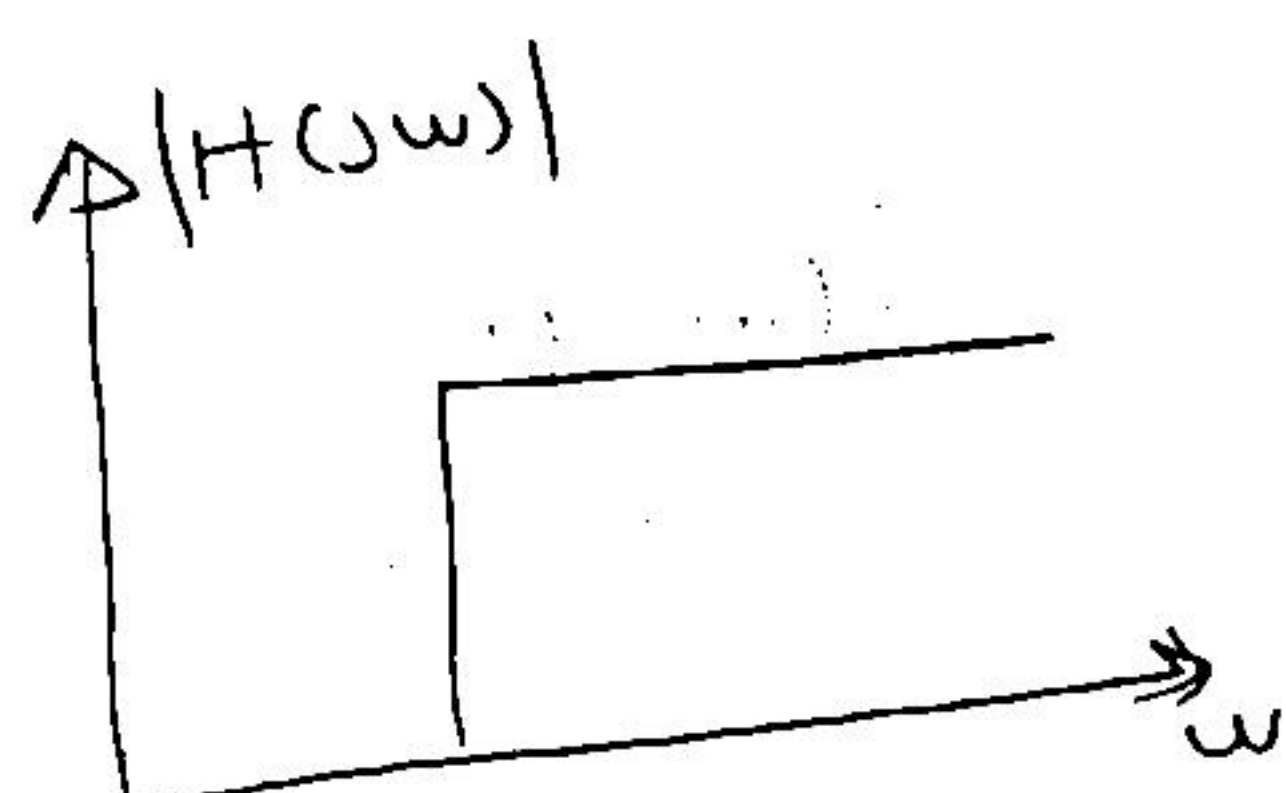

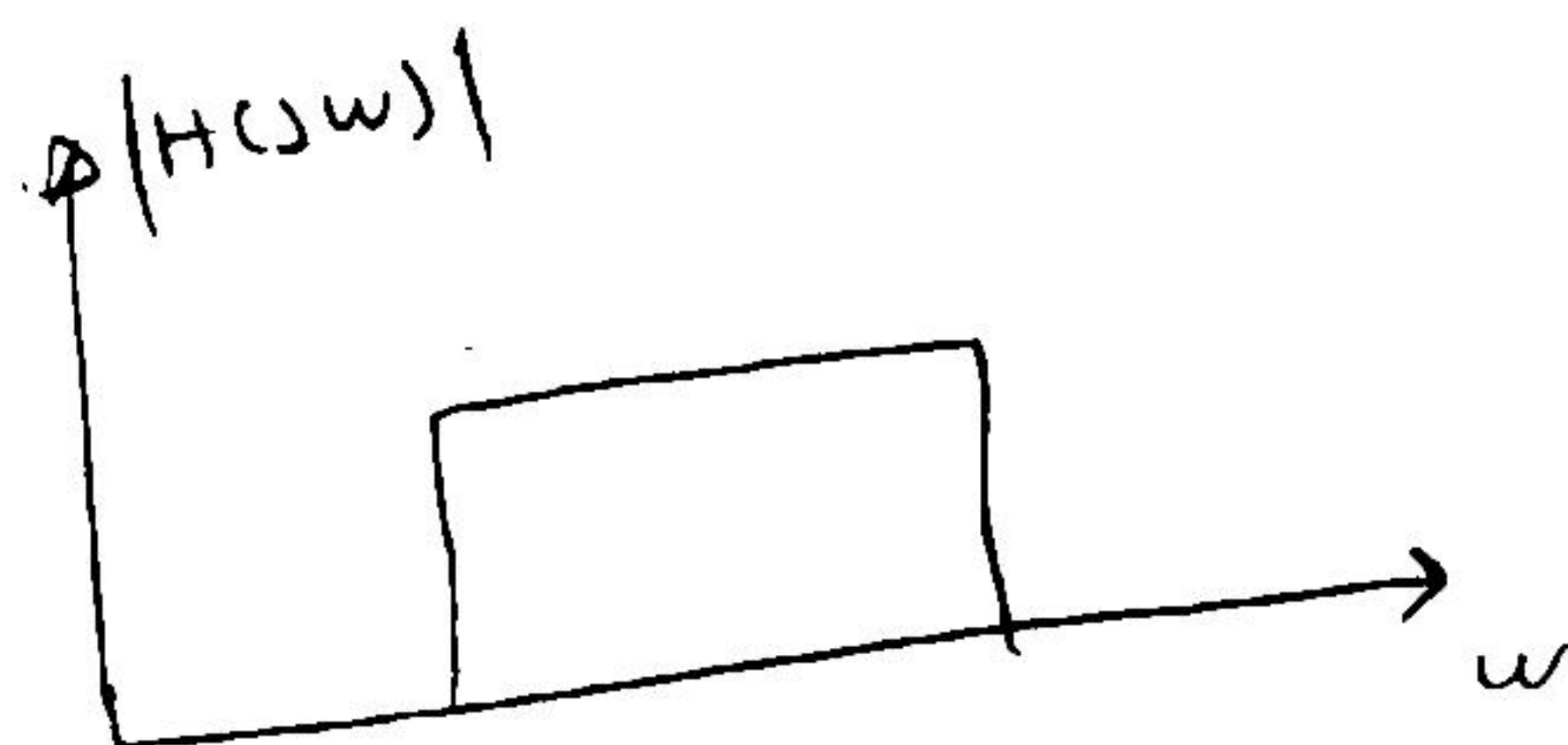
ideal high pass filter
amplitude spectrum



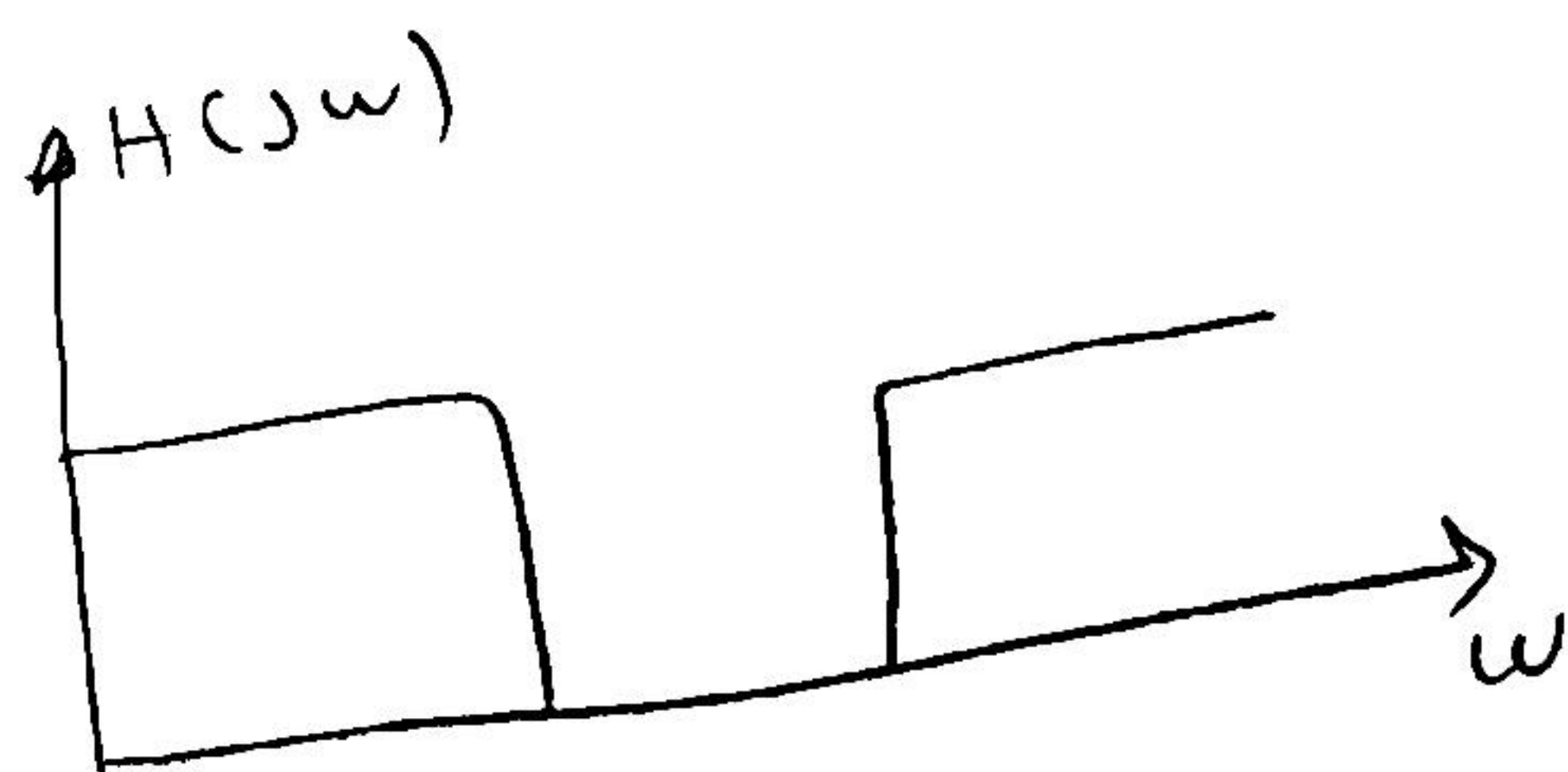
ideal band-pass filter
amplitude spectrum



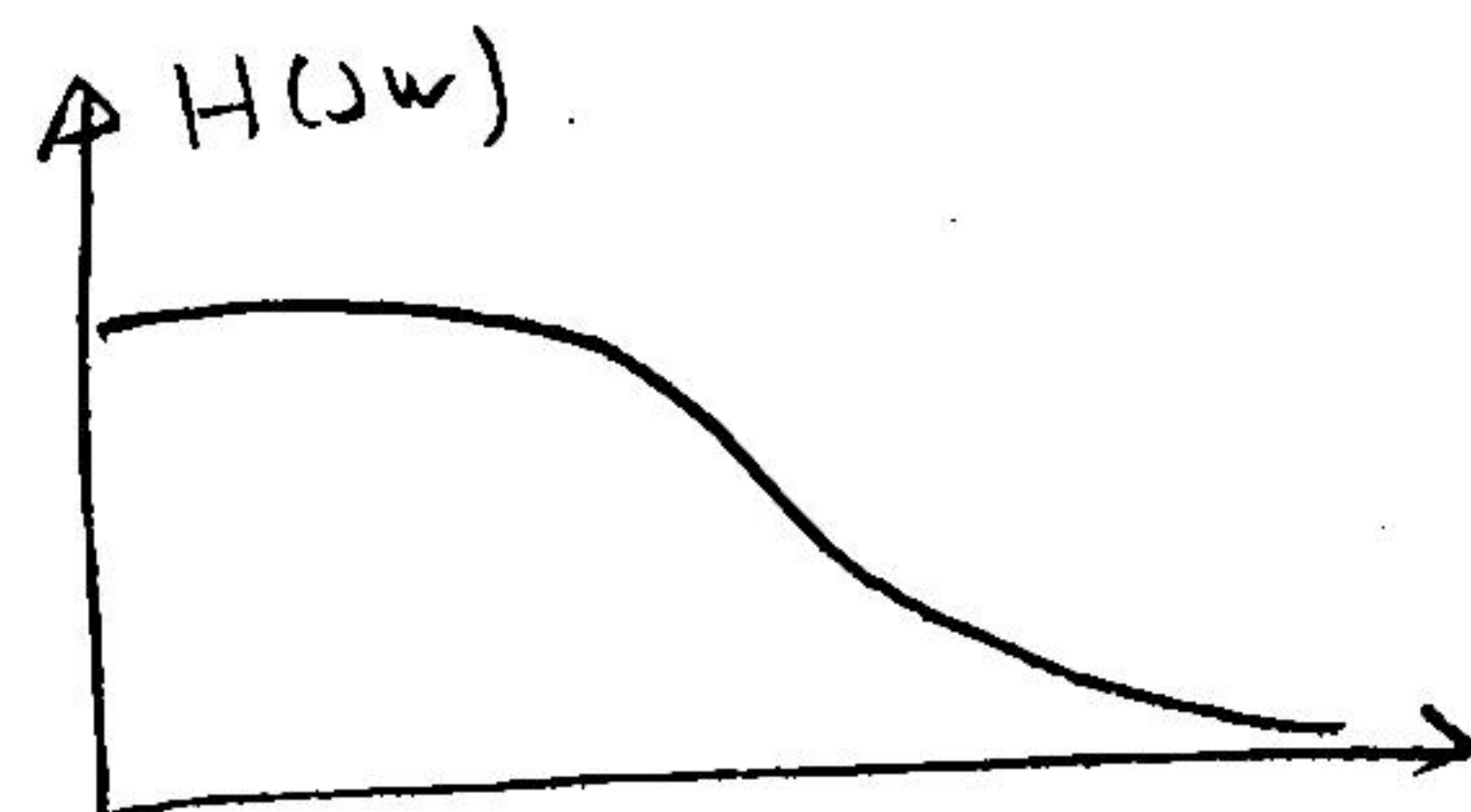
ideal band-stop filter
amplitude spectrum



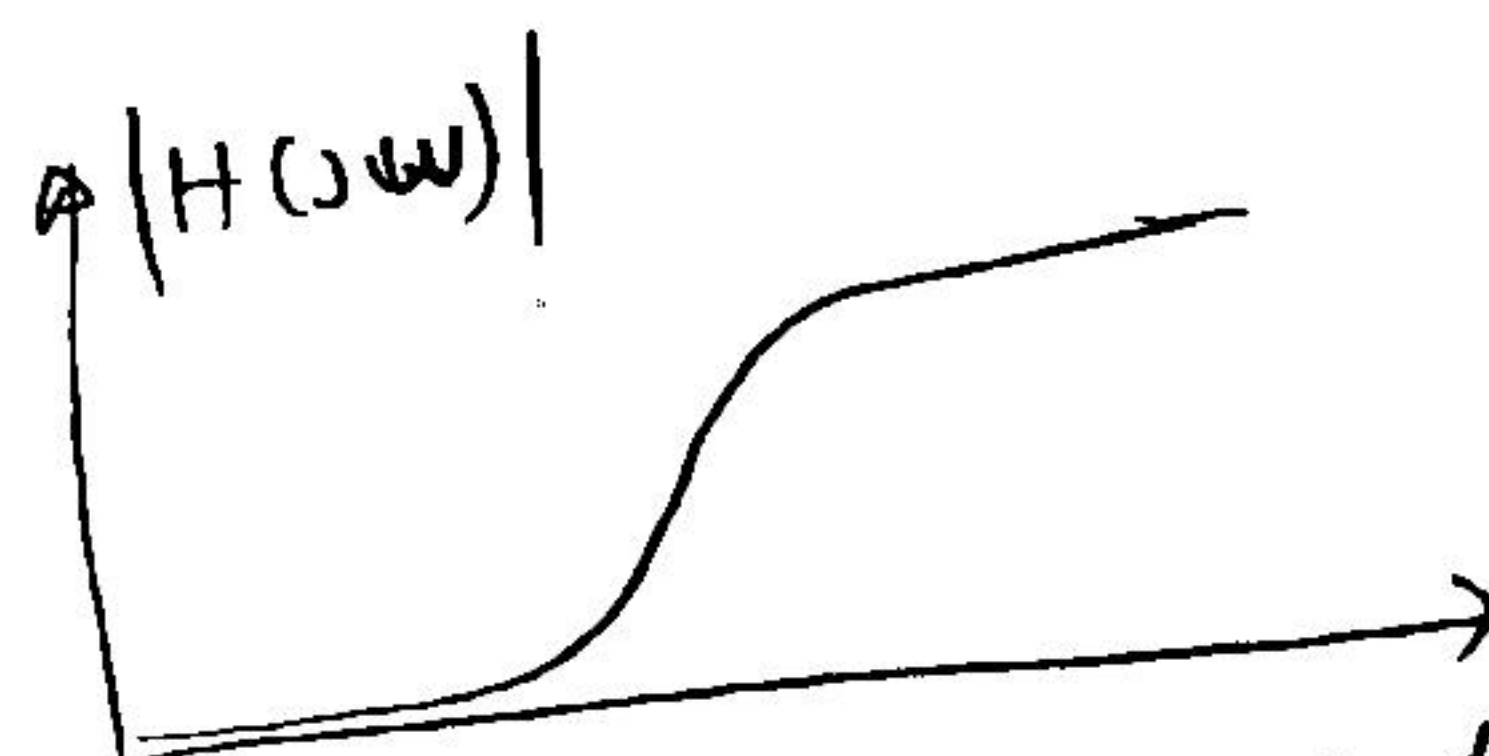
Practical low pass filter
amplitude spectrum



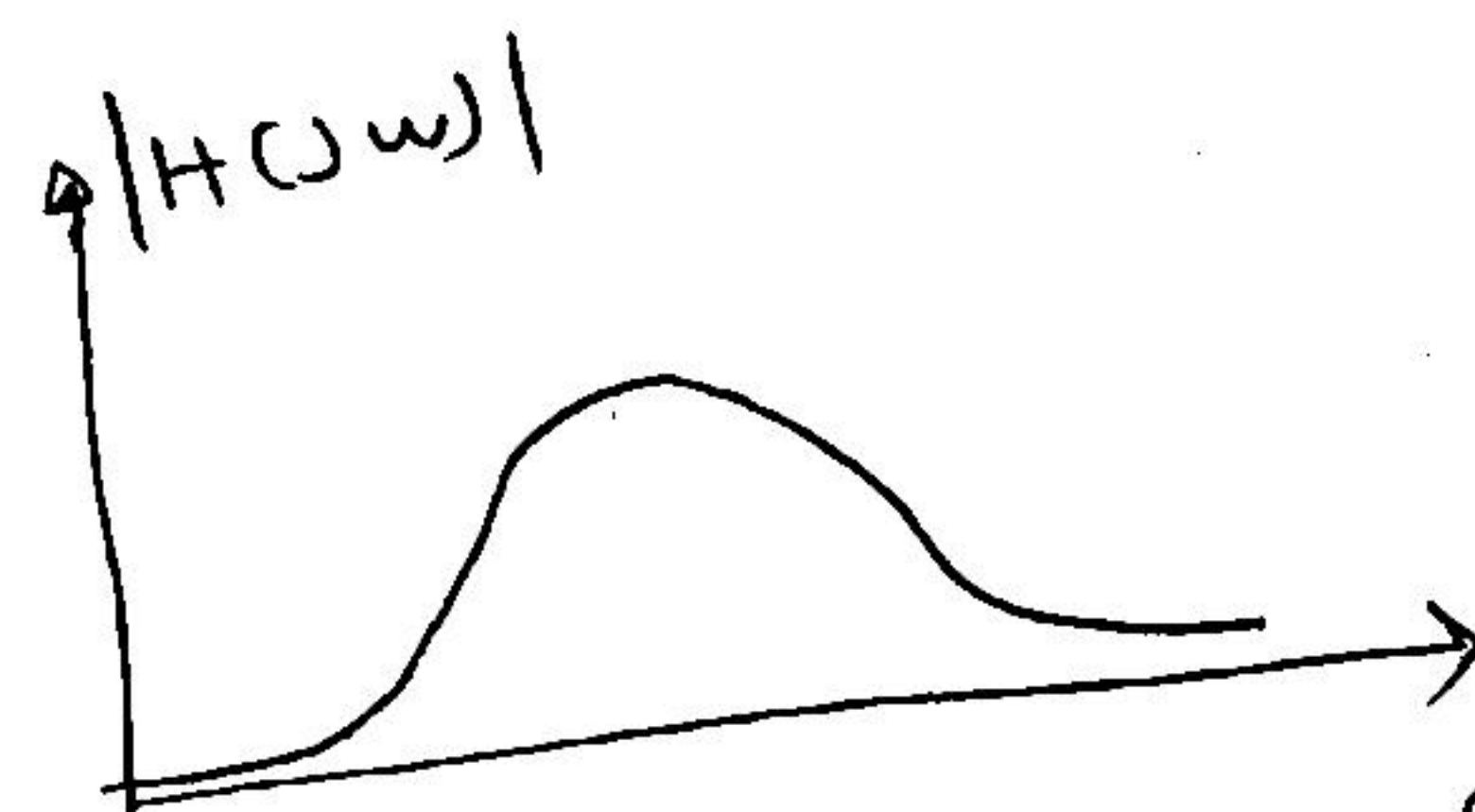Practical high pass filter
amplitude spectrum.




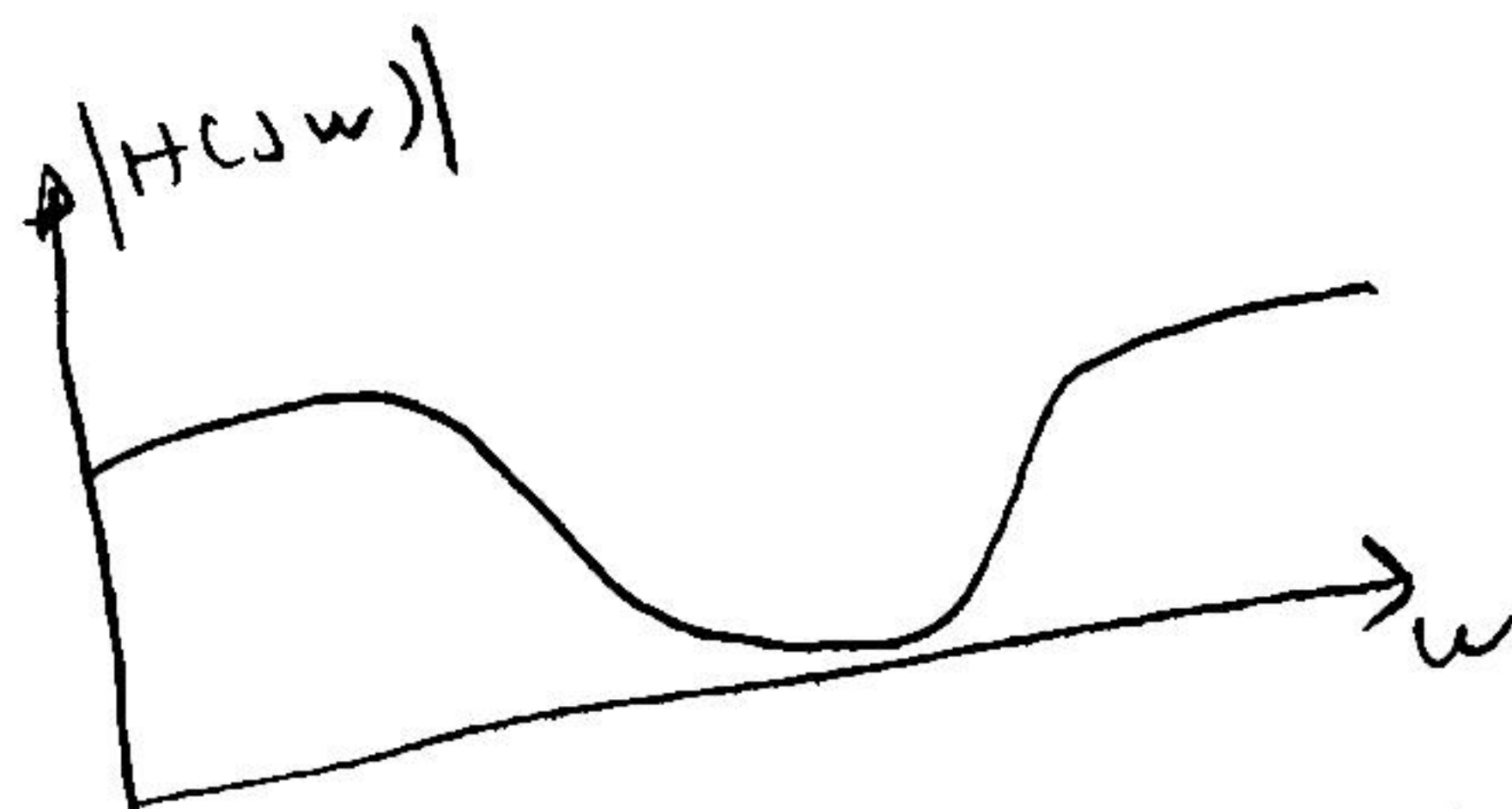
Practical band pass filter
amplitude spectrum




Practical band stop filter
amplitude spectrum.

ideal

e231

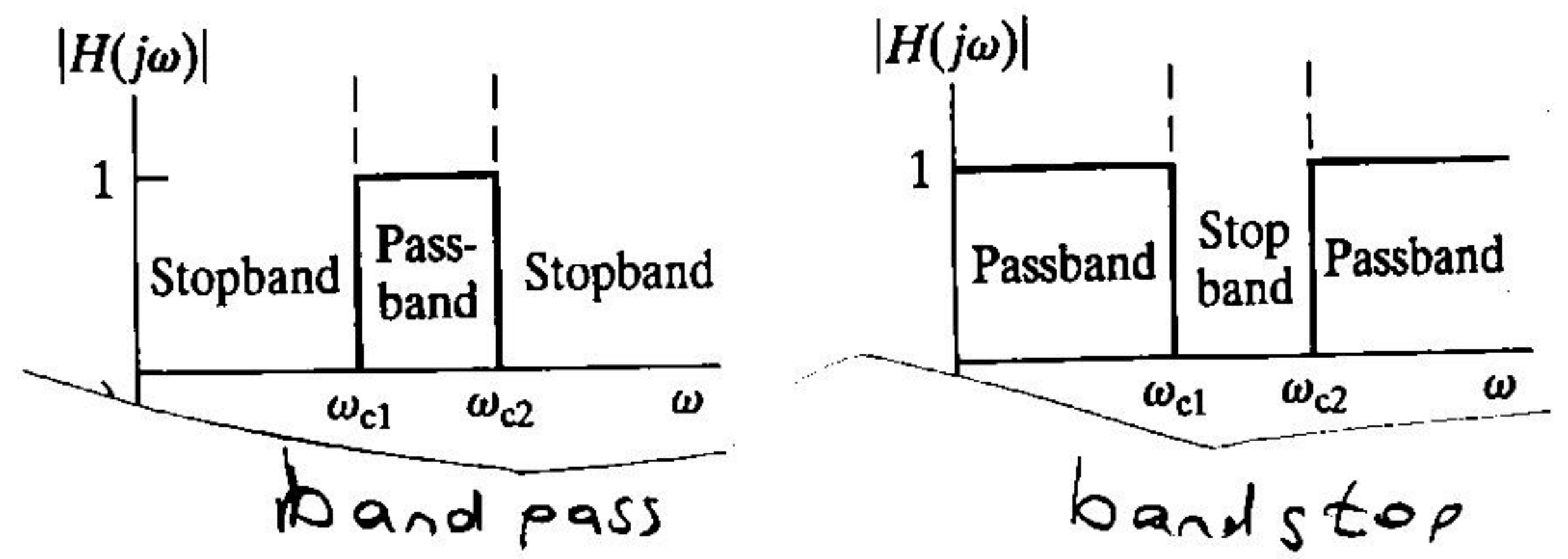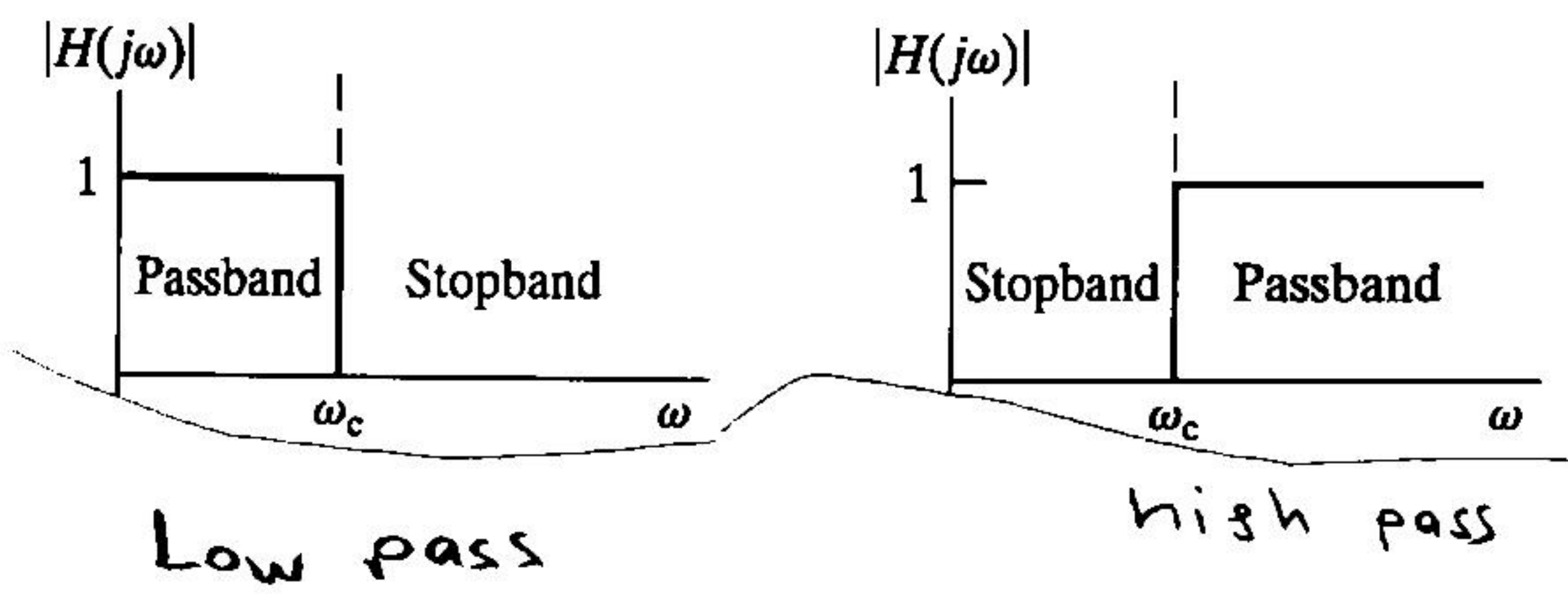

Practical

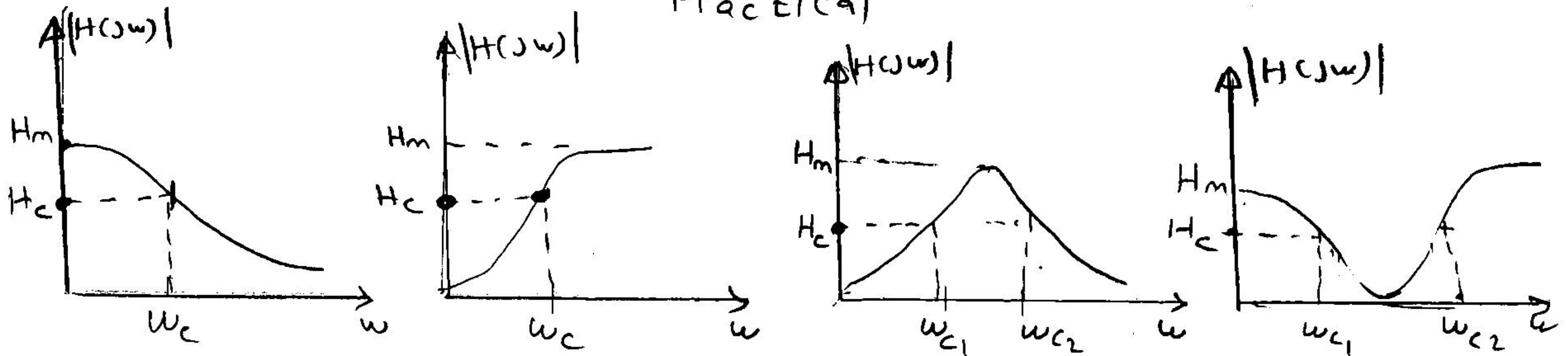

$$H_c = \frac{H_m}{\sqrt{2}}$$


$$H(j\omega_c) = H_c$$

$$H_m = |H(j\omega)|_{\max}$$

ω_c ; Cut off frequency

14.2 ♦ Low-Pass Filters

The Series RL Circuit

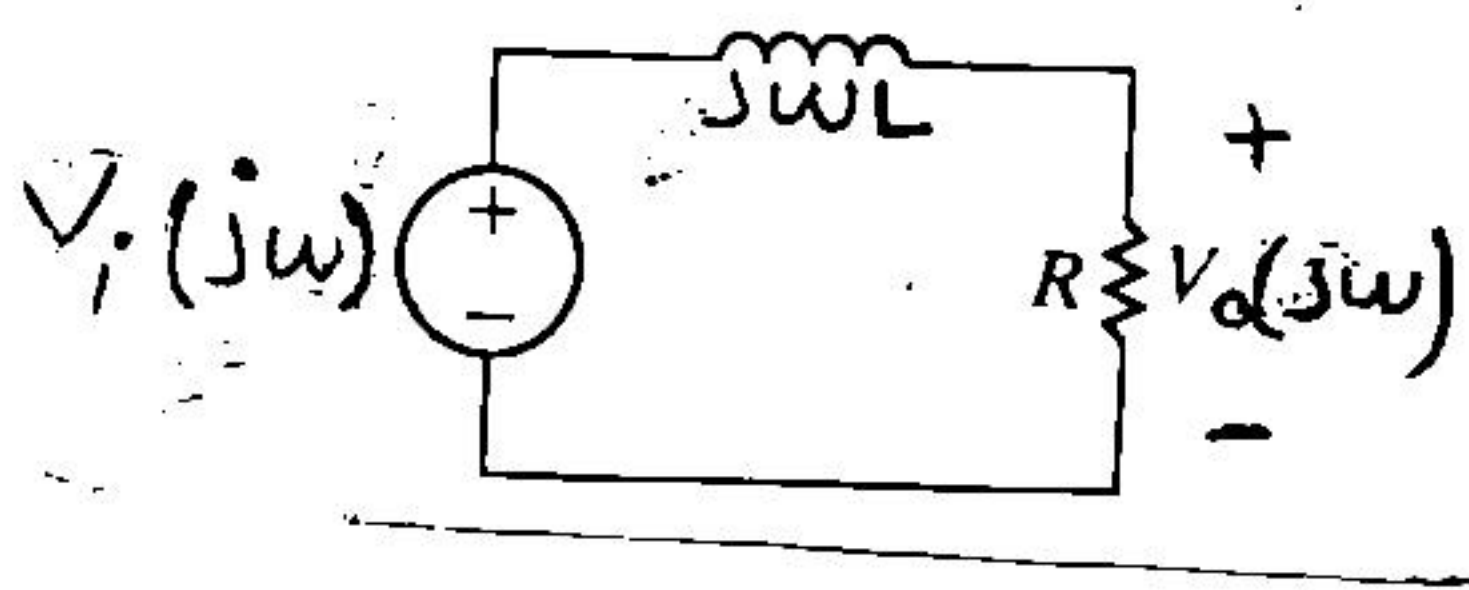

$$V_o(j\omega) = \frac{R}{j\omega L + R} V_i(j\omega)$$

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{R}{j\omega L + R}$$

$$|H(j\omega)| = \frac{R}{\sqrt{(\omega L)^2 + R^2}}$$

$$\theta(j\omega) = -\tan^{-1} \frac{\omega L}{R}$$

at $\omega = 0$ $|H(j\omega)|$ is max

$$H_m = |H(j\omega)|_{\omega=0} = \frac{R}{\sqrt{0^2 + R^2}} = 1$$

at $\omega = \omega_c$ $|H(j\omega)| = \frac{H_m}{\sqrt{2}} = \frac{1}{\sqrt{2}}$

$$\frac{R}{\sqrt{(\omega_c L)^2 + R^2}} = \frac{1}{\sqrt{2}}$$

$$\frac{R^2}{(\omega_c L)^2 + R^2} = \frac{1}{2}$$

$$\frac{R^2}{(\omega_c L)^2 + R^2} = \frac{1}{2}$$

$$2R^2 = \omega_c^2 L^2 + R^2$$

$$2R^2 - R^2 = \omega_c^2 L^2 \quad e232$$

$$R^2 = \omega_c^2 L^2$$

$$\omega_c^2 = \frac{R^2}{L^2}$$

$$\boxed{\omega_c = \frac{R}{L}}$$

EXAMPLE 14.1


Electrocardiology is the study of the electric signals produced by the heart. These signals maintain the heart's rhythmic beat, and they are measured by an instrument called an electrocardiograph. This instrument must be capable of detecting periodic signals whose frequency is about 1 Hz (the normal heart rate is 72 beats per minute). The instrument must operate in the presence of sinusoidal noise consisting of signals from the surrounding electrical environment, whose fundamental frequency is 60 Hz—the frequency at which electric power is supplied.

Choose values for R and L in the circuit of Fig. 14.4(a) such that the resulting circuit could be used in an electrocardiograph to filter out any noise above 10 Hz and pass the electric signals from the heart at or near 1 Hz. Then compute the magnitude of V_o at 1 Hz, 10 Hz, and 60 Hz to see how well the filter performs.

SOLUTION

The problem is to select values for R and L that yield a low-pass filter with a cutoff frequency of 10 Hz. From Eq. 14.12, we see that R and L cannot be specified independently to generate a value for ω_c . Therefore, let's choose a commonly available value of L , 100 mH. Before we use Eq. 14.12 to compute the value of R needed to obtain the desired cutoff frequency, we need to convert the cutoff frequency from hertz to radians per second:
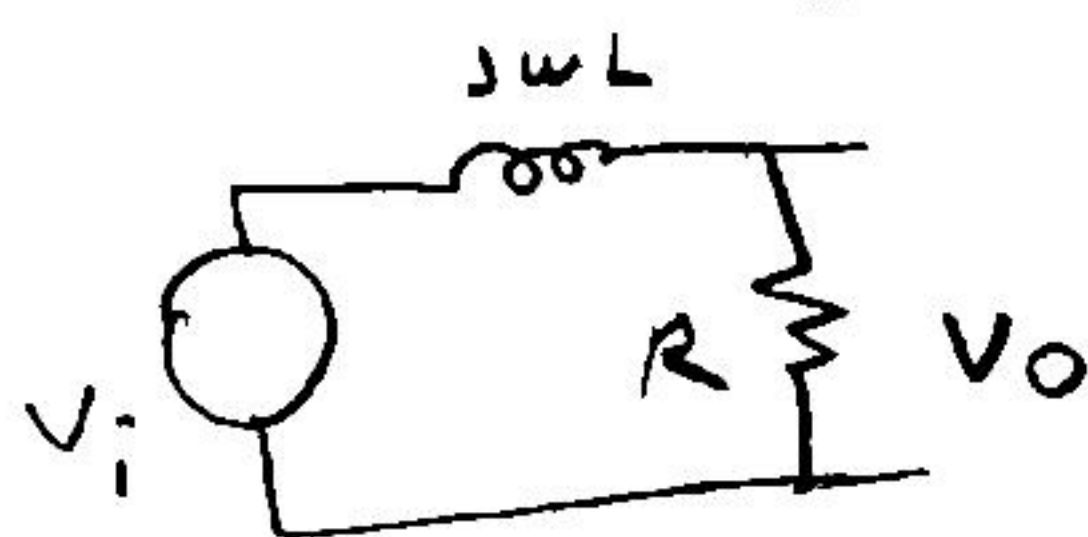
$$\omega_c = 2\pi(10) = 20\pi \text{ rad/s.}$$



$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{R}{j\omega L + R}$$

$$\omega_c = \frac{R}{L} = 20$$

$$L = 100 \text{ mH} = 0.1 \text{ H}$$

$$\frac{R}{L} = 20\pi$$

$$\frac{R}{0.1} = 20\pi \Rightarrow R = 2\pi \Omega = 6.28 \Omega$$

$$|H(j\omega)| = \frac{R}{\sqrt{(\omega L)^2 + R^2}} = \frac{6.28}{\sqrt{(\omega \times 0.1)^2 + 6.28^2}}$$

$$\text{at } f = 1 \quad \omega = 2\pi \quad |H(j2\pi)| = \frac{6.28}{\sqrt{(2\pi \times 0.1)^2 + 6.28^2}} = 0.995$$

$$\text{at } f = 10 \text{ Hz} \quad \omega = 2\pi \times 10 = 20\pi$$


$$|H(j20\pi)| = \frac{6.28}{\sqrt{(20\pi \times 0.1)^2 + 6.28^2}} = 0.707$$

$$\text{at } f = 60 \text{ Hz} \quad \omega = 2\pi \times 60 = 120\pi$$

$$|H(j120\pi)| = \frac{6.28}{\sqrt{(120\pi \times 0.1)^2 + 6.28^2}} = 0.164$$

Assume $|V_i| = 1 \text{ V}$

$f(\text{Hz})$	$ V_i (\text{V})$	$ V_o (\text{V})$
1	1.0	0.995
10	1.0	0.707
60	1.0	0.164

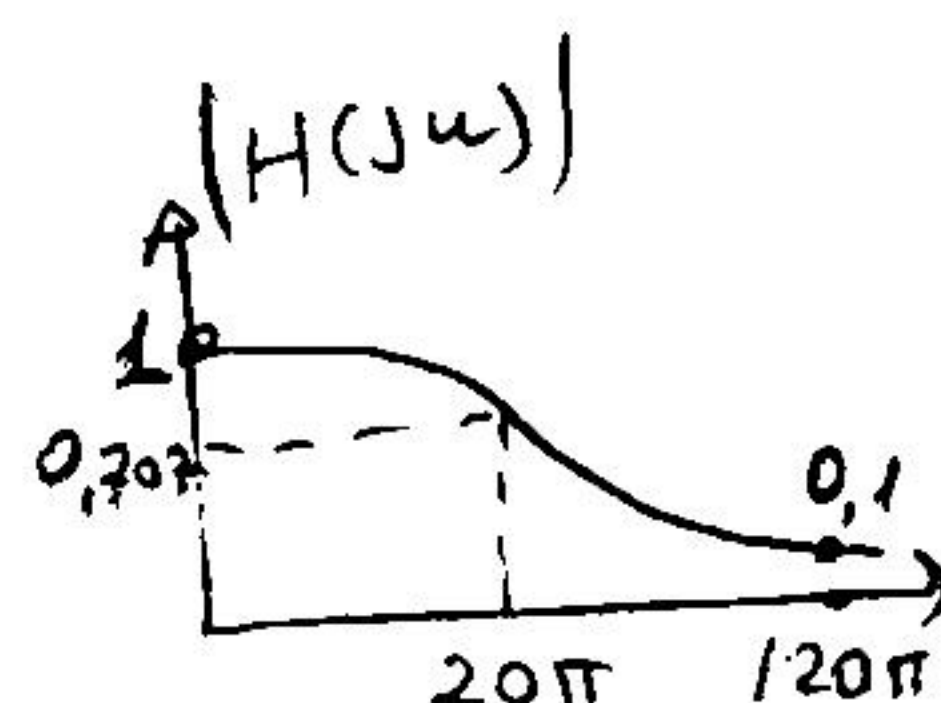

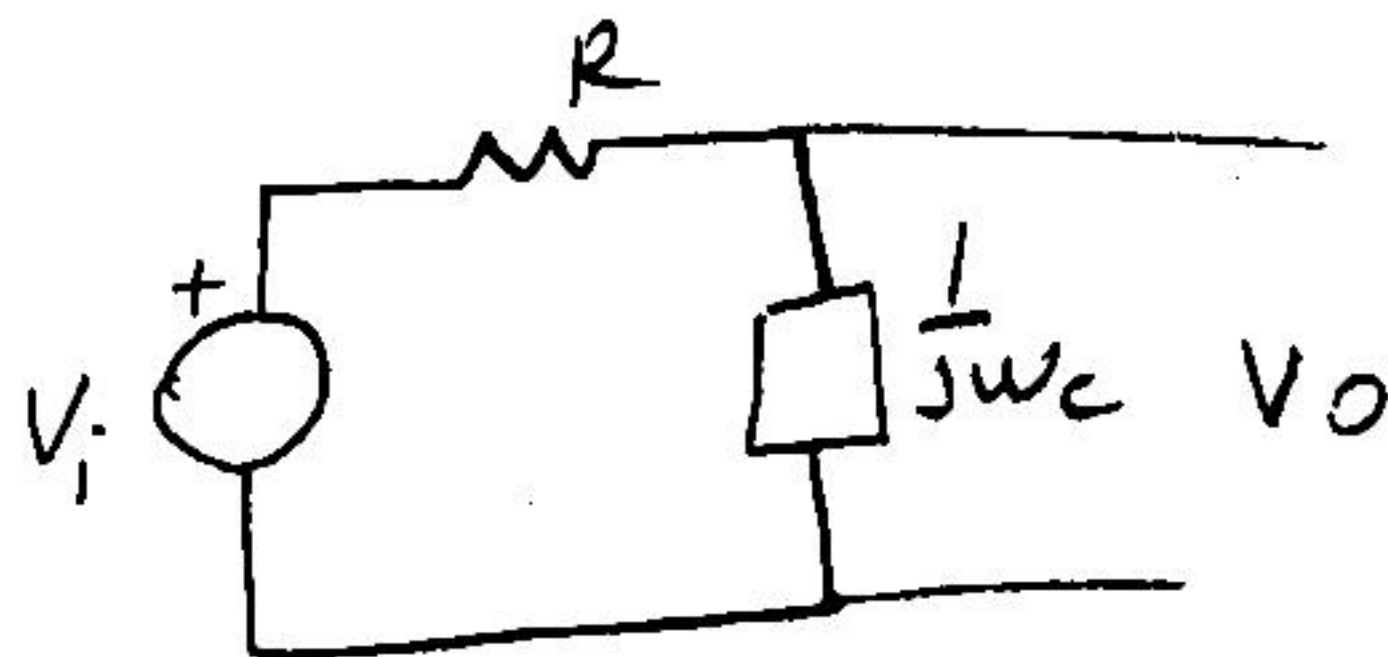
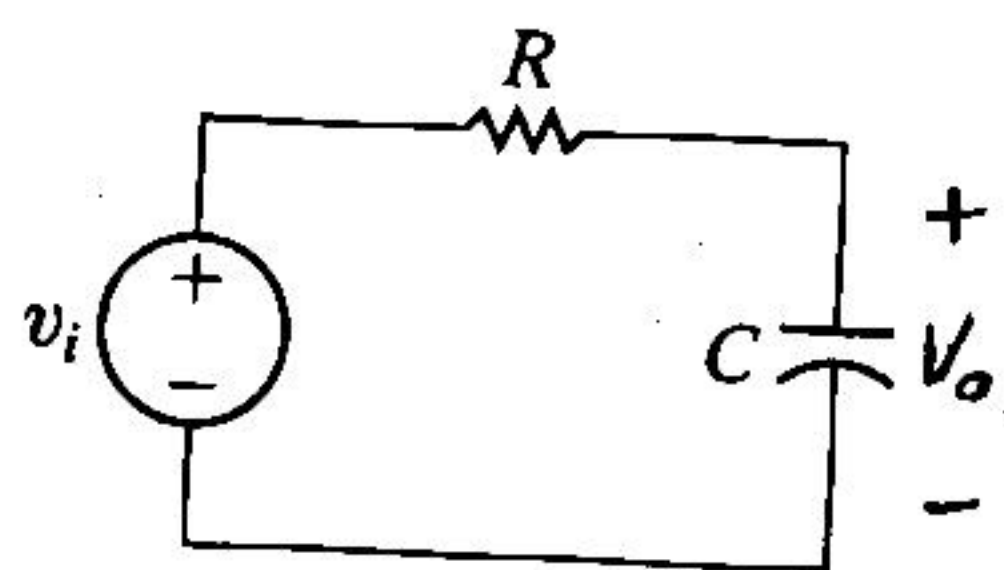


Figure 14.7 A series RC low-pass filter.

$$V_o(j\omega) = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} V_i(j\omega) = \frac{1}{j\omega CR + 1} V_i(j\omega)$$

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{1}{j\omega CR + 1}$$

$$|H(j\omega)| = \frac{1}{\sqrt{(\omega CR)^2 + 1^2}}$$

$$\theta(j\omega) = -\tan^{-1} \frac{\omega CR}{1}$$

at $\omega = 0$ $|H(j\omega)|$ is maximum

$$|H(j\omega)|_{\max} = \frac{1}{\sqrt{0^2 + 1^2}} = 1$$

at $\omega = \omega_c$ $|H(j\omega_c)| = \frac{1}{\sqrt{2}}$

$$\frac{1}{\sqrt{(\omega_c CR)^2 + 1^2}} = \frac{1}{\sqrt{2}} \Rightarrow \frac{1}{(\omega_c CR)^2 + 1^2} = \frac{1}{2}$$

$$(\omega_c CR)^2 + 1^2 = 2$$


$$(\omega_c CR)^2 = 1$$

$$\boxed{\omega_c = \frac{1}{RC}}$$

EXAMPLE 14.2

e239

For the series RC circuit in Fig. 14.7:

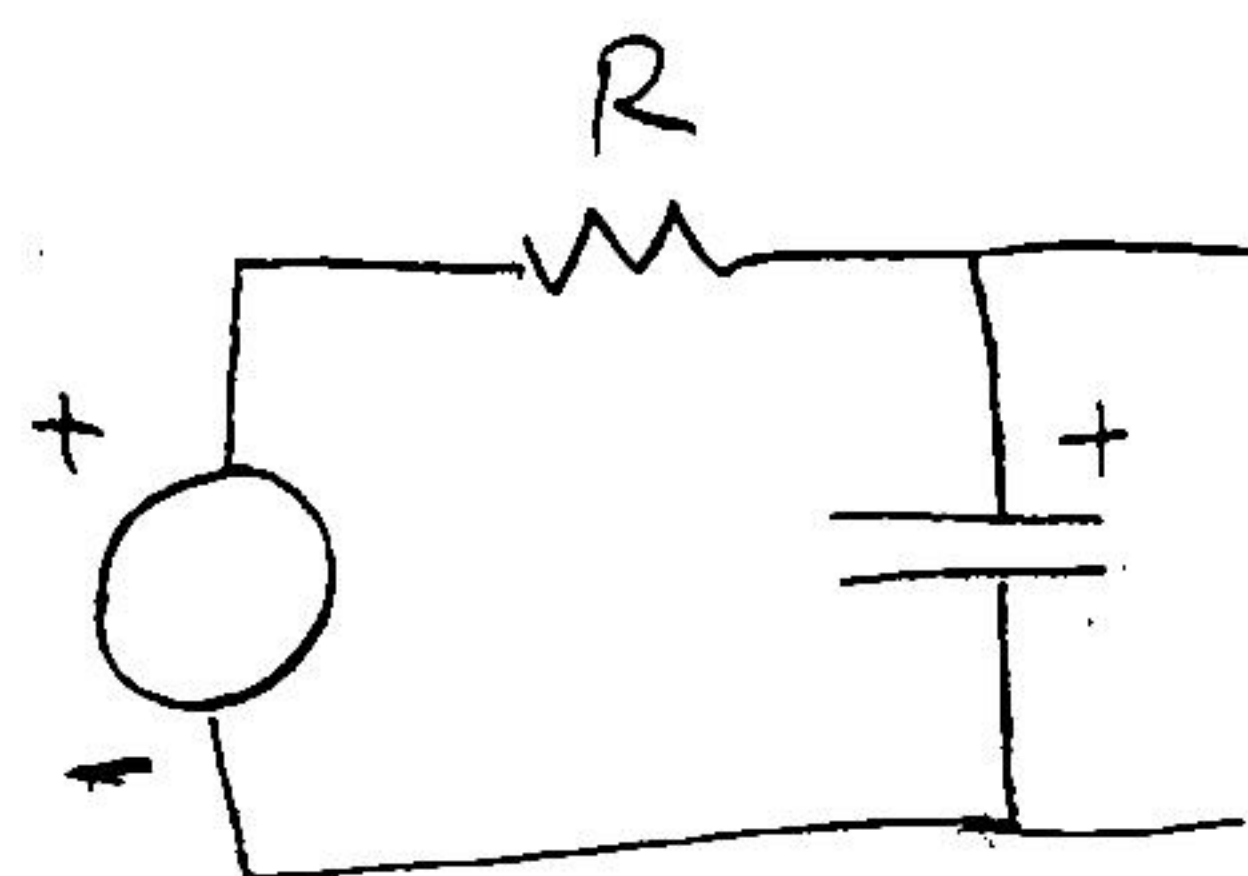


- Find the transfer function between the source voltage and the output voltage.
- Determine an equation for the cutoff frequency in the series RC circuit.
- Choose values for R and C that will yield a low-pass filter with a cutoff frequency of 3 kHz.

a, b, c in previous page

Because R and C cannot be computed independently, let's choose $C = 1 \mu\text{F}$.


$$\omega_c = \frac{1}{RC}$$
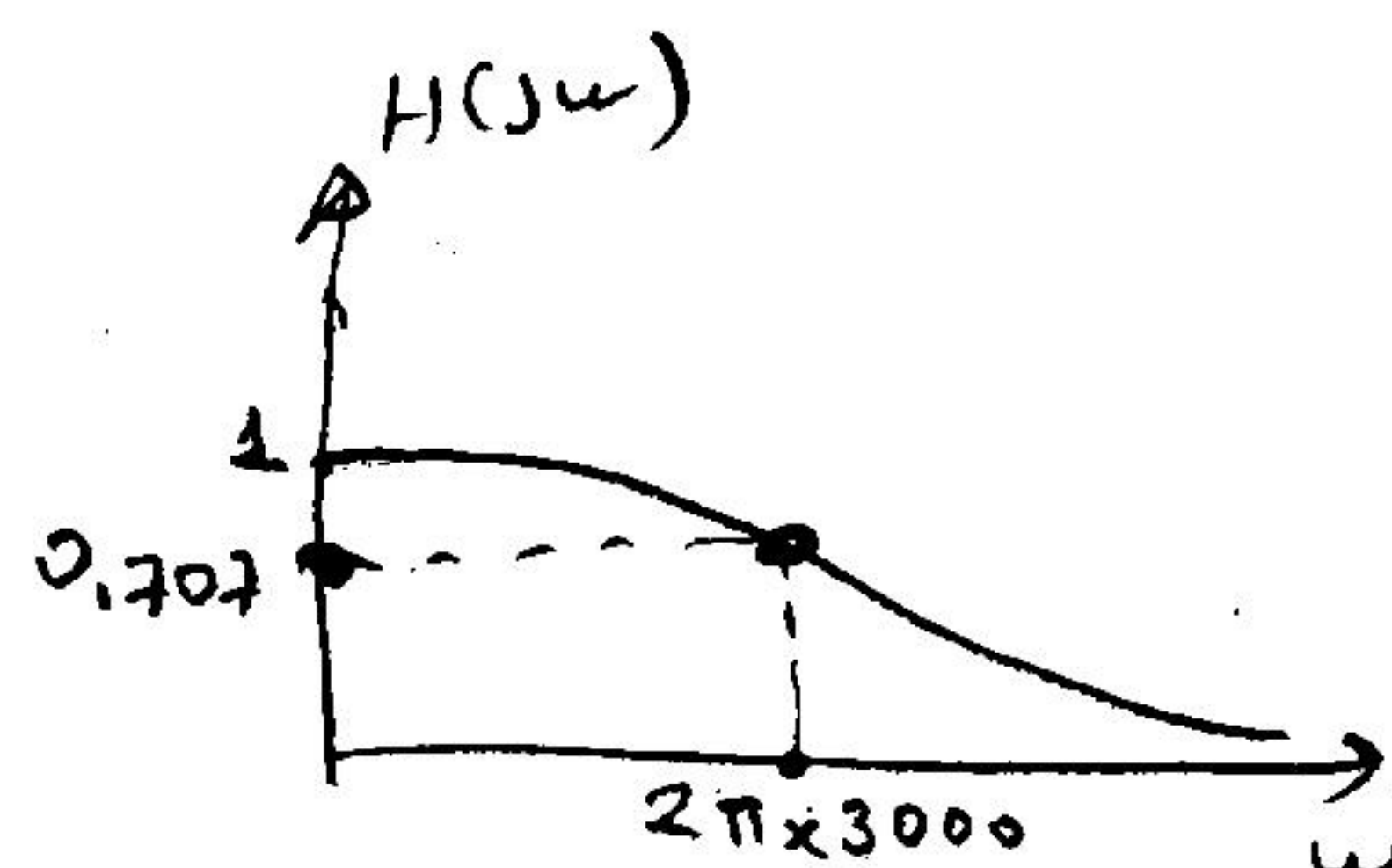
$$\begin{aligned} R &= \frac{1}{\omega_c C} \\ &= \frac{1}{(2\pi)(3 \times 10^3)(1 \times 10^{-6})} \\ &= 53.05 \Omega. \end{aligned}$$



HIGH PASS FILTERS

The Series RC Circuit—

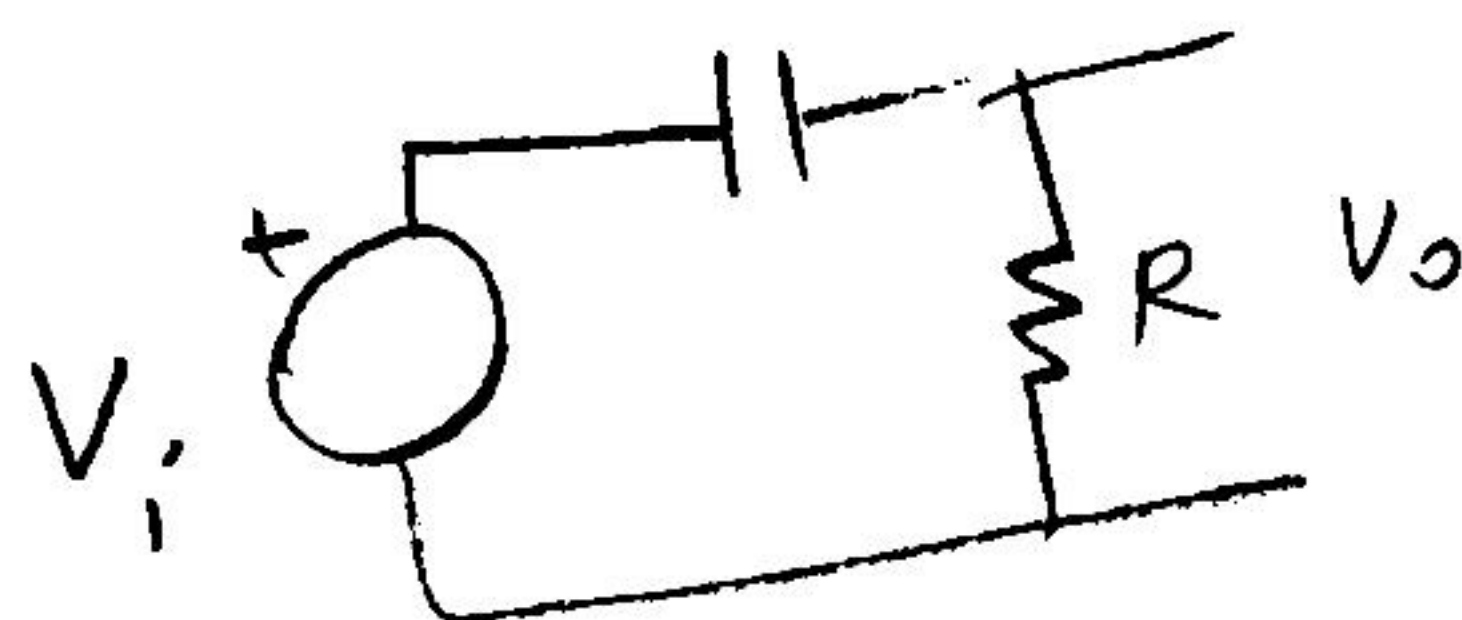

$$V_o = \frac{R}{R + \frac{1}{j\omega C}} V_i(j\omega) = \frac{j\omega CR}{j\omega CR + 1} V_i(j\omega)$$

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{j\omega CR}{j\omega CR + 1}$$

$$|H(j\omega)| = \frac{\omega CR}{\sqrt{(\omega CR)^2 + 1}}$$

$$\theta(j\omega) = 90^\circ - \tan^{-1} \frac{\omega CR}{1}$$

at $\omega = \infty$ $|H(j\omega)|$ is maximum

$$H(j\infty) = \lim_{\omega \rightarrow \infty} \frac{\omega CR}{\sqrt{(\omega CR)^2 + 1}} = 1$$

$$\text{at } \omega = \omega_c \quad |H(j\omega_c)| = \frac{1}{\sqrt{2}}$$

e235


$$\frac{\omega_c R}{\sqrt{(\omega_c R)^2 + 1}} = \frac{1}{\sqrt{2}}$$

$$\frac{(\omega_c R)^2}{(\omega_c R)^2 + 1} = \frac{1}{2}$$

$$2(\omega_c R)^2 = (\omega_c R)^2 + 1$$

$$(\omega_c R)^2 = 1 \quad \omega_c R = 1$$

$$\boxed{\omega_c = \frac{1}{RC}}$$

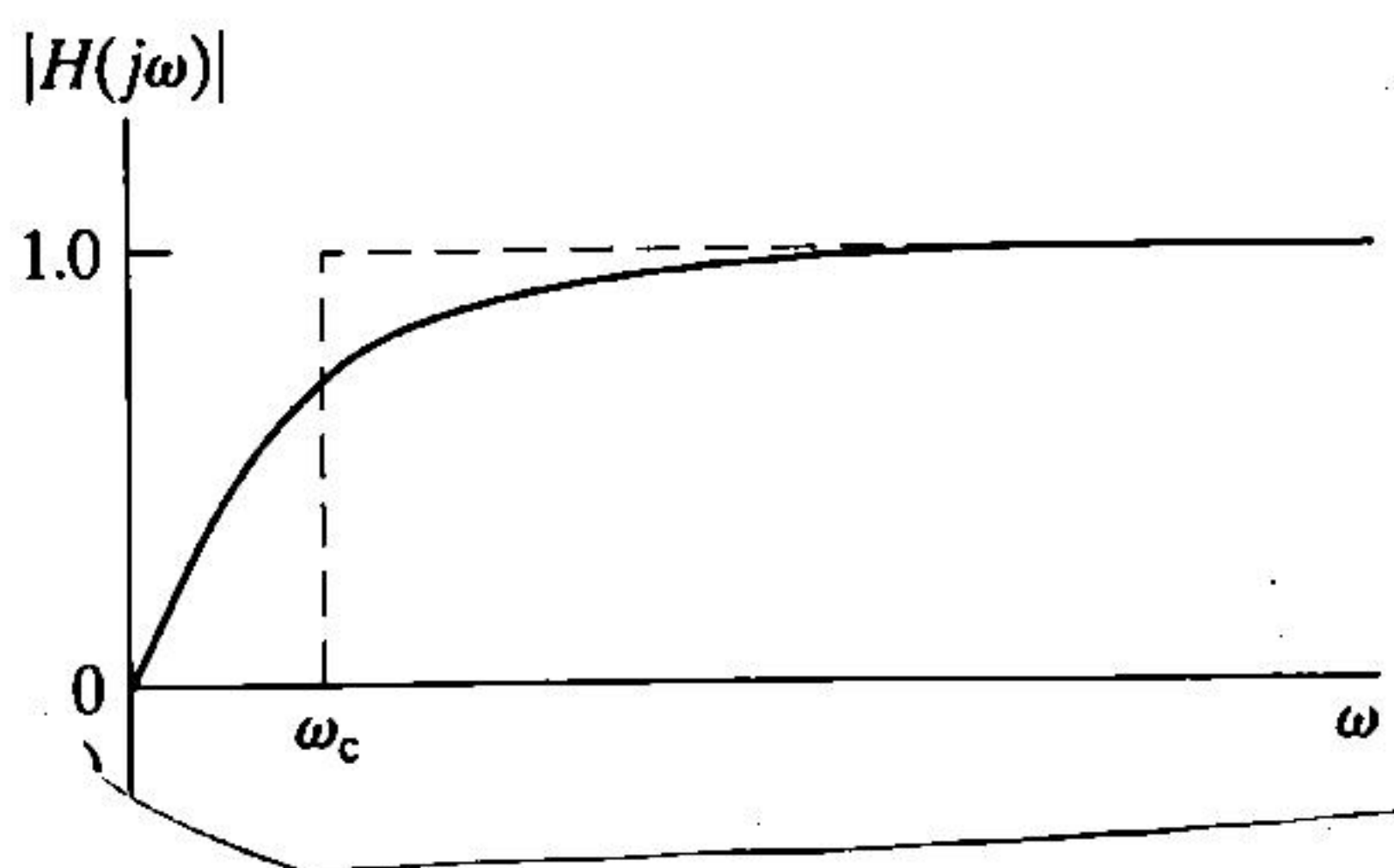

$$RC = 1$$

ω	$ H(j\omega) $
0	0
0.5	0.44
1	0.707
10	0.985
100	0.999995
∞	1

EXAMPLE 14.3

Show that the series RL circuit in Fig. 14.13 also acts like a high-pass filter:

- Derive an expression for the circuit's transfer function.
- Use the result from (a) to determine an equation for the cutoff frequency in the series RL circuit.
- Choose values for R and L that will yield a high-pass filter with a cutoff frequency of 15 kHz.

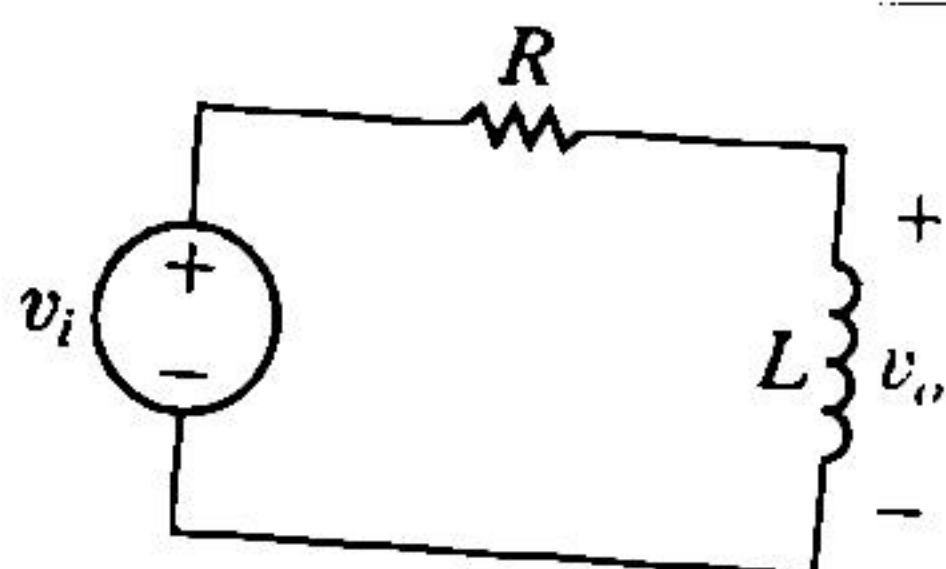


Figure 14.13 The circuit for Example 14.3.

Solution



$$V_o = \frac{j\omega L}{j\omega L + R} V_i$$

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{j\omega L}{j\omega L + R}$$

$$b) \quad |H(j\omega)| = \frac{\omega L}{\sqrt{(\omega L)^2 + R^2}}$$

$$\text{at } \omega = 0 \quad |H(j0)| = \frac{0 \times L}{R} = 0$$

$$\text{at } \omega = \infty \quad |H(j\infty)| = 1$$

$$\text{at } \omega = \omega_c \quad |H(j\omega_c)| = \frac{1}{\sqrt{2}}$$


$$\frac{1}{\sqrt{2}} = \frac{\omega_c L}{\sqrt{(\omega_c L)^2 + R^2}} \Rightarrow \frac{1}{2} = \frac{(\omega_c L)^2}{(\omega_c L)^2 + R^2}$$

$$(\omega_c L)^2 + R^2 = 2(\omega_c L)^2$$

$$R^2 = (\omega_c L)^2 \Rightarrow \boxed{\omega_c = \frac{R}{L}}$$

$$c) \quad L = 0.1 \text{ H (arbitrary)}$$

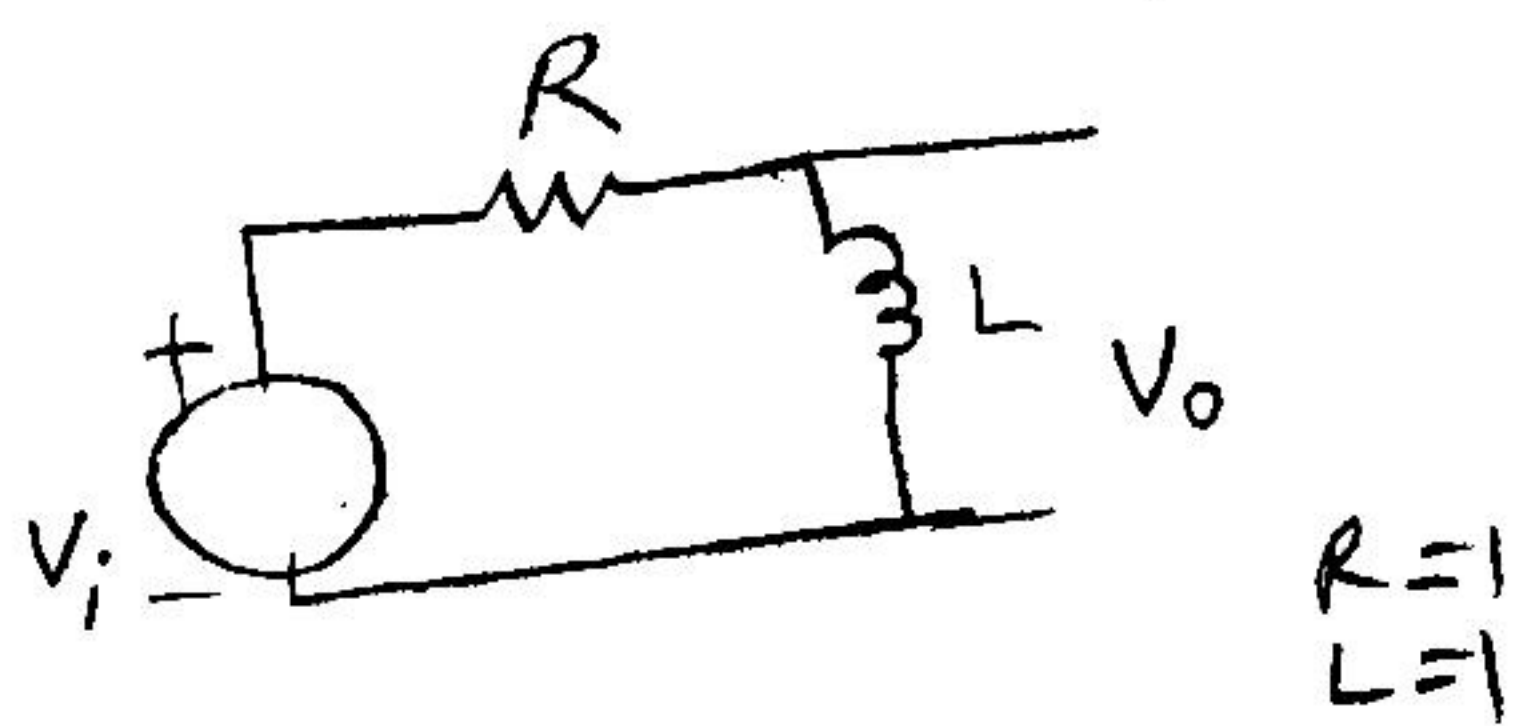
$$R = \omega_c L = 2\pi 15000 \cdot 0.1 = 9424 \, \Omega$$



$$|H(j\omega)| = \frac{\omega L}{\sqrt{(\omega L)^2 + R^2}} = \frac{\omega}{\sqrt{\omega^2 + 1}}$$



e236

ω	0	0.1	0.5	1	10	100	∞
$ H(j\omega) $	0	0.099	0.44	0.707	0.99	0.99995	1

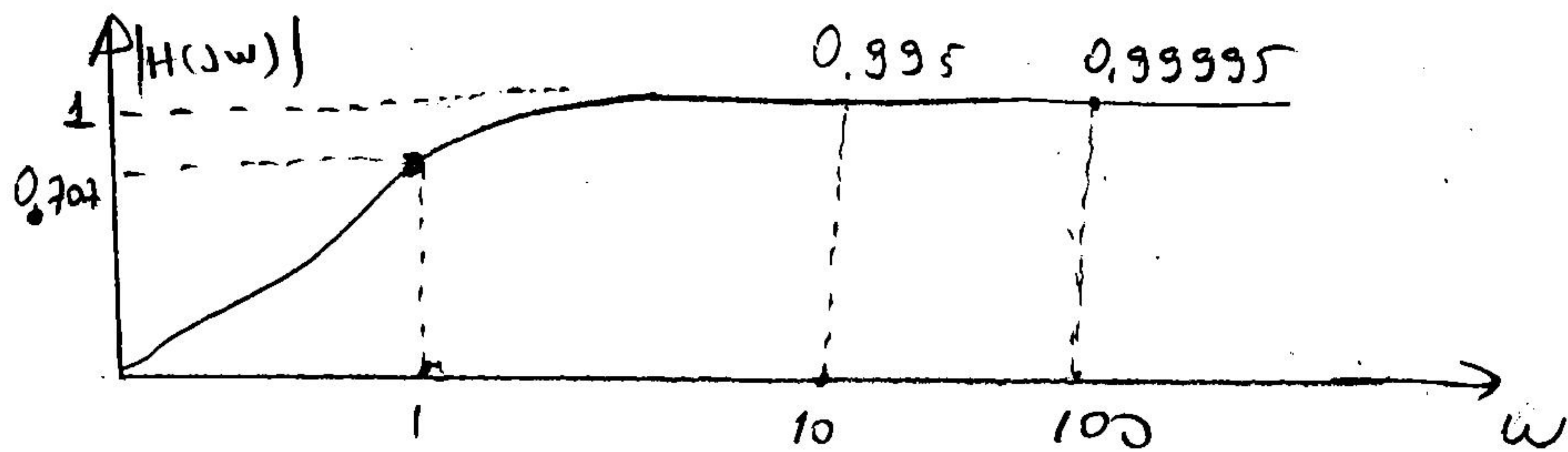

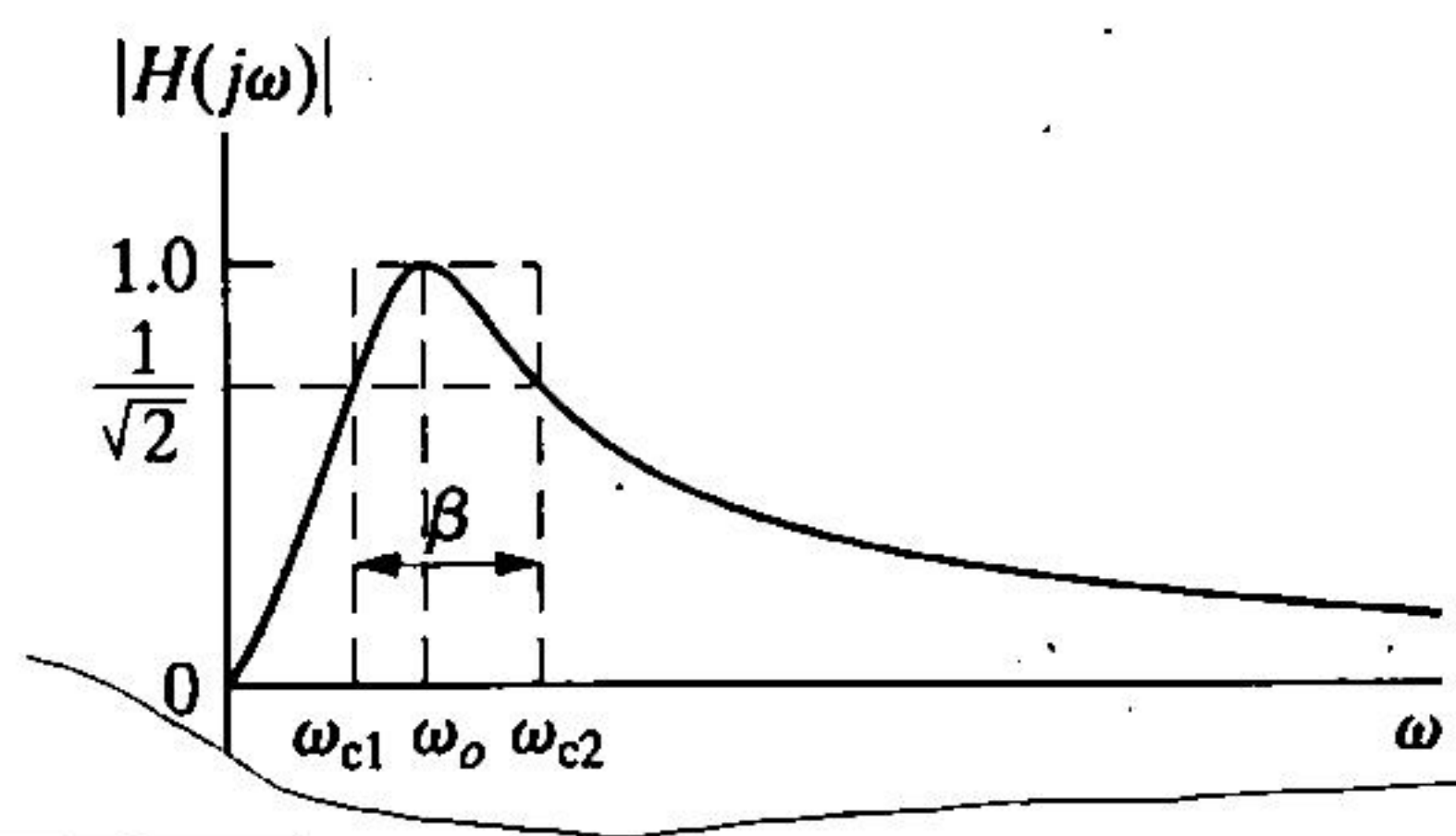
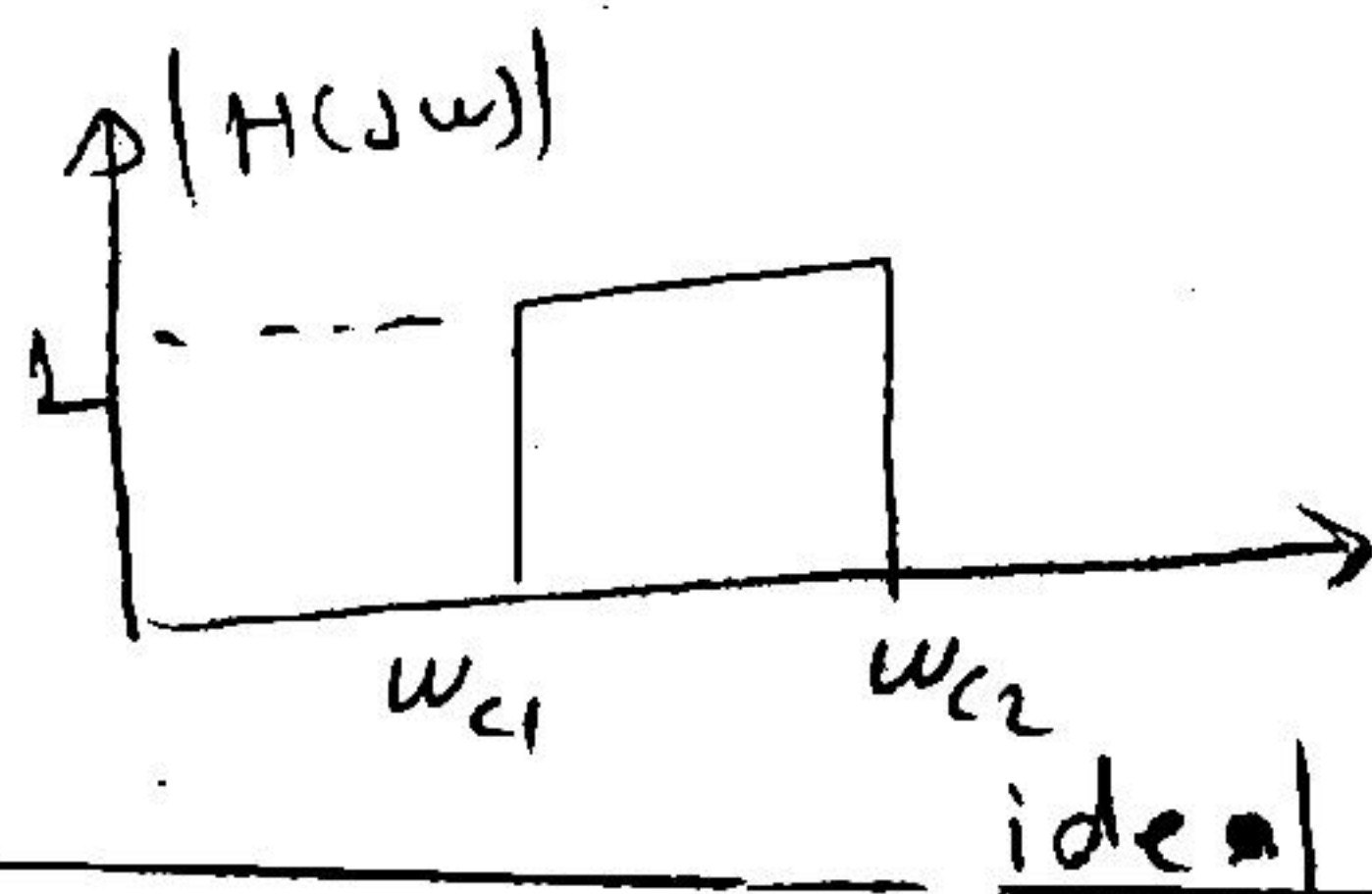
14.4 ♦ Bandpass Filters

Band width $\beta = \omega_{c2} - \omega_{c1}$
Center frequency $\omega_0 = \sqrt{\omega_{c1} \omega_{c2}}$



Quality factor
 $Q = \frac{\omega_0}{\beta}$

The Series RLC Circuit

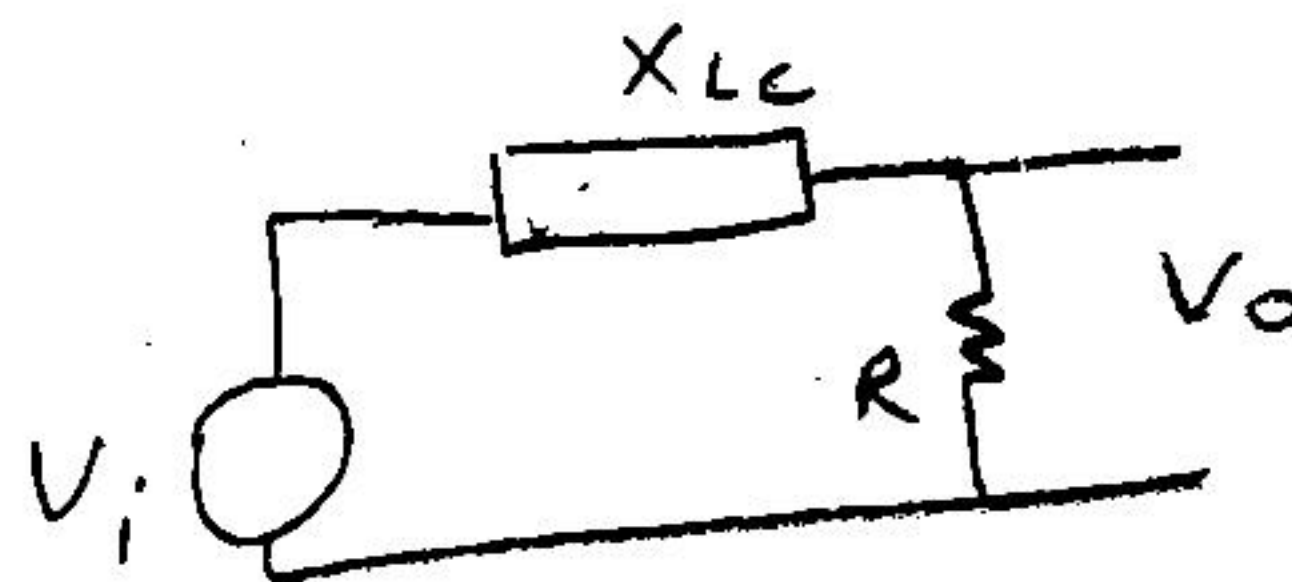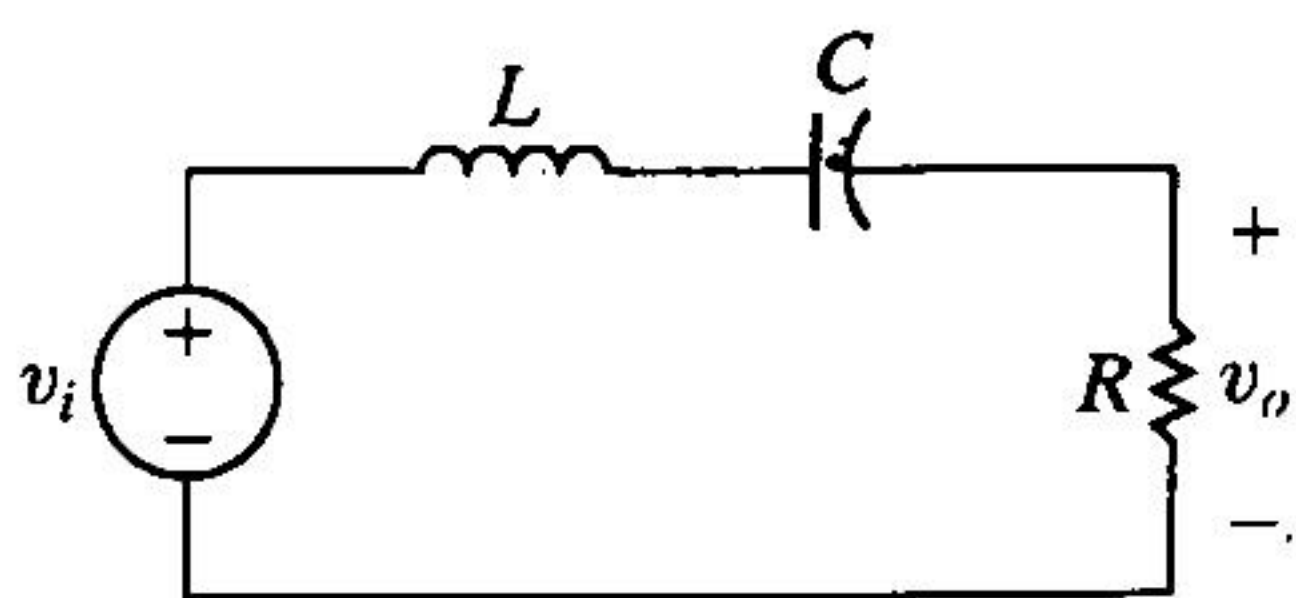

$$V_o = \frac{R}{R + X_{LC}} V_i$$

$$X_{LC} = j\omega L + \frac{1}{j\omega C}$$

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{R}{R + X_{LC}} = \frac{R}{R + j\omega L + \frac{1}{j\omega C}} = \frac{j\omega C R}{j\omega C R + j^2 \omega^2 L C + 1}$$

$$= \frac{j\omega C R}{1 - \omega^2 L C + j\omega C R}$$

$$|H(j\omega)| = \frac{\omega C R}{\sqrt{(1 - \omega^2 L C)^2 + (\omega C R)^2}}$$

$$\Theta(j\omega) = 90 - \tan^{-1} \frac{\omega C R}{1 - \omega^2 L C}$$

it is clear that denominator (المقام) is minimum if $1 - \omega^2 LC = 0$.

Thus $\omega^2 LC = 1$ $\omega = \sqrt{\frac{1}{LC}}$ is the maximum of $|H(j\omega)|$

$$\omega = \sqrt{\frac{1}{LC}} \Rightarrow |H(j\omega)| = \frac{\omega CR}{\sqrt{0^2 + (\omega CR)^2}} = 1$$

$$\text{at } \omega = \omega_c \quad |H(j\omega_c)| = \frac{1}{\sqrt{2}}$$

$$\frac{1}{\sqrt{2}} = \frac{\omega_c RC}{\sqrt{(1 - \omega_c^2 LC)^2 + (\omega_c RC)^2}} \Rightarrow \frac{1}{2} = \frac{(\omega_c RC)^2}{(1 - \omega_c^2 LC)^2 + (\omega_c RC)^2}$$

$$(1 - \omega_c^2 LC)^2 + (\omega_c RC)^2 = 2(\omega_c RC)^2$$

$$1 - 2\omega_c^2 LC + \omega_c^4 (LC)^2 + (\omega_c RC)^2 = 2(\omega_c RC)^2$$

$$1 - 2\omega_c^2 LC + \omega_c^4 (LC)^2 + (\omega_c RC)^2 - 2(\omega_c RC)^2 = 0$$

$$\omega_c^4 (LC)^2 + \omega_c^2 \{-2LC - (RC)^2\} + 1 = 0$$

$$\omega_c^2 = x \quad \omega_c^4 = x^2$$

$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}, \quad (14.29)$$

$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}. \quad (14.30)$$

$$\beta = \omega_{c2} - \omega_{c1}$$

$$Q = \frac{\omega_o}{\beta} = \sqrt{\frac{L}{CR^2}}$$

$$\omega_{c1} = -\frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_o^2}, \quad (14.34)$$


$$\omega_{c1} = \omega_o \cdot \left[-\frac{1}{2Q} + \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \right], \quad (14.36)$$

$$\omega_{c2} = \frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_o^2}. \quad (14.35)$$

$$\omega_{c2} = \omega_o \cdot \left[\frac{1}{2Q} + \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \right]. \quad (14.37)$$

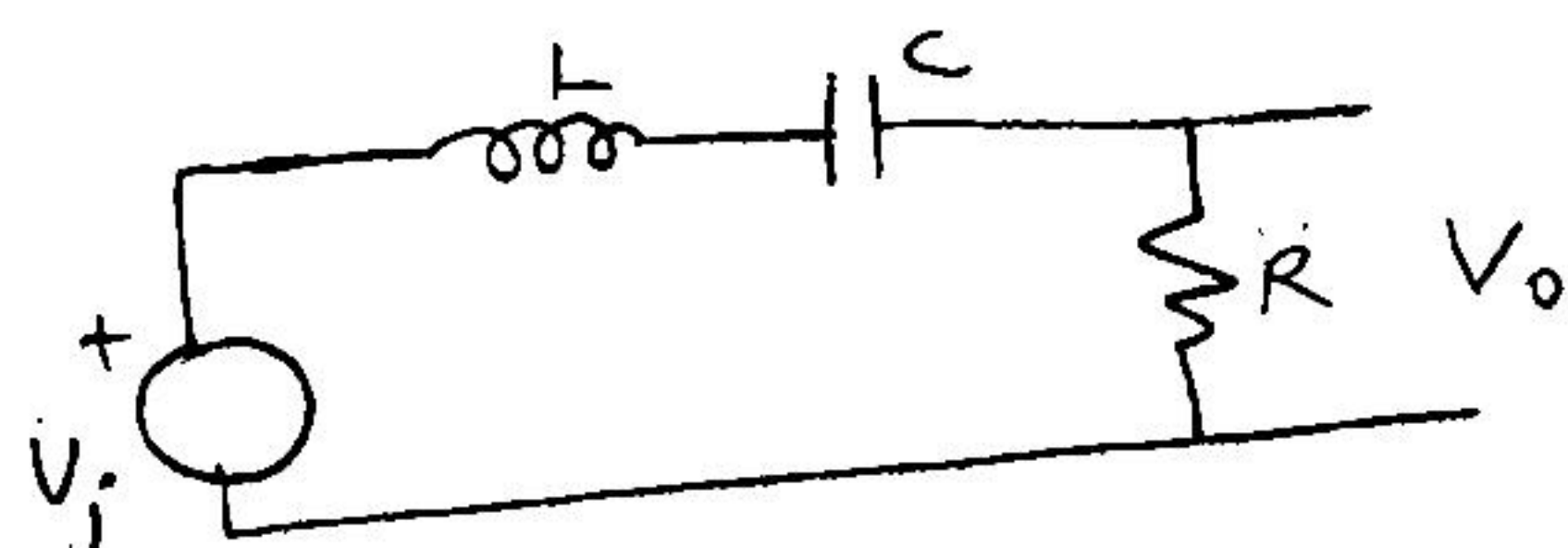EXAMPLE 14.5

A graphic equalizer is an audio amplifier that allows you to select different levels of amplification within different frequency regions. Using the series RLC circuit in Fig. 14.19(a), choose values for R , L , and C that yield a bandpass circuit able to select inputs within the 1–10 kHz frequency band. Such a circuit might be used in a graphic equalizer to select this frequency band from the larger audio band (generally 0–20 kHz) prior to amplification.



Solution:

1–10 kHz

$$f_{c1} = 1 \text{ kHz} \quad f_{c2} = 10 \text{ kHz}$$

$$\omega_{c1} = 2\pi \times 1000$$

$$\omega_{c2} = 2\pi \times 10000$$

$$\omega_0 = \sqrt{\omega_{c1} \omega_{c2}} = \sqrt{2\pi \times 1000 \times 2\pi \times 10000}$$

$$\omega_0 = 2\pi \times 3162.2$$

$$\omega_0 = \sqrt{\frac{1}{LC}} \Rightarrow \omega_0^2 = \frac{1}{LC} \Rightarrow L = \frac{1}{\omega_0^2 C}$$

$$C = 1 \mu\text{F} = 10^{-6} \text{ F (arbitrary)}$$

$$L = \frac{1}{\omega_0^2 C} = \frac{1}{(2\pi \times 3162)^2 \times 10^{-6}} = 2.5 \times 10^{-3}$$

$$L = 2.5 \text{ mH}$$

$$\phi = \frac{\omega_0}{\beta} = \frac{\omega_0}{\omega_{c2} - \omega_{c1}} = \frac{2\pi \times 3162}{2\pi (10000 - 1000)}$$

$$= 0.3514$$

e238

$$\phi = \sqrt{\frac{L}{CR^2}} \Rightarrow \phi^2 = \frac{L}{CR^2}$$

$$R = \sqrt{\frac{L}{\phi^2 C}} = \sqrt{\frac{2.5 \times 10^{-3}}{0.35^2 \times 10^{-6}}} =$$

$$= 142.8 \Omega$$

Draw the amplitude spectrum for $C = 10^{-6}$


$$R = 142.8 \quad L = 2.5 \times 10^{-3}$$

$$|H(j\omega)| = \frac{\omega CR}{\sqrt{(1 - \omega^2 LC)^2 + (\omega CR)^2}}$$

$$= \frac{\omega \times 10^{-6} \times 142}{\sqrt{(1 - \omega^2 \times 2.5 \times 10^{-3} \times 10^{-6})^2 + (\omega \times 10^{-6} \times 142)^2}}$$

$$\text{for } \omega = 0 \Rightarrow H(j\omega) = 0$$

f	ω	$ H(j\omega) $
0	0	0
1	6.28	0.0009
10	62.8	0.0090
1000	6283	0.7055
3160	19854	0.999986
3162	19867	0.999989
3170	19917	0.999988
5000	31415	0.9504
10000	62831	0.7112
100000	628318	0.0906
∞	∞	0

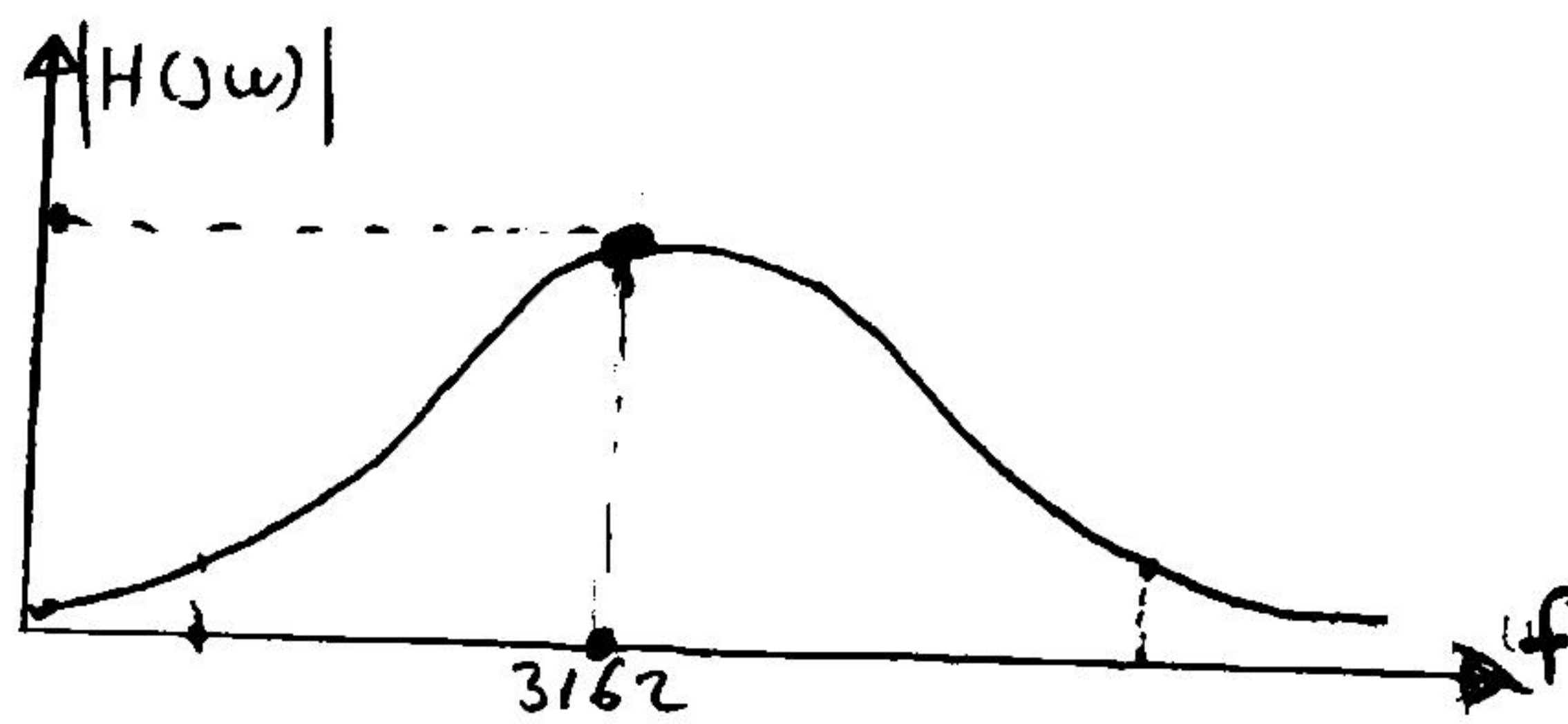

EXAMPLE 14.6

- Show that the RLC circuit in Fig. 14.22 is also a bandpass filter by deriving an expression for the transfer function $H(s)$.
- Compute the center frequency, ω_0 .
- Calculate the cutoff frequencies, ω_{c1} and ω_{c2} , the bandwidth, β , and the quality factor, Q .
- Compute values for R and L to yield a bandpass filter with a center frequency of 5 kHz and a bandwidth of 200 Hz, using a $5 \mu\text{F}$ capacitor.


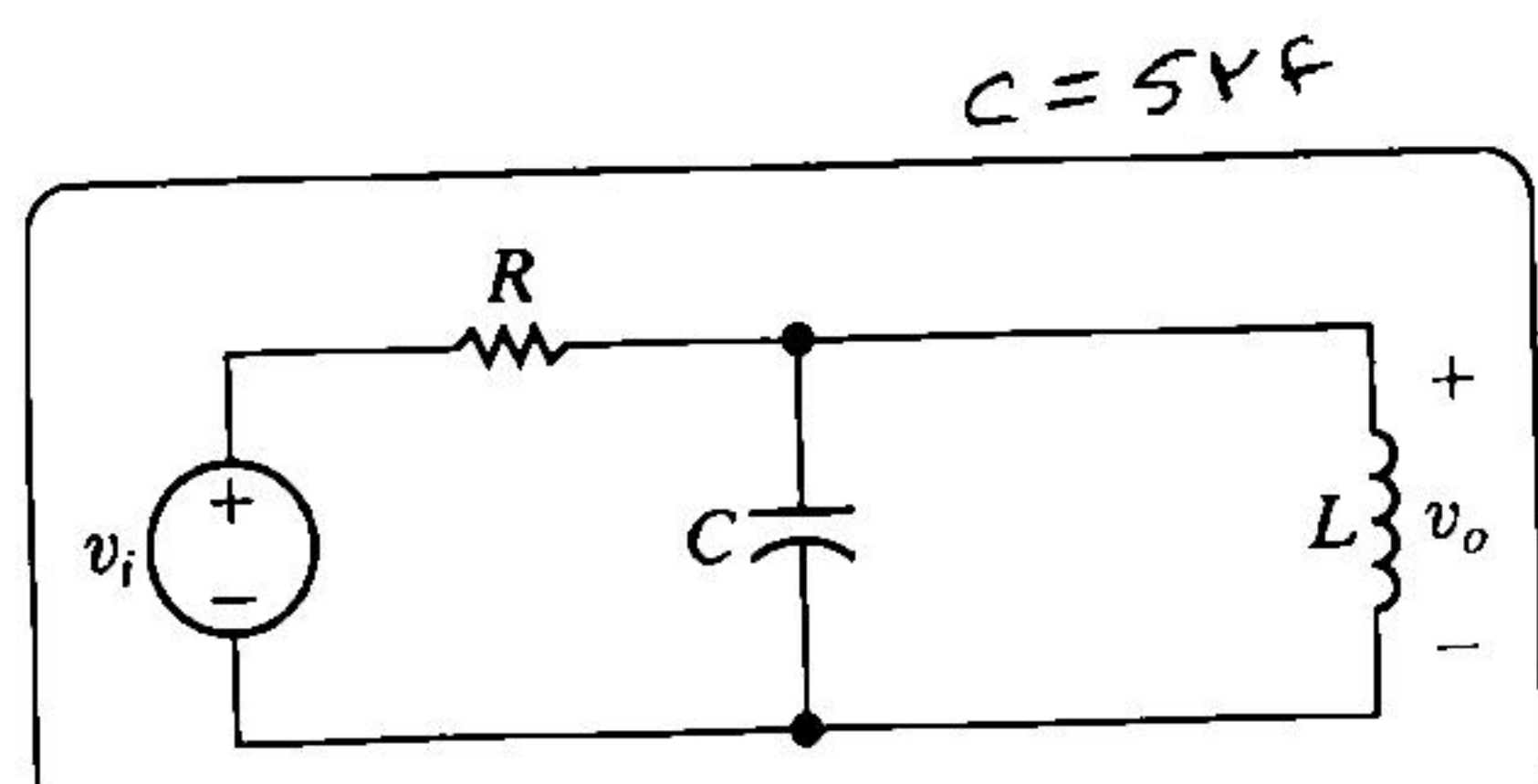


Figure 14.22 The circuit for Example 14.6.

solution

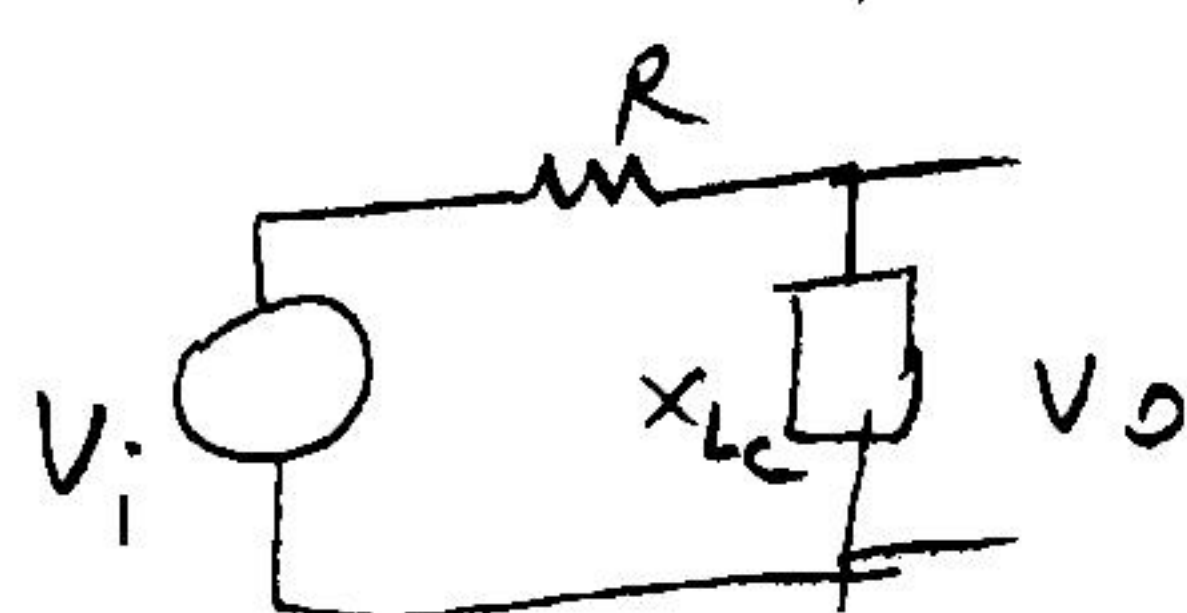

$$X_{LC} = j\omega L \parallel \frac{1}{j\omega C}$$

$$X_{LC} = \frac{j\omega L \cdot \frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C}} = \frac{j\omega L}{1 - \omega^2 LC}$$

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{X_{LC}}{X_{LC} + R} = \frac{\frac{j\omega L}{1 - \omega^2 LC}}{\frac{j\omega L}{1 - \omega^2 LC} + R}$$

$$= \frac{j\omega L}{j\omega L + R(1 - \omega^2 LC)}$$

$$|H(j\omega)| = \frac{\omega L}{\sqrt{[R(1 - \omega^2 LC)]^2 + (\omega L)^2}}$$

$$\theta(j\omega) = 90^\circ - \tan^{-1} \frac{\omega L}{R(1 - \omega^2 LC)}$$

$$\text{if } 1 - \omega^2 LC = 0 \Rightarrow |H(j\omega)| = 1$$

maximum value of $|H(j\omega)|$ is 1

$$1 - \omega_0^2 LC = 0 \Rightarrow \omega_0 = \sqrt{\frac{1}{LC}}$$

$$\text{at } \omega = \omega_c \quad |H(j\omega_c)| = \frac{1}{\sqrt{2}}$$

$$\frac{1}{\sqrt{2}} = \frac{\omega_c L}{\sqrt{[R(1 - \omega_c^2 LC)]^2 + (\omega_c L)^2}}$$

$$\frac{1}{2} = \frac{(\omega_c L)^2}{R^2(1 - \omega_c^2 LC)^2 + (\omega_c L)^2}$$

$$R^2(1 - \omega_c^2 LC)^2 + (\omega_c L)^2 = 2(\omega_c L)^2$$

$$R^2[1 - 2\omega_c^2 LC + \omega_c^4 (LC)^2] - (\omega_c L)^2 = 0$$

$$\omega_c^4 (RLC)^2 + \omega_c^2 (-2R^2 LC - L^2) + R^2 = 0$$

$$\omega_c^2 = x \quad \omega_c^4 = x^2$$

$$\omega_{c1} = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$\omega_{c2} = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$\beta = \omega_{c2} - \omega_{c1} = \frac{1}{RC}$$


$$Q = \omega_0 / \beta = \sqrt{\frac{R^2 C}{L}}$$

$$\text{d) } \omega_0 = 2\pi \times 5000 \quad C = 5 \times 10^{-6} \quad \beta = 200$$

$$R = \frac{1}{\beta C} = 158.15 \Omega$$

$$L = \frac{1}{\omega_0^2 C} = 202.6 \times 10^{-6}$$

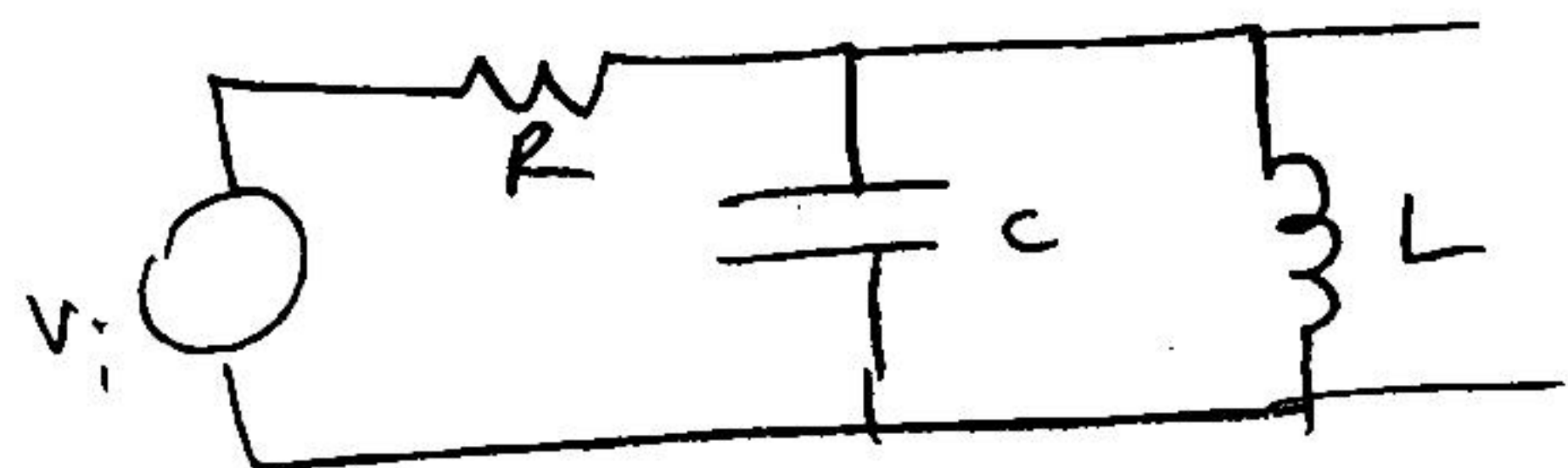
Draw the amplitude spectrum for $C=5\mu F$ $R=160\Omega$ $L=2 \times 10^{-4}$ e240



$$|H(\omega)| = \frac{\omega L}{\sqrt{[R(1 - \omega^2 LC)]^2 + (\omega L)^2}}$$


$$|H(\omega)| = \frac{\omega \cdot 2 \times 10^{-4}}{\sqrt{[160(1 - \omega^2 \cdot 2 \times 10^{-4} \times 5 \times 10^{-6})]^2 + (\omega \times 2 \times 10^{-4})^2}}$$

f	ω	$ H(\omega) $
0	0	0
1	6.28	0.0050
10	62.8	0.0502
100	628	0.449
1000	6283	0.9822
4990	31353	0.99999
5000	31416	1.000
5010	31479	0.99999
5100	32044	0.9999
10000	62832	0.9828
100000	628319	0.787
∞	0	0

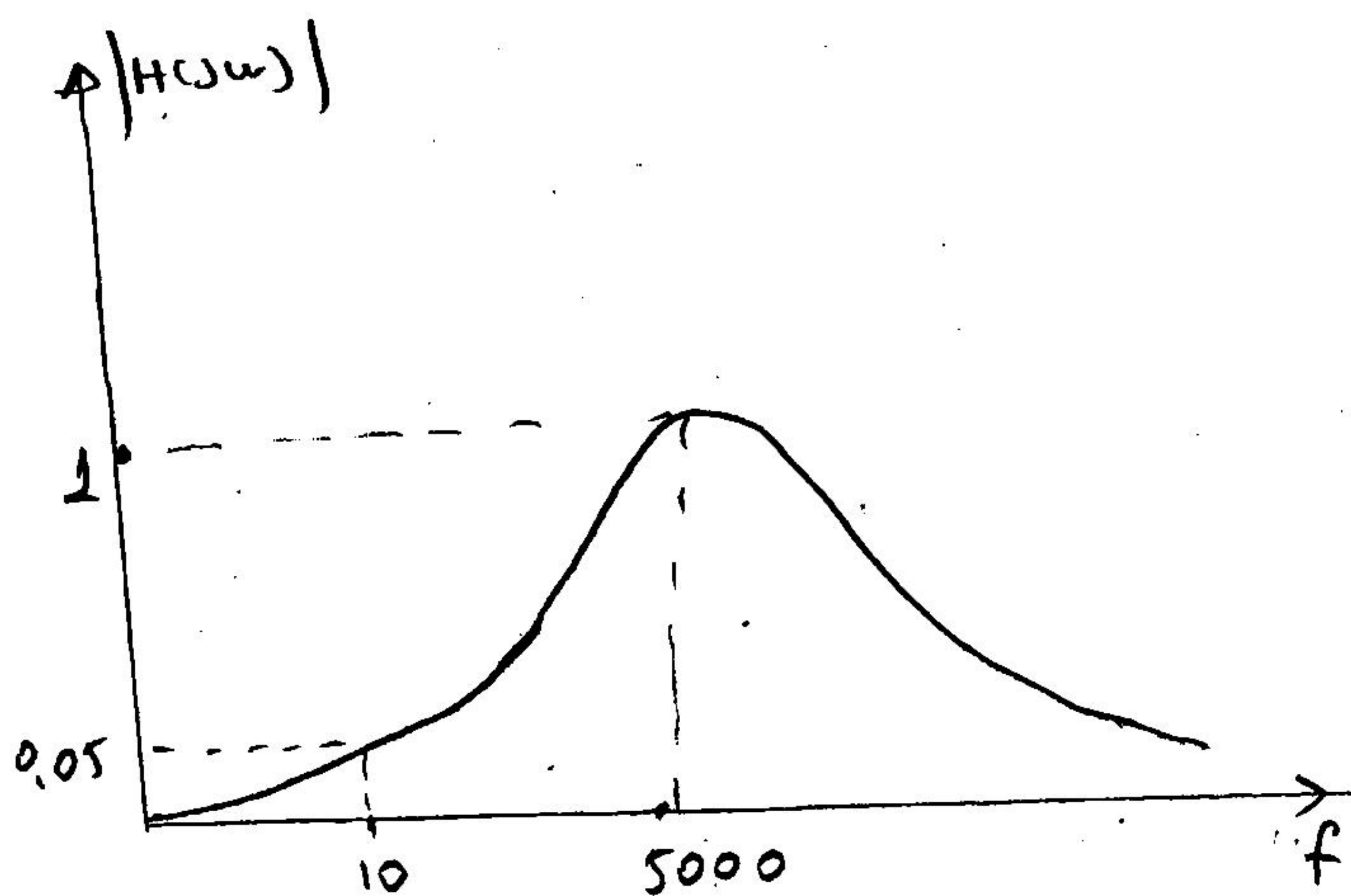

14.5 ♦ Bandreject Filters

Example

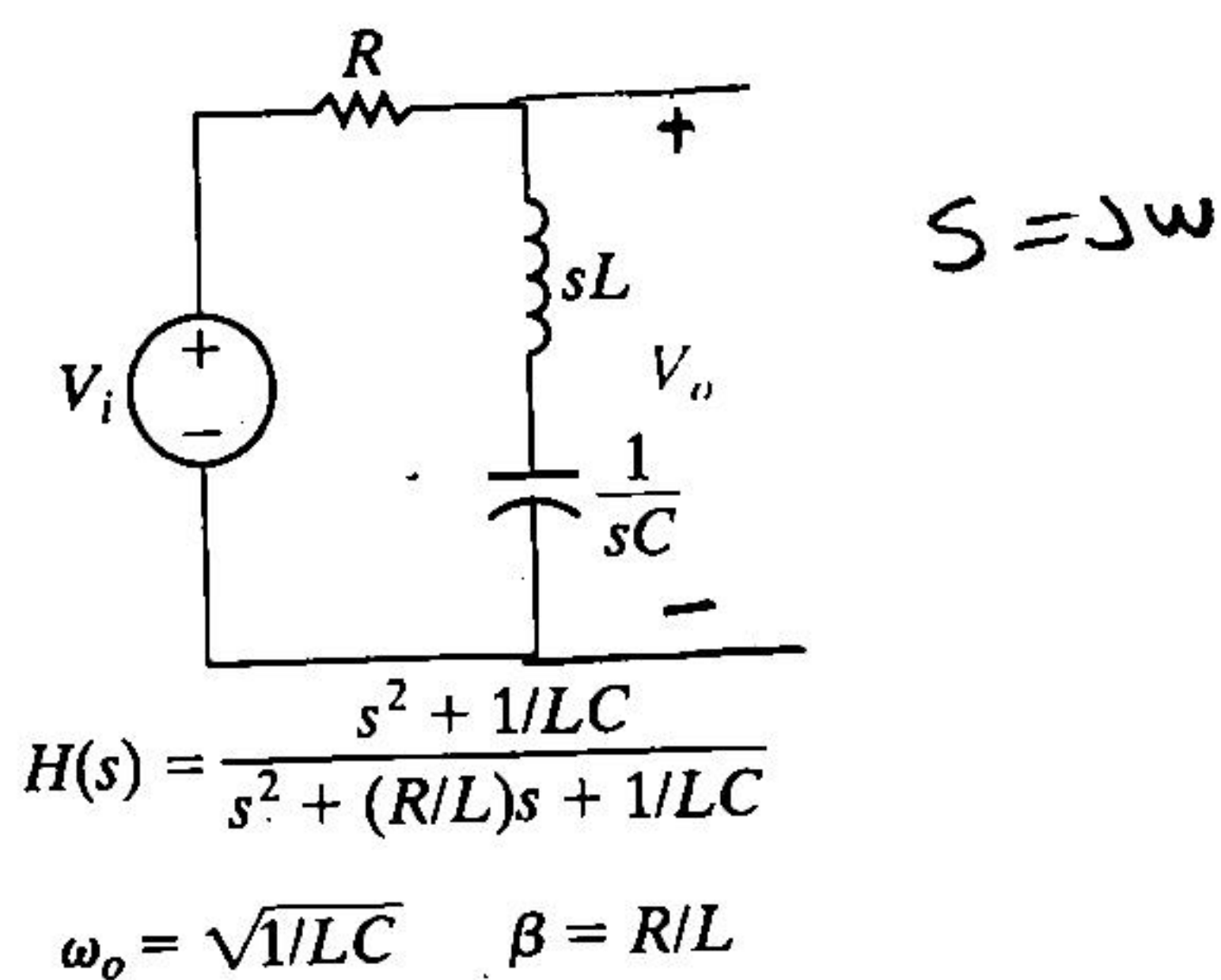


Draw amplitude spectrum for
 $C = 0.5275 \times 10^{-6} \text{ F}$ $L = 3 \times 10^{-3}$ $R = 15 \Omega$

$$H(j\omega) = \frac{(j\omega)^2 + 1/LC}{(j\omega)^2 + (\frac{R}{L})j\omega + \frac{1}{LC}}$$


$$|H(j\omega)| = \frac{|-\omega^2 + 1/LC|}{\sqrt{(\frac{1}{LC} - \omega^2)^2 + (\frac{R\omega}{L})^2}}$$

f	ω	$ H(j\omega) $
0	0	1
1	6.28	1
10	62.8	1
100	628	0.9999
1000	6283	0.9986
3990	25069	0.272
4000	25132	0.02
4010	25195	0.231
5000	31415	0.914
10000	62831	0.9955
∞	∞	1

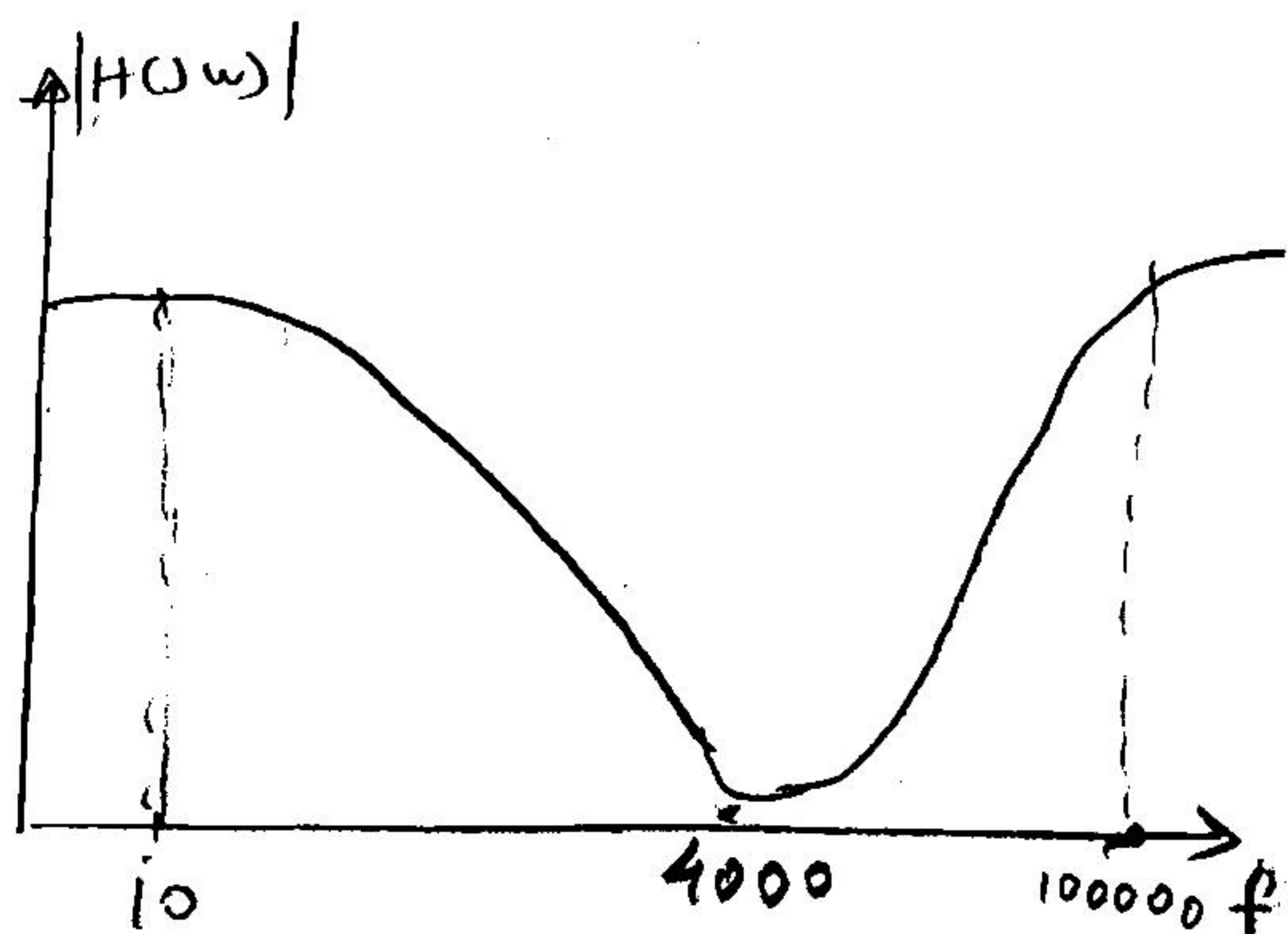

Example

e241

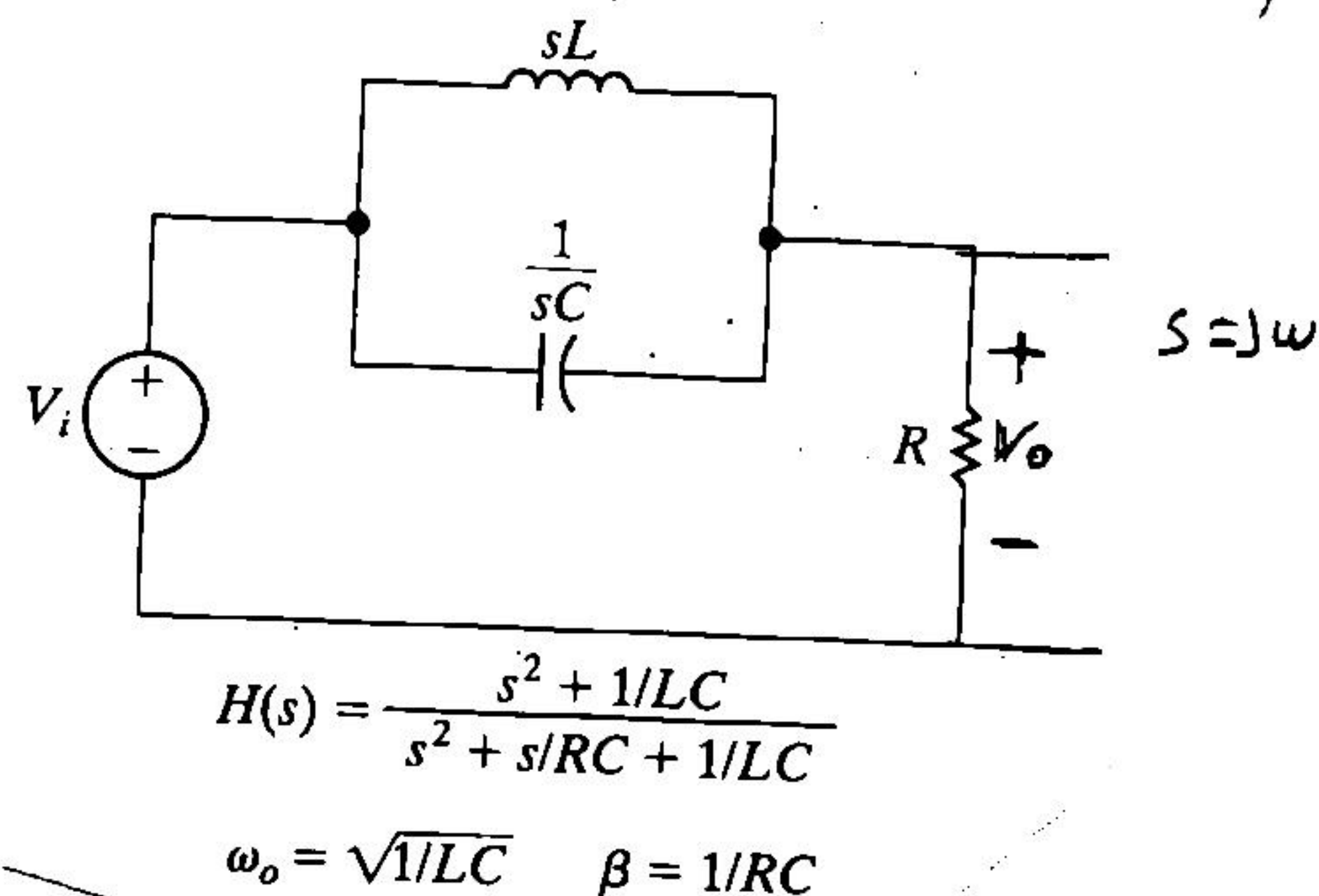


Draw amplitude spectrum for
 $C = 0.5 \times 10^{-6}$ $L = 3 \times 10^{-3}$ $R = 15$


$$H(j\omega) = \frac{(j\omega)^2 + 1/LC}{(j\omega)^2 + \frac{1}{RC}j\omega + \frac{1}{LC}}$$


$$|H(j\omega)| = \frac{|\frac{1}{LC} - \omega^2|}{\sqrt{(\frac{1}{LC} - \omega^2)^2 + (\frac{\omega}{RC})^2}}$$

f	ω	$H(j\omega)$
0	0	1
1	6.28	1
10	62.8	0.9999
100	628.3	0.9922
1000	6283	0.598
3990	25069	0.001
4000	25132	0.0001
4010	25195	0.001
5000	31415	0.0891
10000	62831	0.3853
100000	628318	0.9803
∞	∞	1

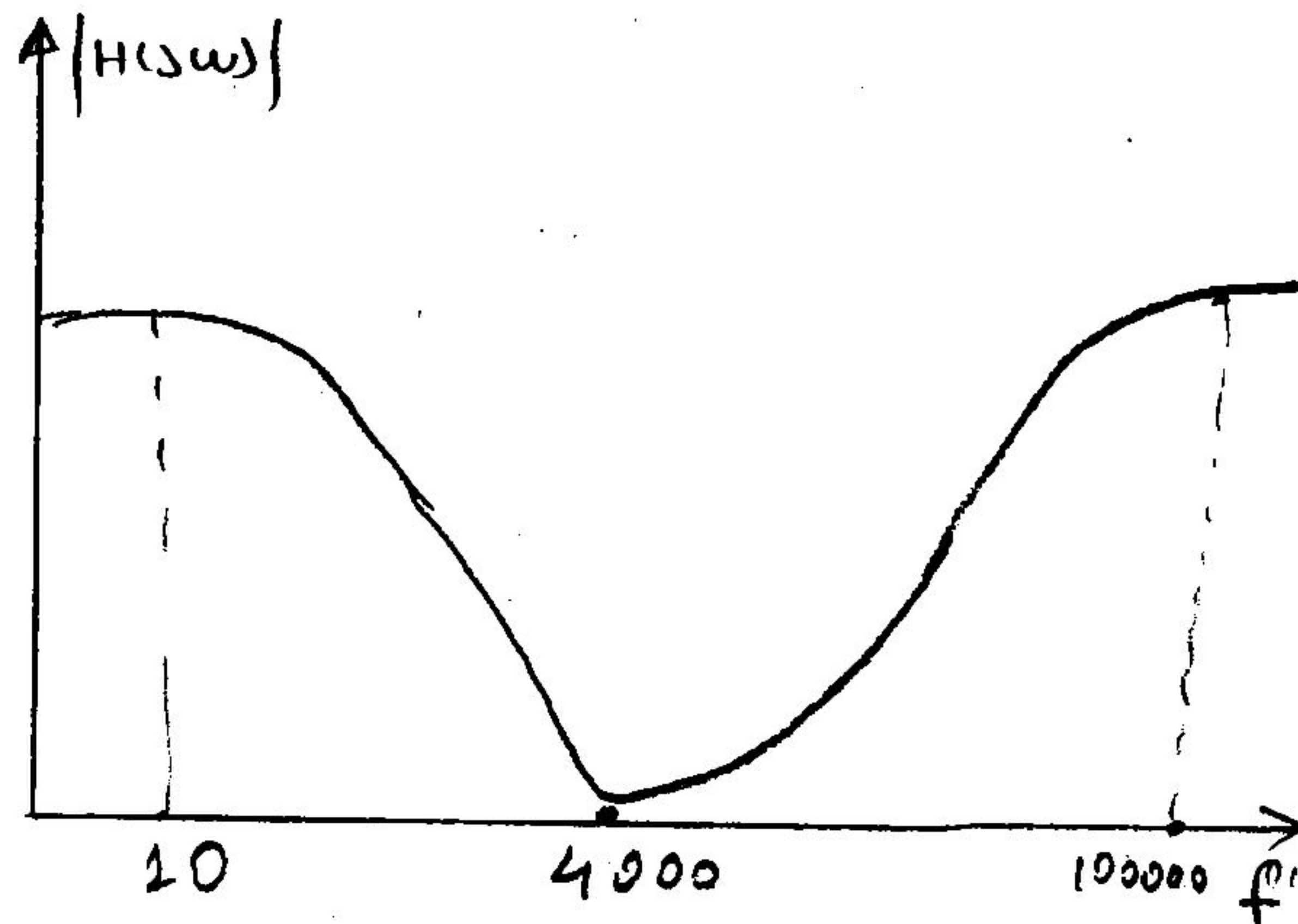

frequency Response by Inspection 251

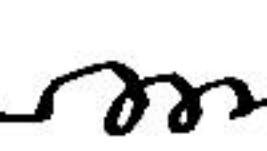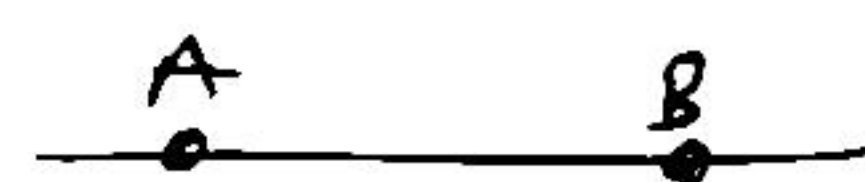
A —  — B $Z_L = j\omega L$ $\omega = 0 \Rightarrow Z_L = 0 \Rightarrow$ Short circuit



$\omega = \infty \Rightarrow Z_L = \infty \Rightarrow$ Open circuit



$\omega = 0 \Rightarrow$

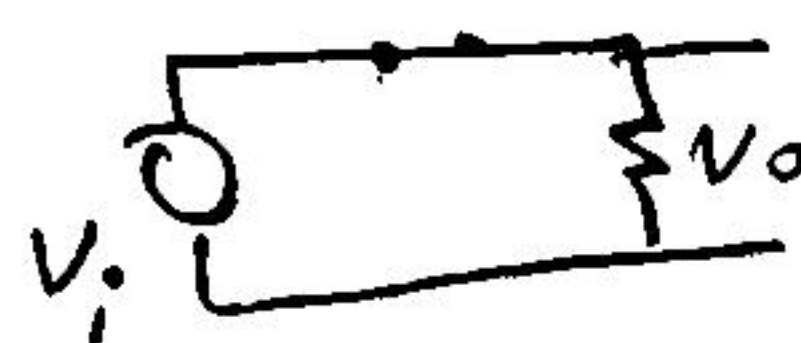


$$V_o = V_i \quad |H| = \left| \frac{V_o}{V_i} \right| = 1$$


$\omega = \infty \Rightarrow$



$$V_o = 0 \quad |H| = \left| \frac{V_o}{V_i} \right| = 0$$

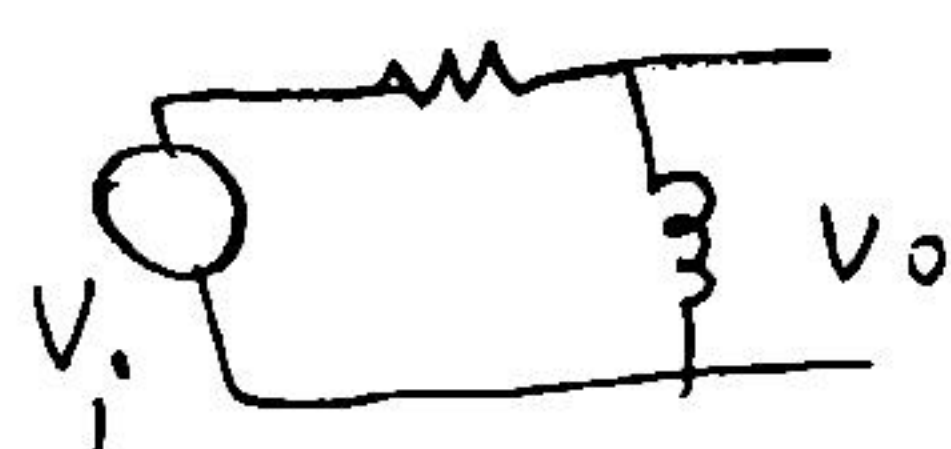


$\omega = 0 \Rightarrow$

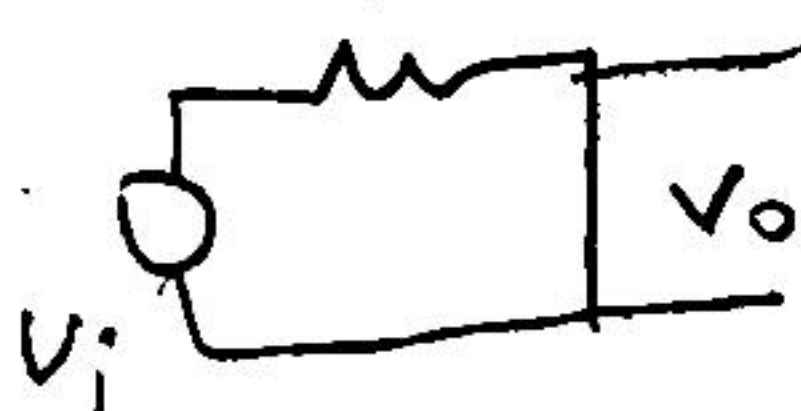


$$V_o = 0 \quad |H| = \left| \frac{V_o}{V_i} \right| = 0$$

$\omega = \infty \Rightarrow$

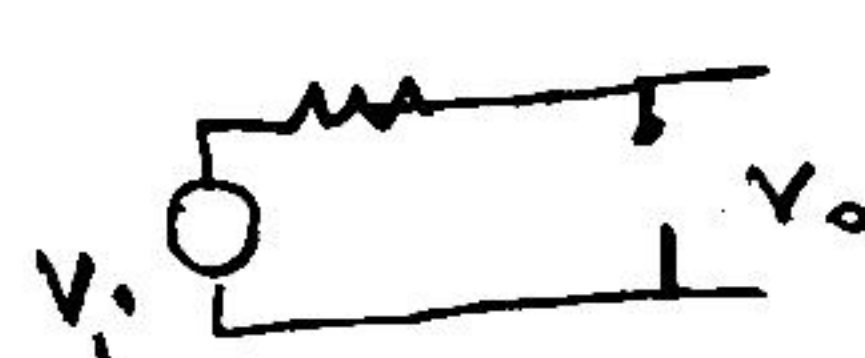


$$V_o = V_i \quad |H| = \left| \frac{V_o}{V_i} \right| = 1$$

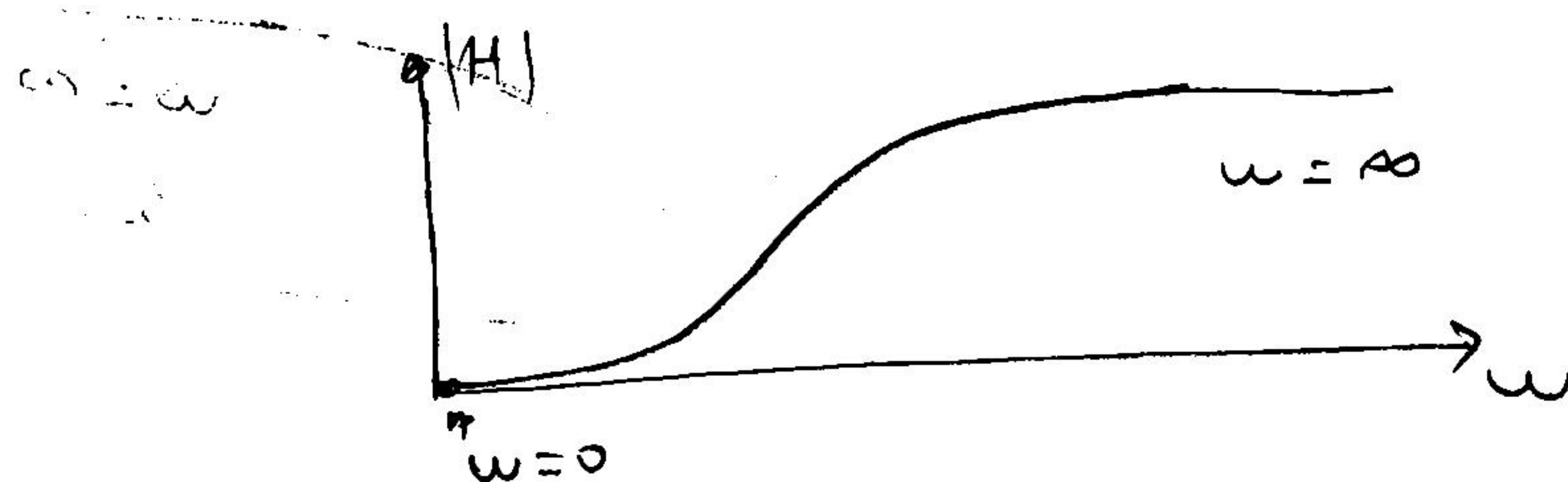


$$\text{---} \text{||} \text{---} \quad Z_c = \frac{1}{j\omega C} \quad \omega = 0 \quad Z_c = \frac{1}{0} = \infty \Rightarrow \text{Open circuit}$$
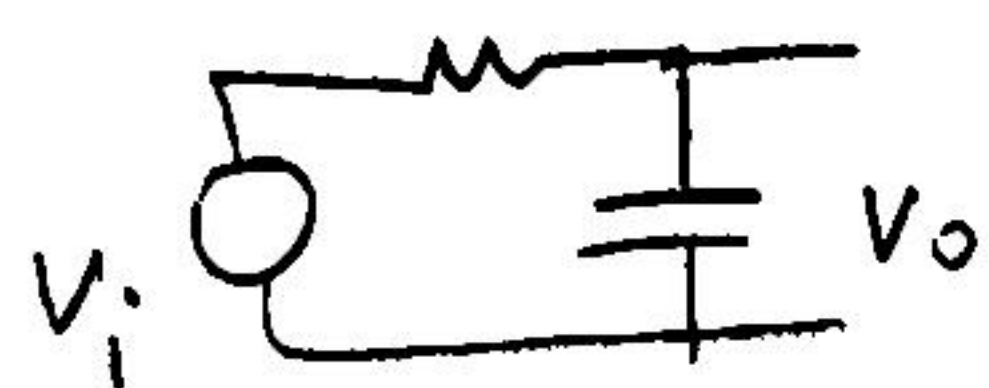
$$\omega = \infty \quad Z_c = \frac{1}{\infty} = 0 \Rightarrow \text{short circuit}$$




$$\omega = 0$$


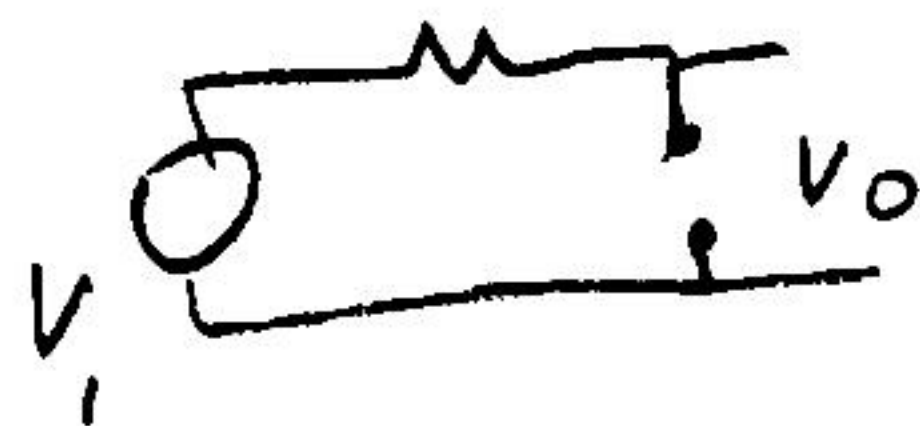


$$V_o = V_i \quad |H| = \left| \frac{V_o}{V_i} \right| = 1$$


$$\omega = \infty$$

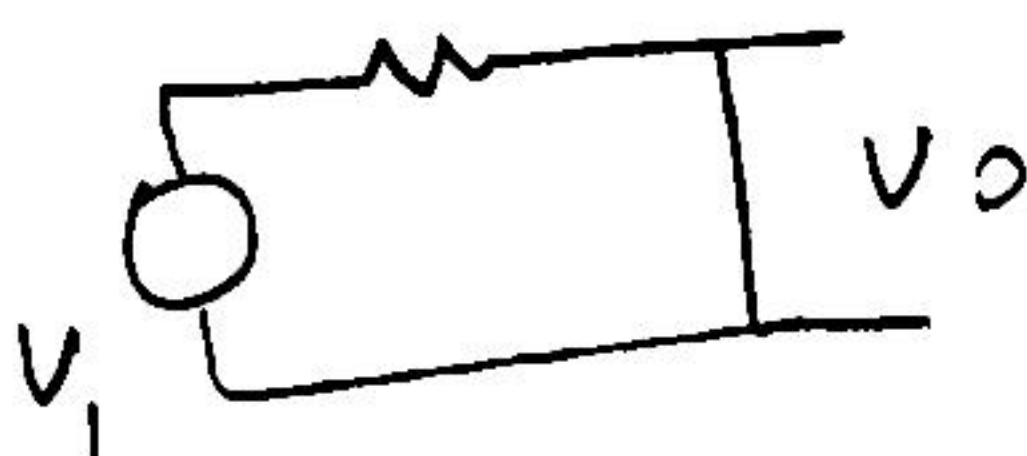

$$V_o = 0 \quad |H| = \left| \frac{V_o}{V_i} \right| = 0$$

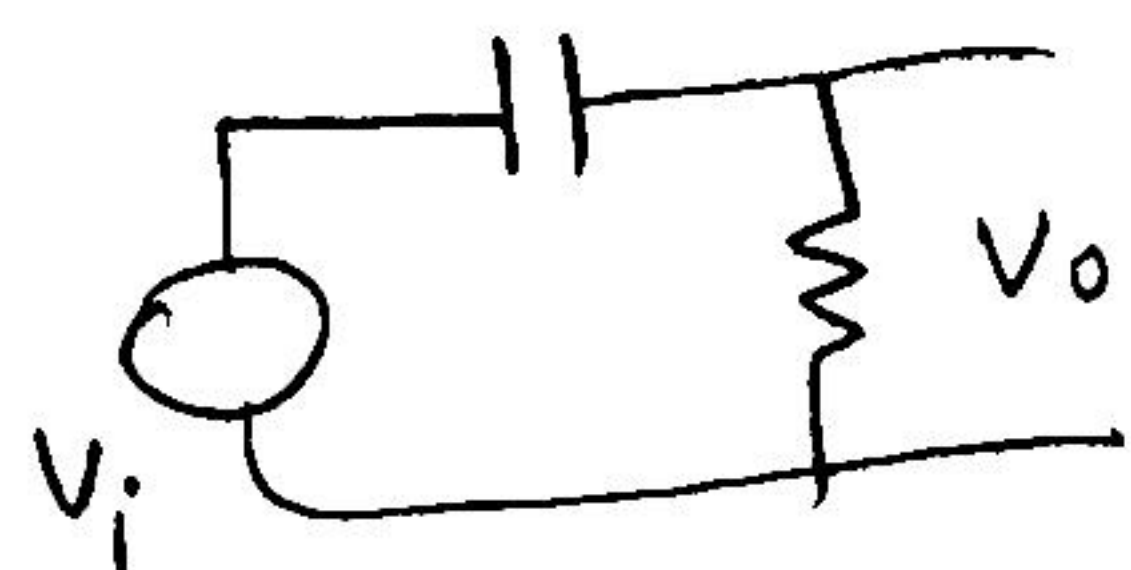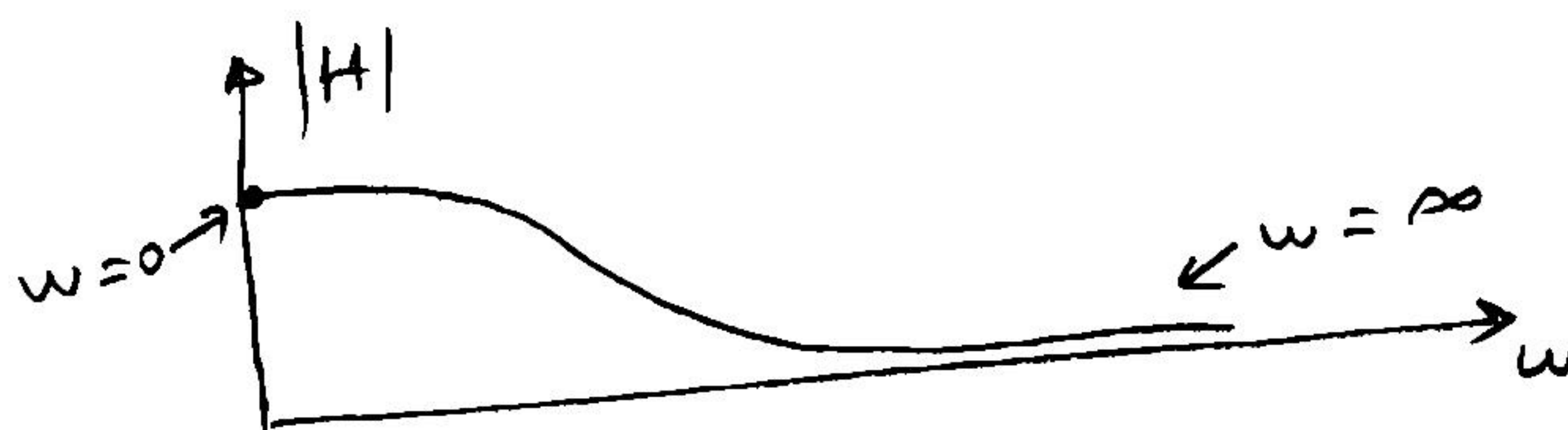


$$\omega = 0$$

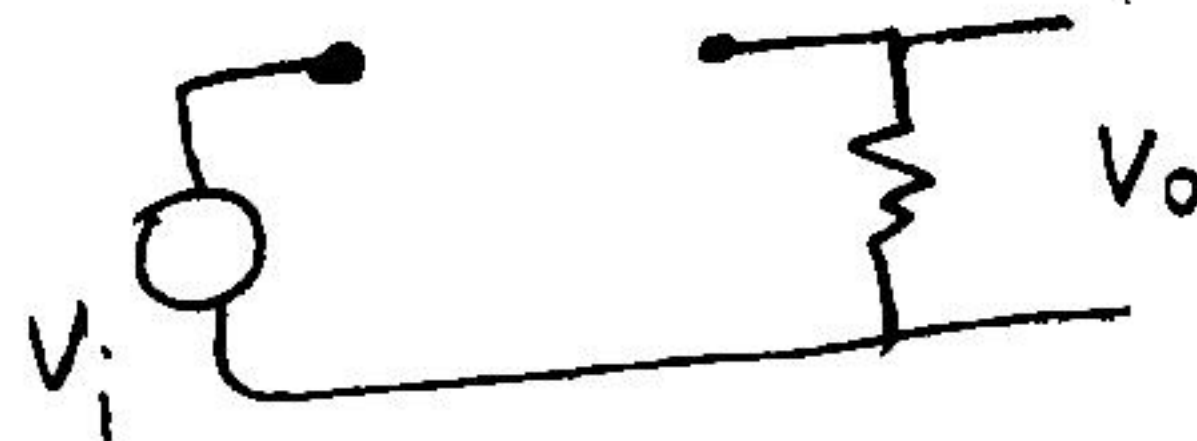



$$V_o = 0 \quad |H| = \left| \frac{V_o}{V_i} \right| = 0$$

$$\omega = \infty$$

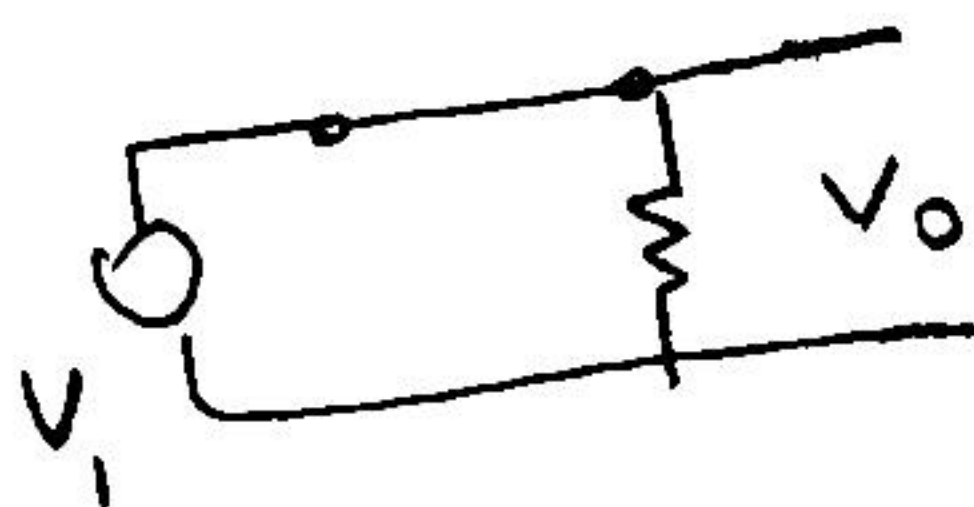


$$V_o = V_i \quad |H| = \left| \frac{V_o}{V_i} \right| = 1$$

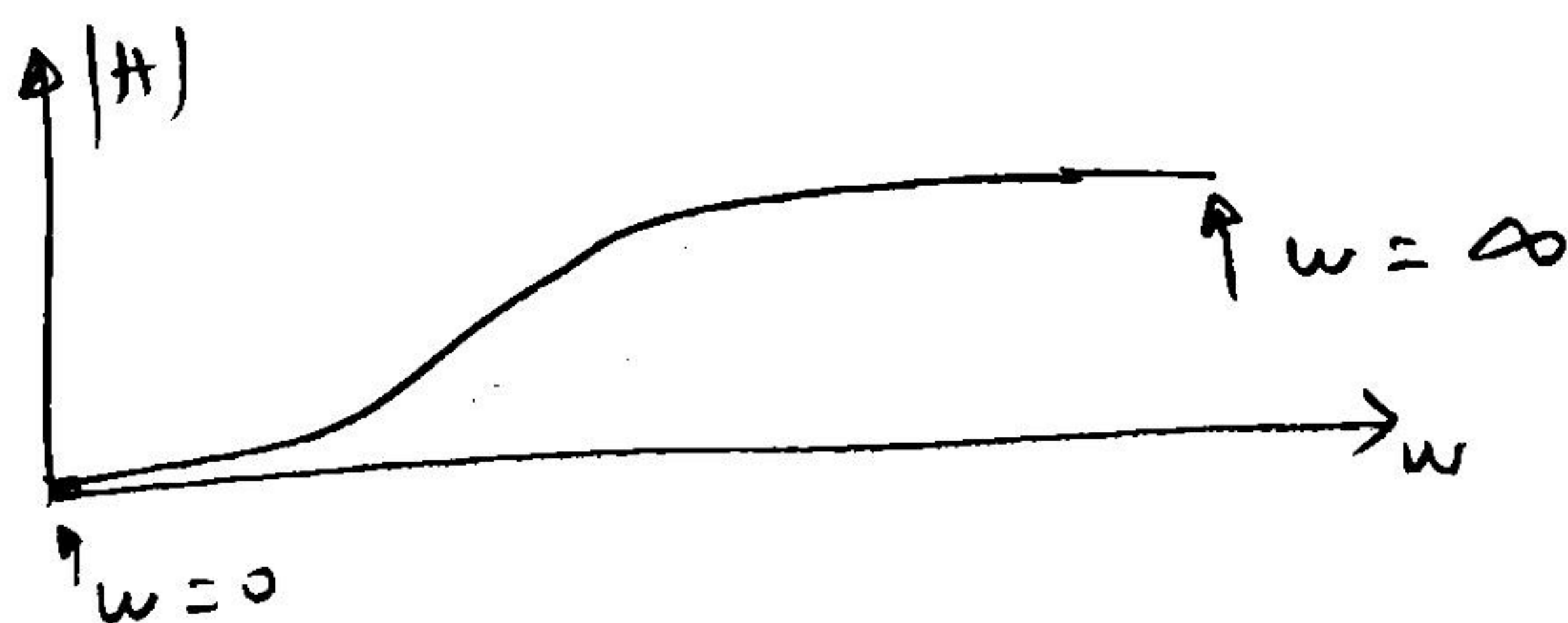

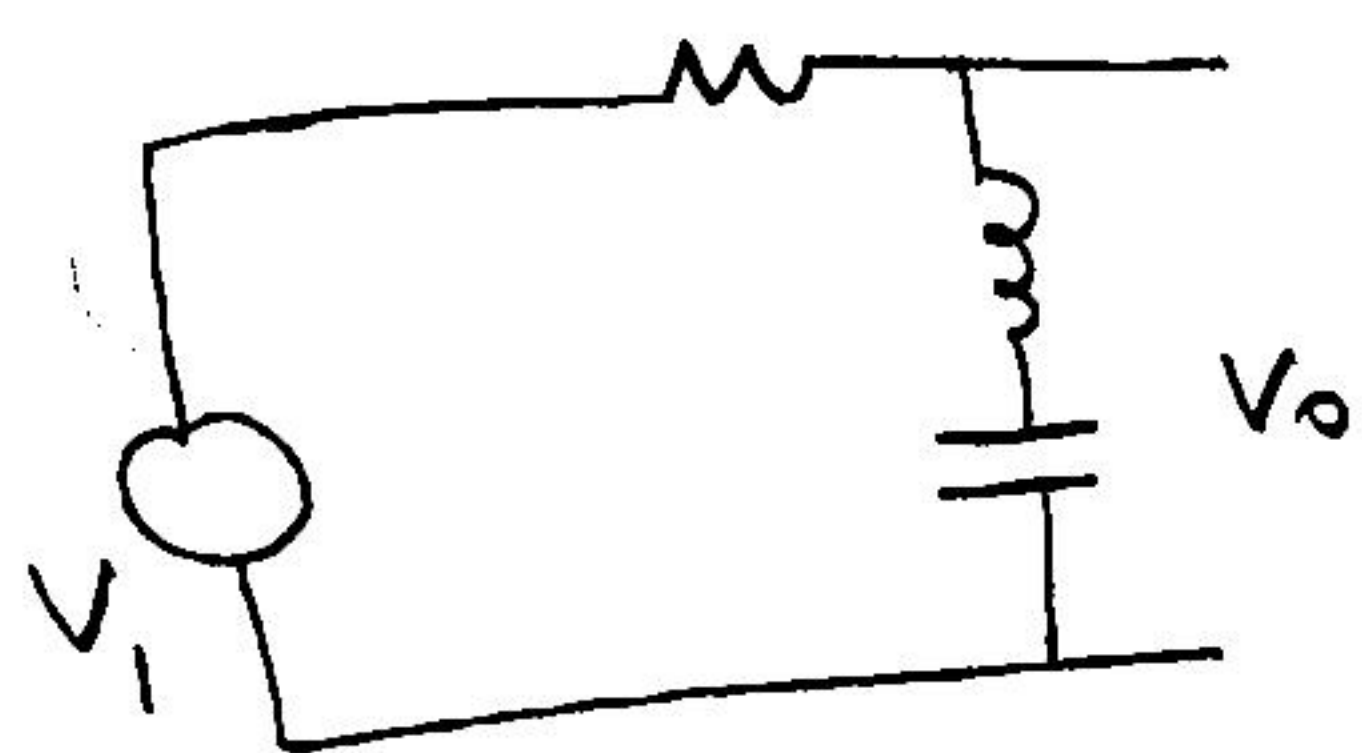


$$\omega = 0$$

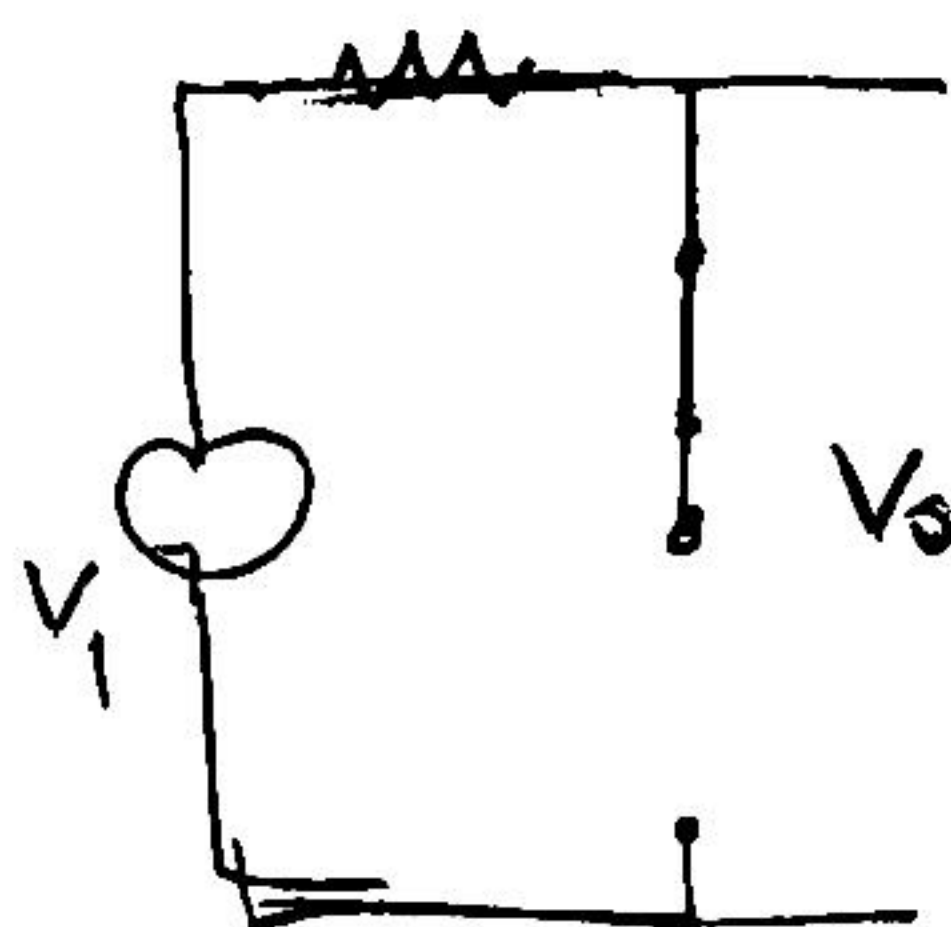


$$V_o = V_1 \quad |H| = \left| \frac{V_o}{V_1} \right| = 1$$

$$\omega = \frac{1}{\sqrt{LC}}$$

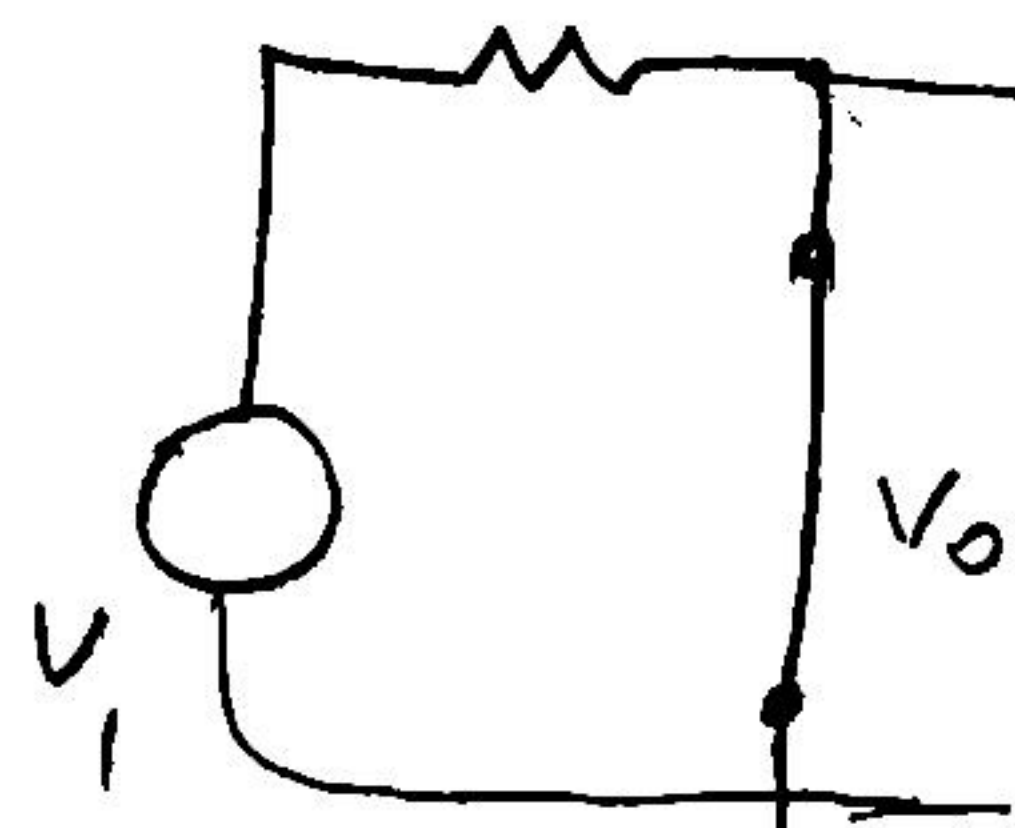



$$V_o = 0 \quad |H| = \left| \frac{V_o}{V_1} \right| = 0$$

$$\omega = \infty$$

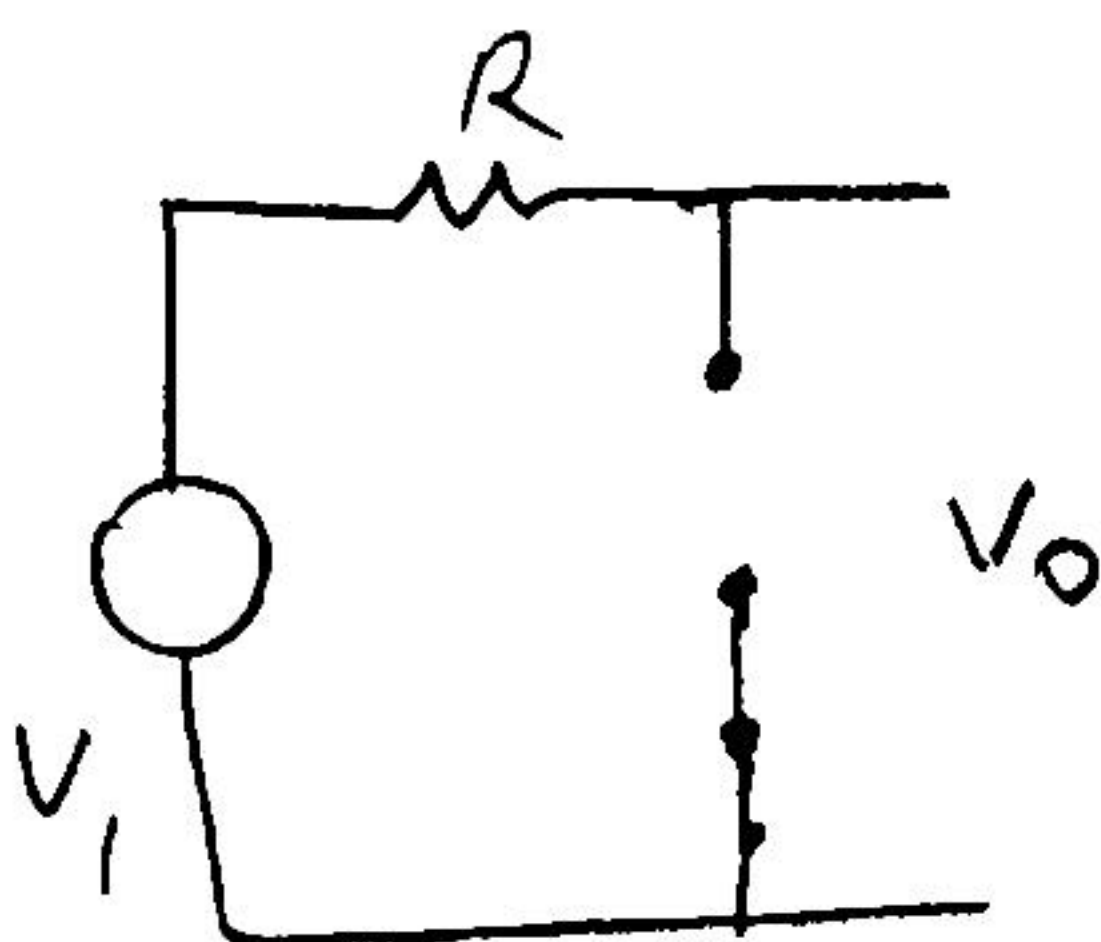

$$V_o = V_1 \quad |H| = \left| \frac{V_o}{V_1} \right| = 1$$

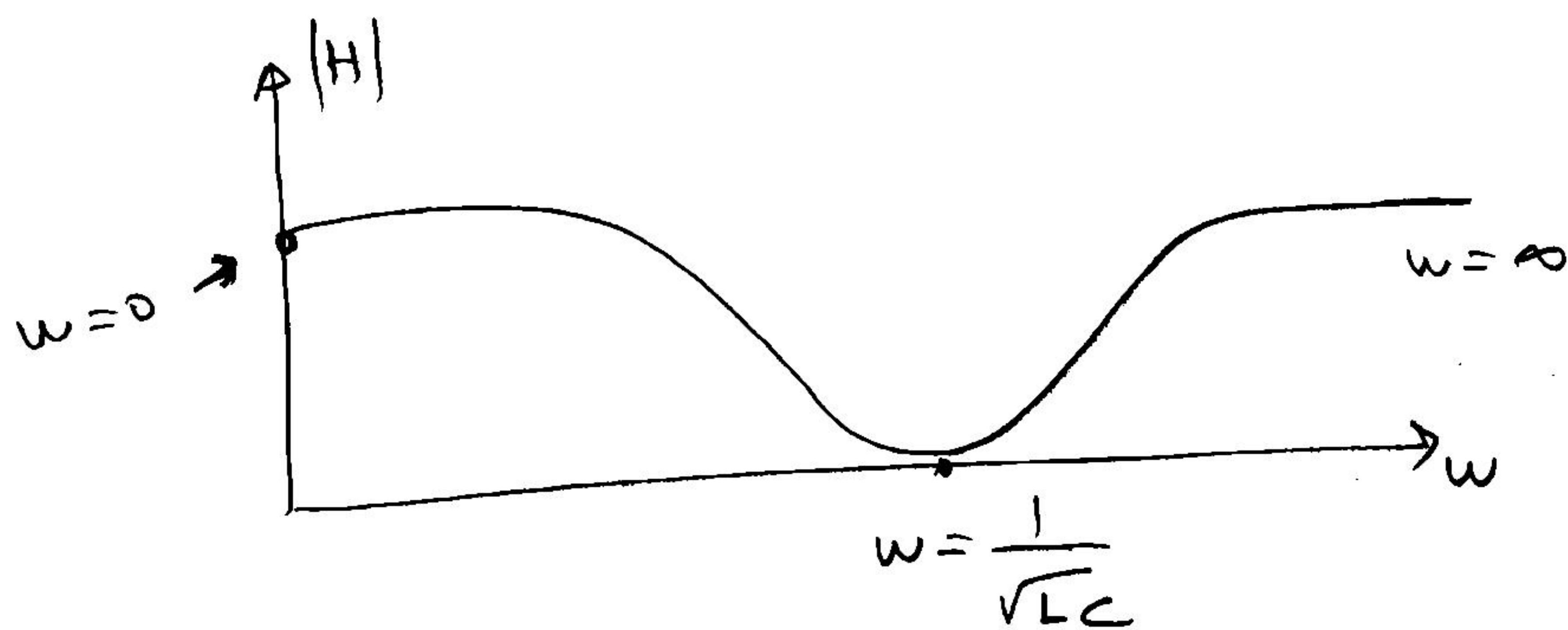

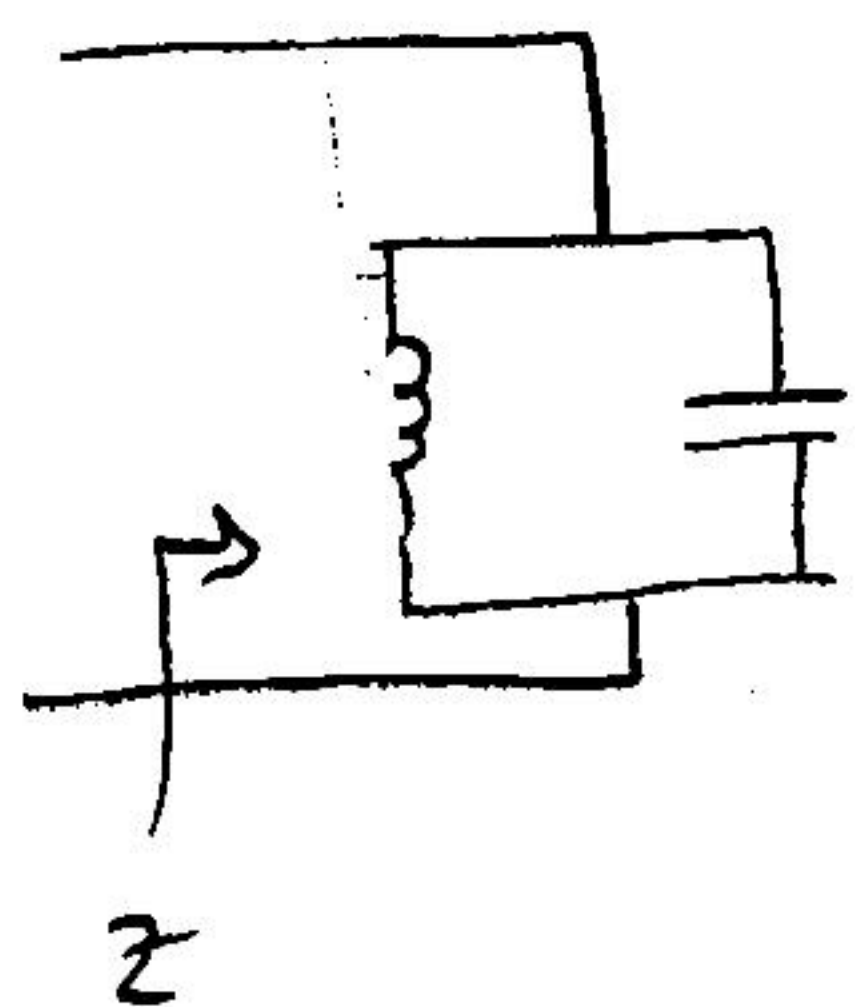


$$\frac{1}{z} = \frac{1}{j\omega L} + \frac{1}{\frac{1}{j\omega C}} = \frac{1}{j\omega L} + j\omega C = -\frac{j}{\omega L} + j\omega C$$

$$\frac{1}{z} = j\left(\omega C - \frac{1}{\omega L}\right) \Rightarrow z = \frac{1}{j\left(\omega C - \frac{1}{\omega L}\right)}$$


if $\omega C - \frac{1}{\omega L} = 0 \Rightarrow z = \frac{1}{0} = \infty$ (open circuit)

$$\omega C - \frac{1}{\omega L} = 0 \Rightarrow \omega C = \frac{1}{\omega L} \Rightarrow \omega^2 = \frac{1}{LC} \Rightarrow \omega = \frac{1}{\sqrt{LC}}$$

Parallel resonance

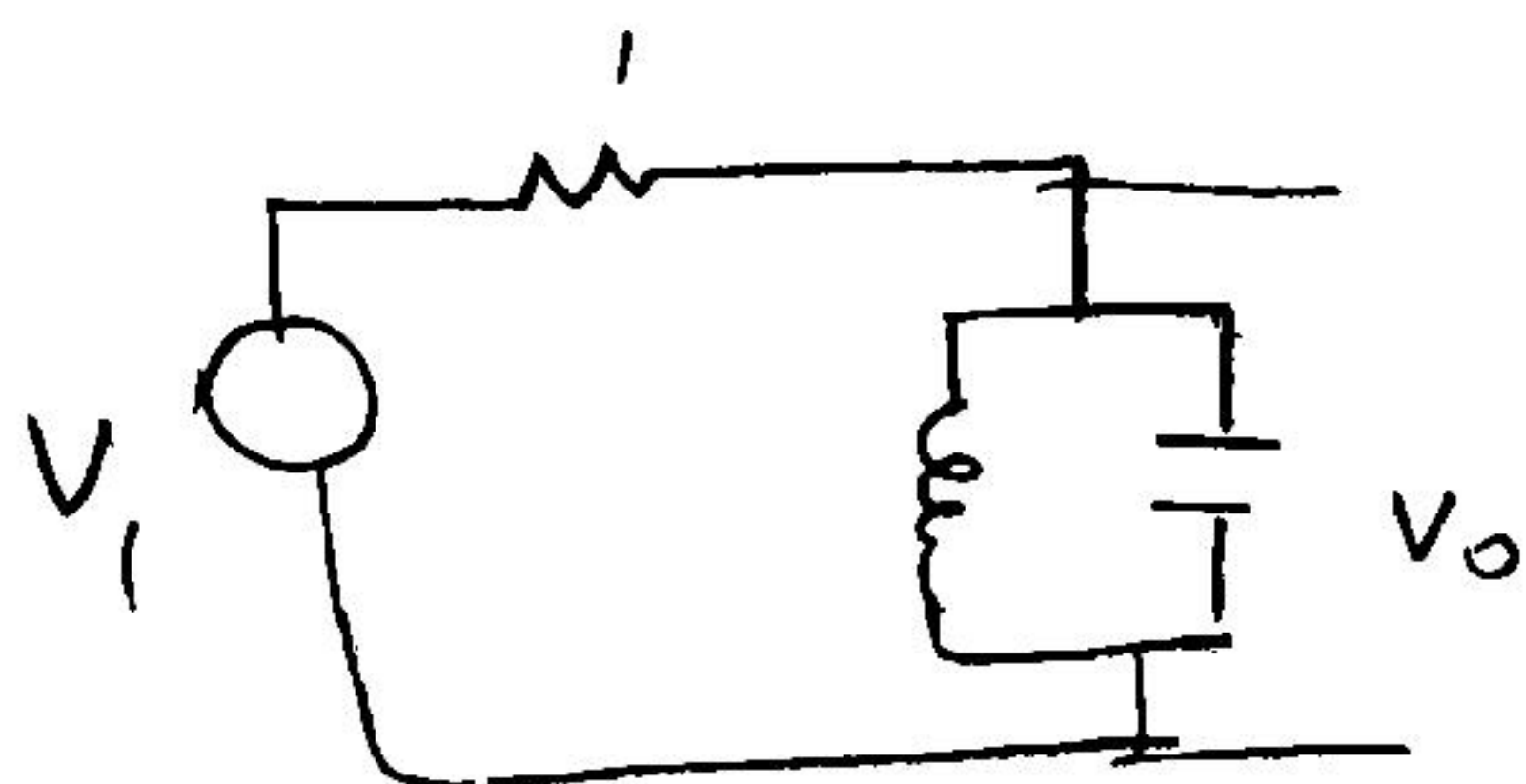


$$\omega = 0 \Rightarrow$$

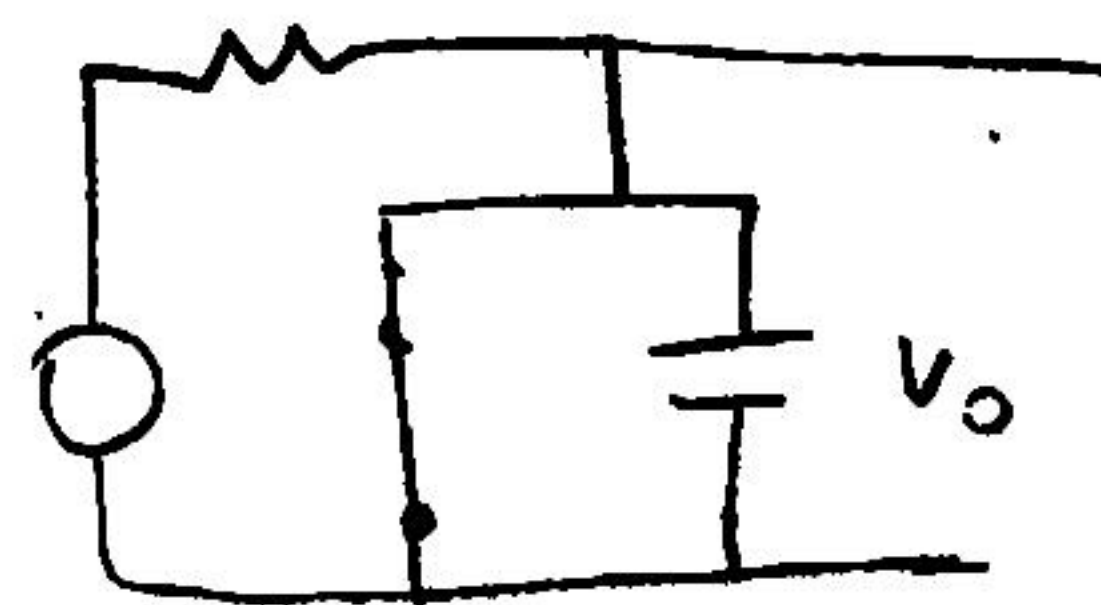

$$V_0 = 0$$

$$|H| = \left| \frac{V_0}{V_1} \right| = 0$$


$$\omega = \frac{1}{\sqrt{LC}}$$

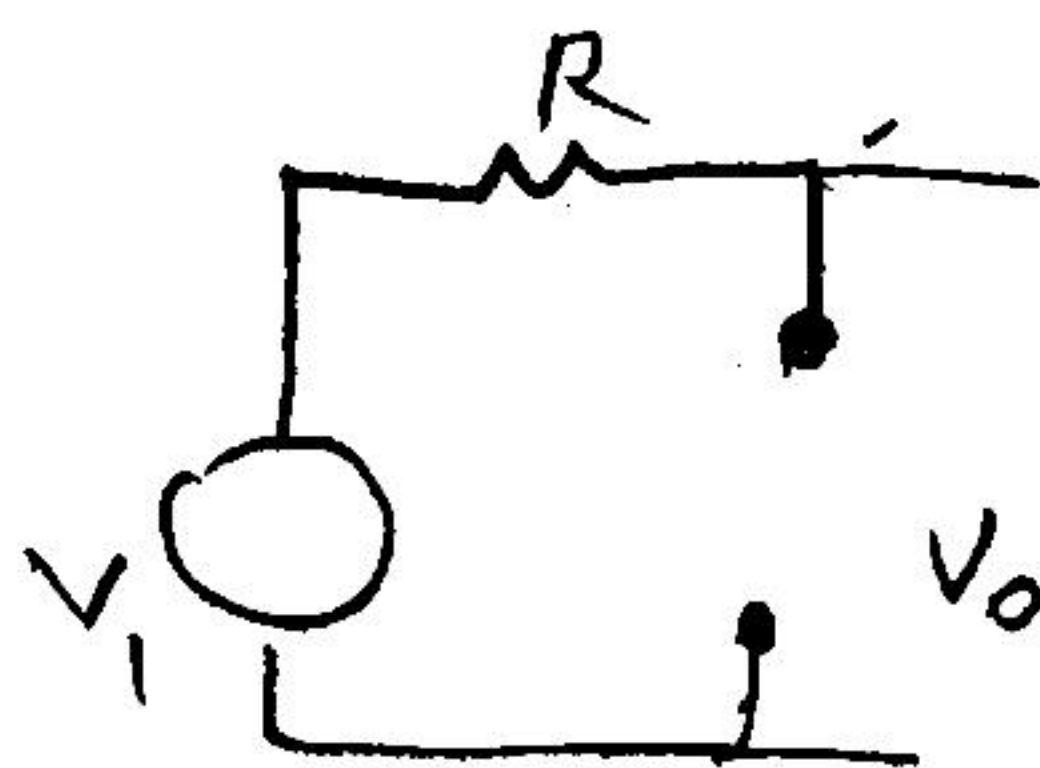

$$V_0 = V_1$$


$$|H| = \left| \frac{V_0}{V_1} \right| = 1$$

$$\omega = \infty$$

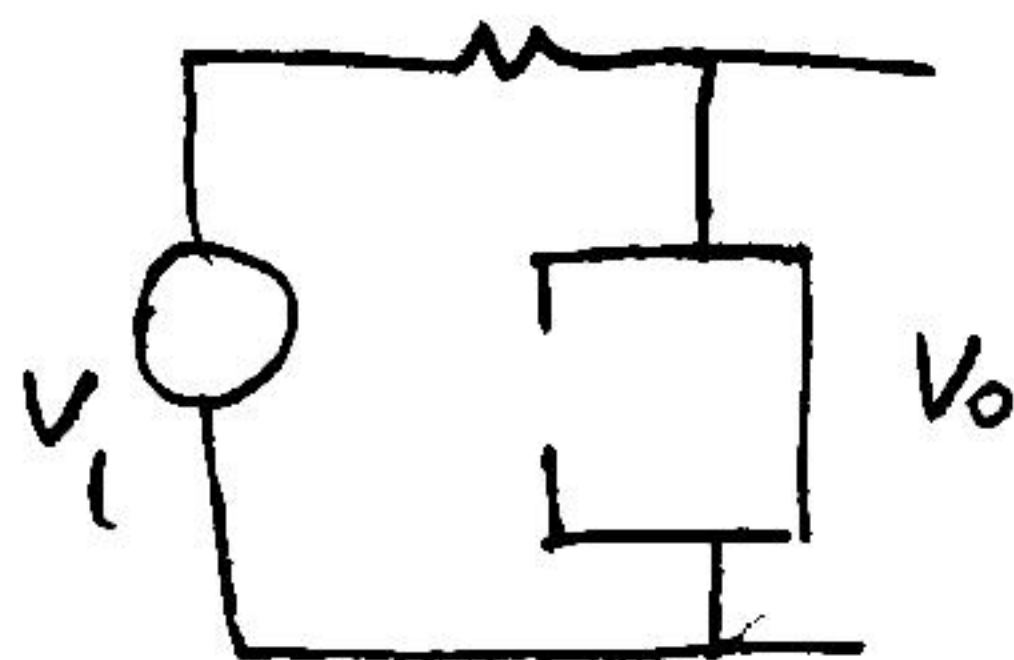

$$V_0 = 0$$

$$|H| = \left| \frac{V_0}{V_1} \right| = 0$$

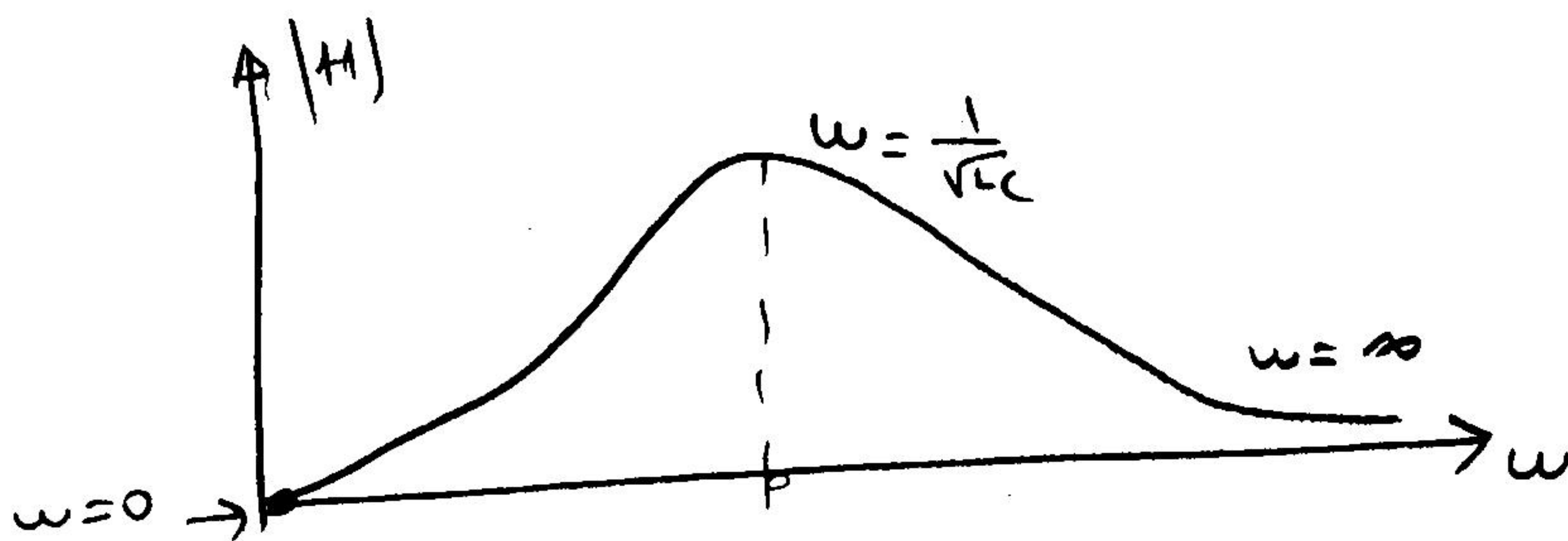

Parallel
resonance
circuit
response